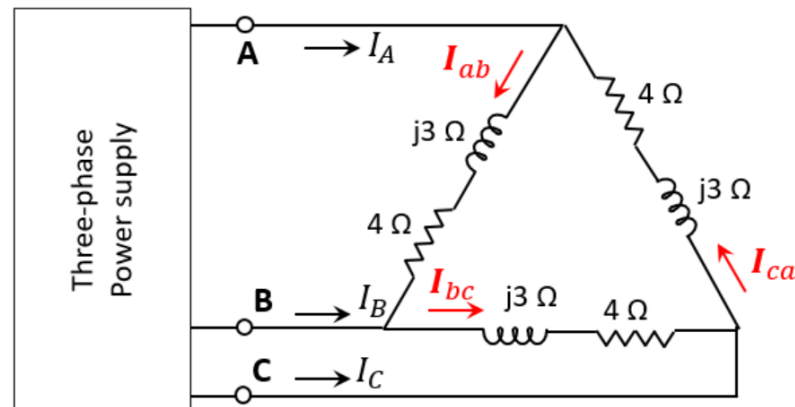


- 1 Consider a Δ -connected three phase balance load with phase impedance of $Z_p = (4 + j3) \Omega$. This load is supplied through a 3-phase power supply with line voltage of $V_L = 208 \text{ V}$.

- a) Find the line current I_L b) Find the complex power of the load
c) How do you compare the currents and voltages with the case of star connected load (results of the Week 5 class example)?

Solution:

- a) Schematic diagram of this three-phase system is given here:



Line voltage of this system is 208 V, so considering cba phase sequence a set of phase and line voltages for the power supply are:

Phase voltages:	Line voltages:
$V_{AN} = 120 \angle 0^\circ \text{ V}$	$V_{AB} = 208 \angle -30^\circ \text{ V}$
$V_{BN} = 120 \angle 120^\circ \text{ V}$	$V_{BC} = 208 \angle 90^\circ \text{ V}$
$V_{CN} = 120 \angle -120^\circ \text{ V}$	$V_{CA} = 208 \angle -150^\circ \text{ V}$

For Δ -connected loads, line voltages are applied across the phase impedance (on other word $V_{ph} = V_L$), therefore in this analysis line voltages are used.

To find the line currents, first we need to find the phase currents:

$$I_{ab} = \frac{V_{AB}}{Z_{AB}} = \frac{208 \angle -30^\circ}{4 + j3} = \frac{208 \angle -30^\circ}{5 \angle 36.87^\circ} = 41.7 \angle -66.87^\circ \text{ A}$$

$$I_{bc} = \frac{V_{BC}}{Z_{BC}} = \frac{208 \angle 90^\circ}{4 + j3} = 41.7 \angle 53.13^\circ \text{ A}$$

$$I_{ca} = \frac{V_{CA}}{Z_{CA}} = \frac{208 \angle -150^\circ}{4 + j3} = 41.7 \angle -186.87^\circ \text{ A}$$

Line currents can be calculated by applying KCL to each node of the circuit:

$$I_A = I_{ab} - I_{ca} = 41.7 \angle -66.87^\circ - 41.7 \angle -186.87^\circ = 72 \angle -36.9^\circ \text{ A}$$

$$I_B = I_{bc} - I_{ab} = 72 \angle 83.1^\circ \text{ A}$$

$$I_C = I_{ca} - I_{bc} = 72 \angle 203.1^\circ \text{ A}$$

- b) To find the complex power of the load, we can calculate active and reactive powers individually:

$$P_L = \sqrt{3}V_L I_L \cos \varphi = \sqrt{3} \times 208 \times 72 \times \cos(36.87^\circ) = 20.87 \text{ kW}$$

$$Q_L = \sqrt{3}V_L I_L \sin \varphi = \sqrt{3} \times 208 \times 72 \times \sin(36.87^\circ) = 15.65 \text{ kVAR}$$


$$S_L = 20.87 + j15.65 \text{ KVA}$$

- c) Ratio of the line current of Δ connection to Y connection is:

$$\frac{I_{L\Delta}}{I_{LY}} = \frac{72}{24} = 3$$

This is the case for any three phase balanced load.

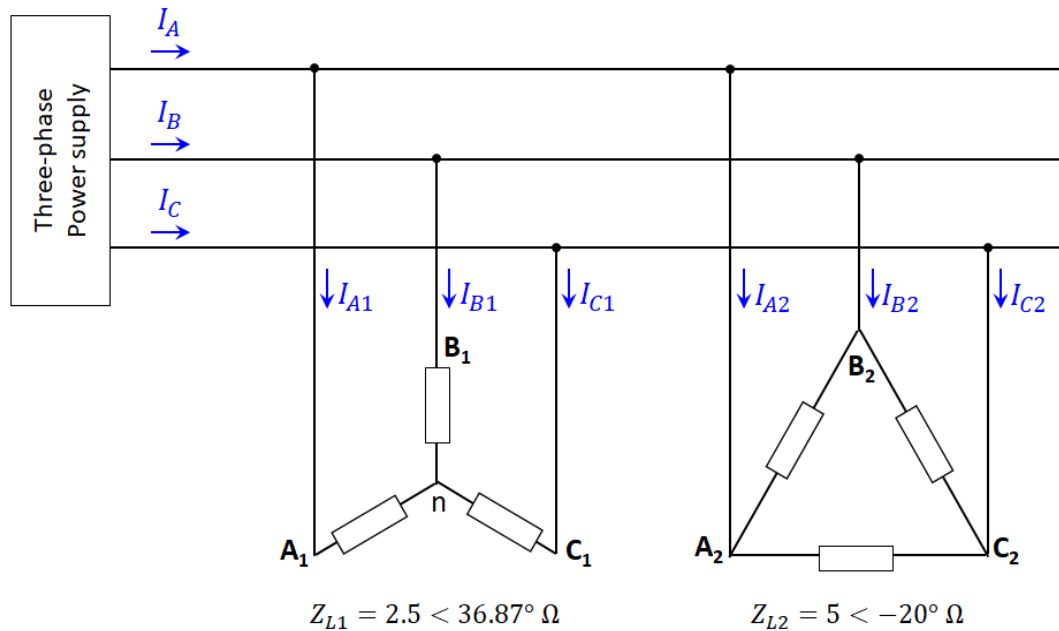- 2 A three phase power supply with line voltage of $V_L=400$ V supplies to balanced loads as shown in the schematic diagram. Load # 1 has phase impedance of $Z_{L1} = 2.5 \angle 36.87^\circ \Omega$ with λ connection, and load # 2 has phase impedance of $Z_{L2} = 5 \angle -20^\circ \Omega$ with Δ connection.



- Find the line current of the source
- Find the complex power of the source

Solution:

- In this network first we need to find current of each load. Considering a positive phase sequence, line and phase voltages are:

Phase voltages	Line voltages
$V_A = 230 \angle 0^\circ \text{ V}$	$V_{AB} = 400 \angle 30^\circ \text{ V}$
$V_B = 230 \angle -120^\circ \text{ V}$	$V_{BC} = 400 \angle -90^\circ \text{ V}$
$V_C = 230 \angle 120^\circ \text{ V}$	$V_{CA} = 400 \angle 150^\circ \text{ V}$

For the Y connected load:

$$I_{A1} = \frac{V_A}{Z_{L1}} = \frac{230 \angle 0^\circ}{2.5 \angle 36.86^\circ} = 92 \angle -36.86^\circ \text{ A}$$

$$I_{B1} = 92 \angle -156.86^\circ \text{ A} \quad I_{C1} = 92 \angle 83.14^\circ \text{ A}$$

Therefore, power analysis of this load is:

$$P_{L1} = \sqrt{3}V_L I_L \cos \varphi = \sqrt{3} \times 400 \times 92 \times \cos(36.86^\circ) = 51.2 \text{ kW}$$

$$Q_{L1} = \sqrt{3}V_L I_L \sin \varphi = \sqrt{3} \times 400 \times 92 \times \sin(36.86^\circ) = 38.4 \text{ kVAR}$$

$$S_{L1} = 51.2 + j38.4 \text{ KVA}$$

Similar analysis for the Δ connected load:

Phase currents:

$$I_{AB2} = \frac{V_{AB}}{Z_{p2}} = \frac{400 \angle 30^\circ}{5 \angle -20^\circ} = 80 \angle 50^\circ \text{ A}$$

$$I_{BC2} = 80 \angle -70^\circ \text{ A} \quad I_{CA2} = 80 \angle 170^\circ \text{ A}$$

Line currents:

$$I_{A2} = I_{AB2} - I_{CA2} = 80 \angle 50^\circ - 80 \angle 170^\circ = 138.55 \angle 20^\circ \text{ A}$$

$$I_{B2} = I_{BC2} - I_{AB2} = 138.55 \angle -100^\circ \text{ A}$$

$$I_{C2} = I_{CA2} - I_{BC2} = 138.55 \angle 140^\circ \text{ A}$$

And power analysis of this load is:

$$P_{L2} = \sqrt{3}V_L I_L \cos \varphi = \sqrt{3} \times 400 \times 138.55 \times \cos(-20^\circ) = 90.2 \text{ kW}$$

$$Q_{L2} = \sqrt{3}V_L I_L \sin \varphi = \sqrt{3} \times 400 \times 138.55 \times \sin(-20^\circ) = -32.83 \text{ kVAR}$$

$$S_{L2} = 90.2 - j32.83 \text{ KVA}$$

b) Total current of the source:

$$I_A = I_{A1} + I_{A2} = 92 \angle -36.86^\circ + 138.55 \angle 20^\circ = 203.95 \angle -2.2^\circ \text{ A}$$

$$I_C = I_{B1} + I_{B2} = 203.95 \angle -122.2^\circ \text{ A}$$

$$I_C = I_{C1} + I_{C2} = 203.95 \angle 117.8^\circ \text{ A}$$

And finally power analysis of the source is:

$$P_{Lt} = \sqrt{3} V_L I_L \cos \varphi = \sqrt{3} \times 400 \times 203.95 \times \cos(2.2^\circ) = 141.2 \text{ kW}$$

$$Q_{Lt} = \sqrt{3} V_L I_L \sin \varphi = \sqrt{3} \times 400 \times 203.95 \times \sin(2.2^\circ) = 5.45 \text{ kVAR}$$

$$S_{Lt} = 141.2 + j5.45 \text{ KVA}$$

Total power of the source can be also calculated by adding power of the individual load:

$$P_{Lt} = P_{L1} + P_{L2} \qquad Q_{Lt} = Q_{L1} + Q_{L2}$$

Negative sign of the total current I_A shows that the total impedance seen by the source has an inductive nature with lagging power factor.