

# Electrical Engineering II

## ENGL2191

Circuit Analysis in Phasor Domain

**Dr Hamed Bahmani**  
**Hamed.h.bahmani@Durham.ac.uk**  
**E108**



## Lecture Objectives:

### Aim of this lecture:

The aim of this lecture is to analyse electric circuits in phasor domain.


### Intended Learning Outcomes:

**At the completion of the lecture and associated problems you should be able to:**


- Understand the characteristics of sinusoidal functions.
- Identify phasor representation of sinusoids.
- Converting between time and frequency domains.
- Identify the performance of the basic ideal circuit elements in phasor domain.
- Analyse the electric circuits in phasor domain.



# Physics of Basic Electric Elements


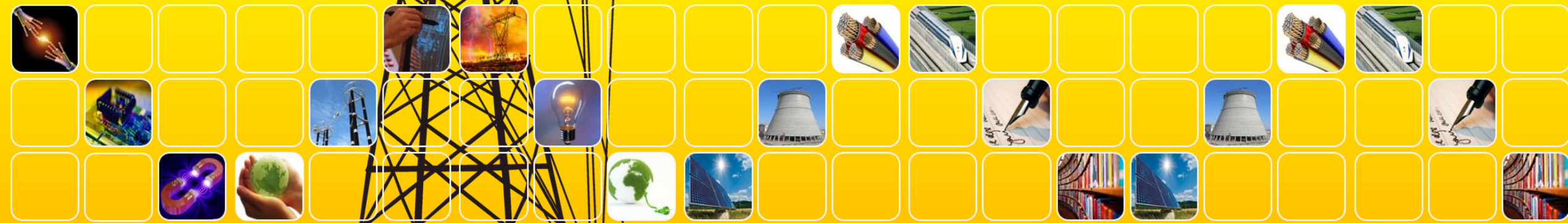


## Ideal Electric Elements:

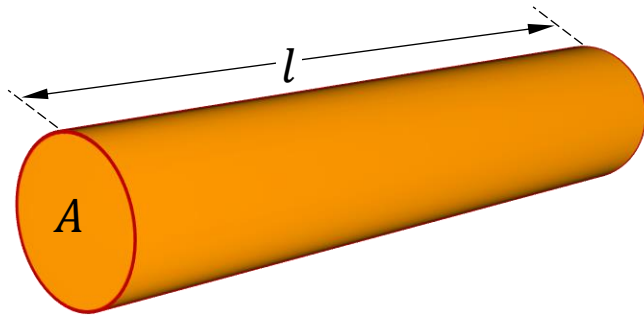



$$R = \rho \frac{l}{A}$$

$$V = R I$$

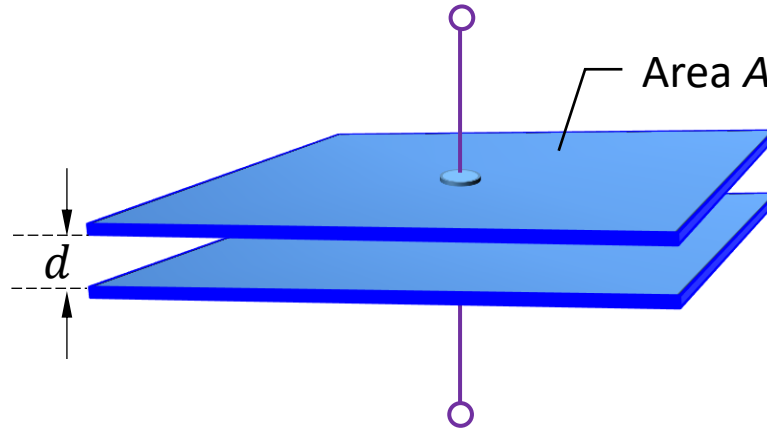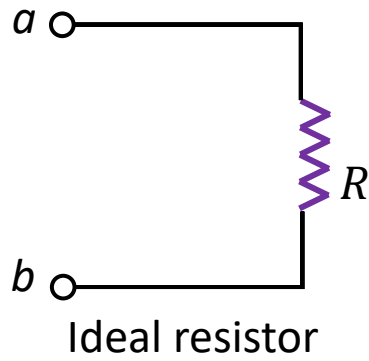


$$C = \epsilon_0 \frac{A}{d}$$

$$q = C V$$

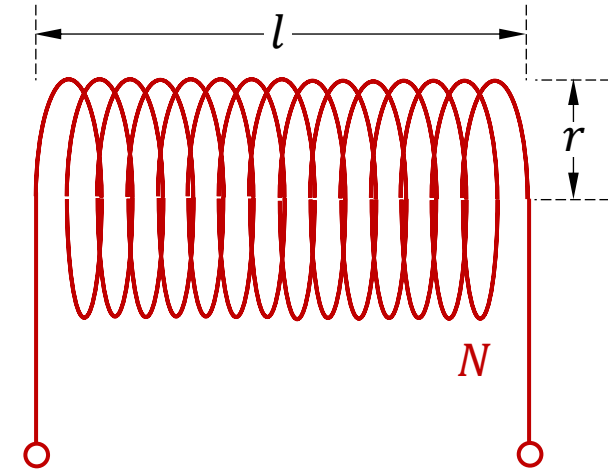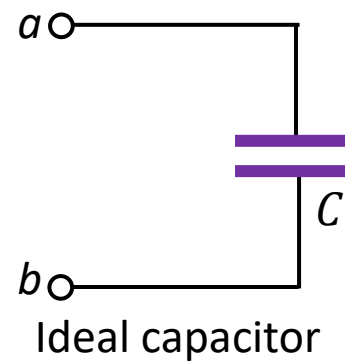

$$L = \mu_0 \frac{N^2 A}{l}$$

$$\Phi_B = L I$$

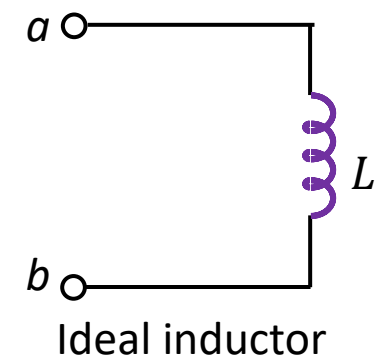

**Resistance  $R$ , capacitance  $C$  and self-inductance  $L$  are purely geometric.**




## Ideal Electric Elements:

### Different types of Resistors:




### Colour Code Resistor

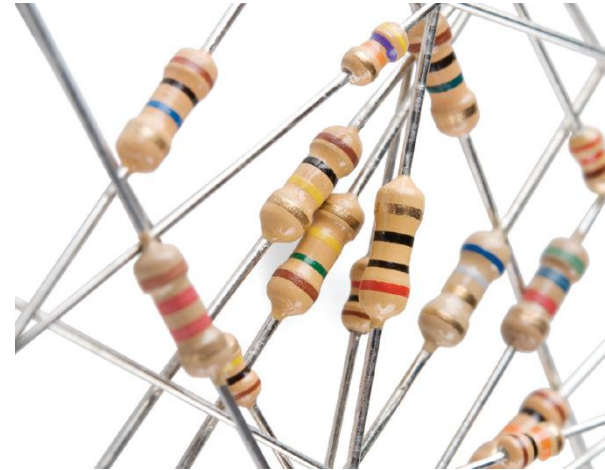


### Power Resistor



Photo Sensor

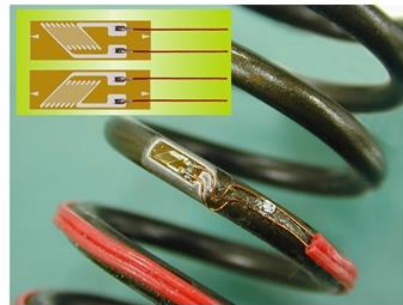

Strain Gauge

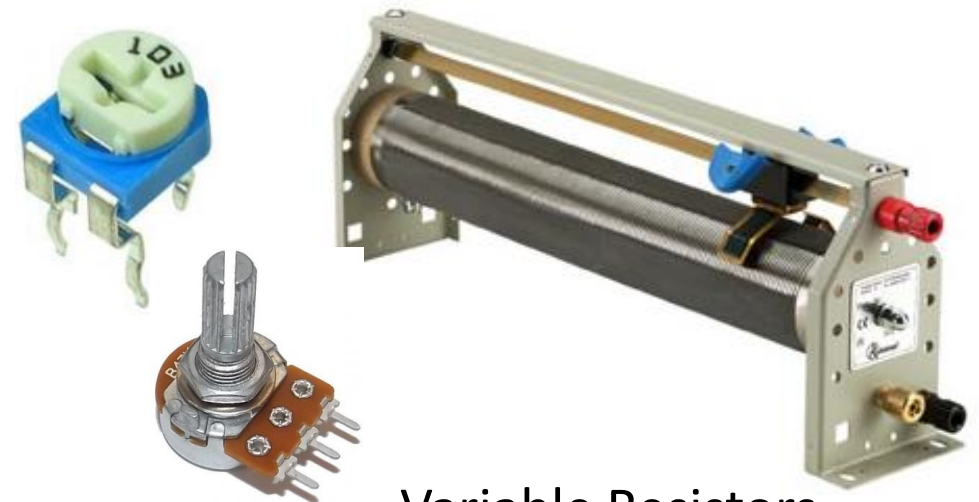


Variable Resistors



## Ideal Electric Elements:

### Different types of Capacitors:

Fixed capacitors

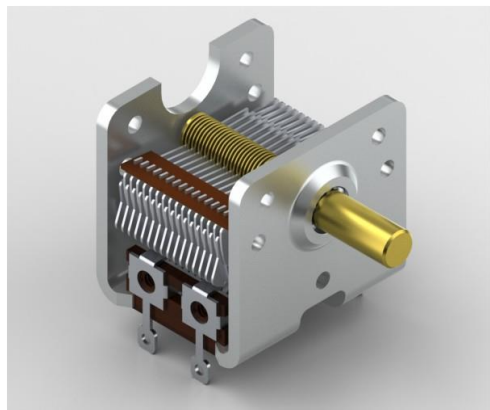

Variable capacitors



400 kV capacitor bank in power system




## Ideal Electric Elements:

### Different types of Inductors:



Inductors used in  
electronic circuits

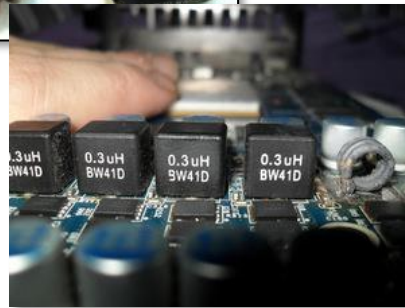

Current-limiting inductor installed at a 345 kV  
power plant in South Korea








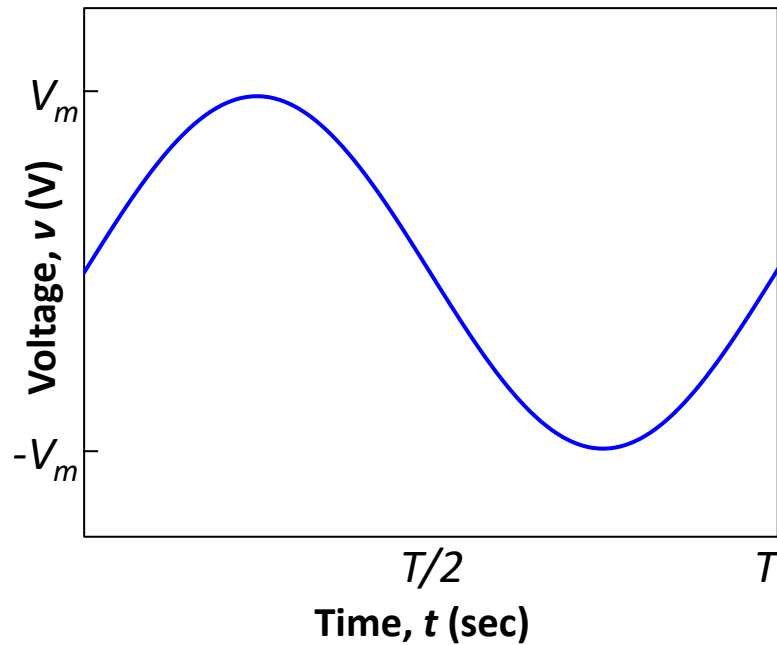
## Alternating Currents and Phasors:

$$v(t) = V_m \sin(\omega t \pm \varphi)$$




$$V(\omega) = V_m \angle \pm \varphi$$

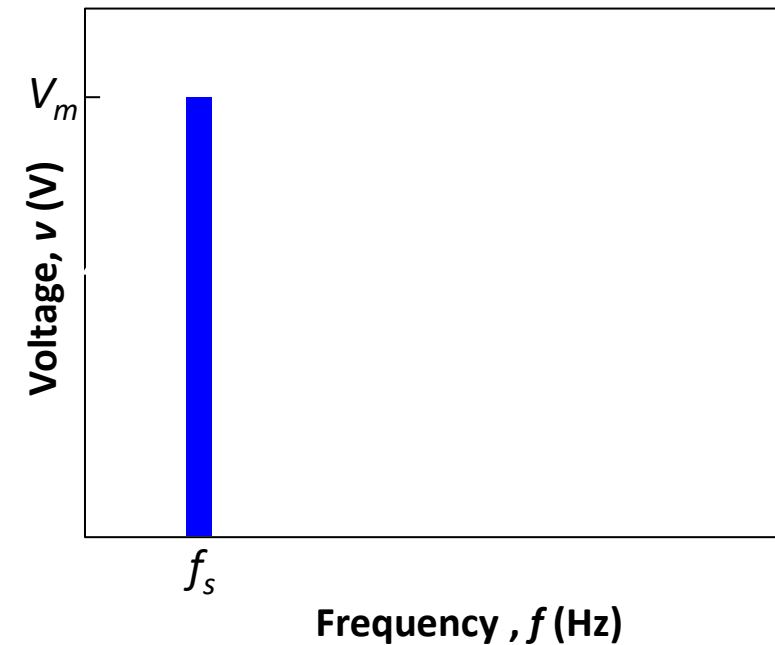

In engineering and physics, phasor is a complex number representing a sinusoidal function whose amplitude, angular frequency, and phase angle are time-invariant.
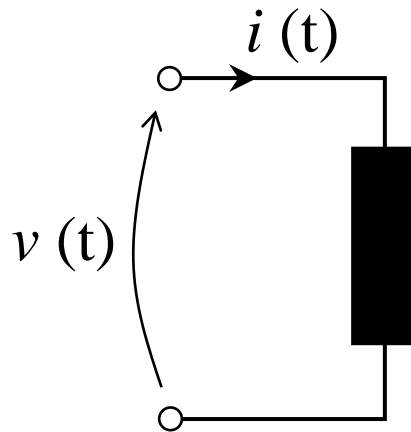
## ▶ Alternating Currents and Phasors:

Voltage and current representation  
in “time domain”




$$v(t) = V_m \sin(\omega t + \theta_v)$$

$$i(t) = I_m \sin(\omega t + \theta_i)$$



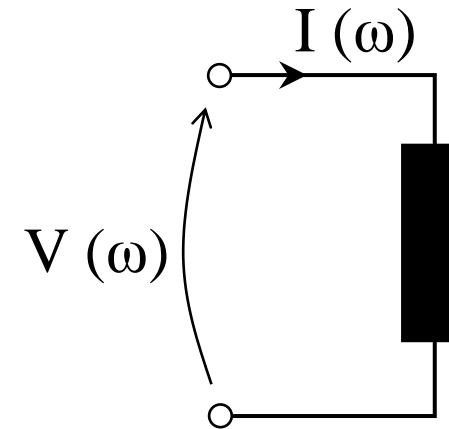Voltage and current representation  
in “frequency domain”




$$V(\omega) = V_{rms} \angle \theta_v$$

$$I(\omega) = I_{rms} \angle \theta_i$$

▶▶▶ In network analysis, phasor of voltage and current are given as the *rms* values.





## Alternating Currents and Phasors:

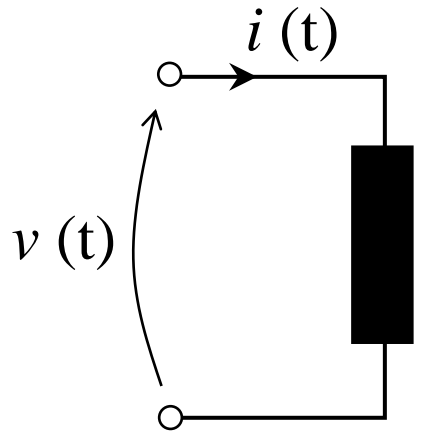


$$v(t) = 100 \times \sqrt{2} \sin(\omega t + 10)$$
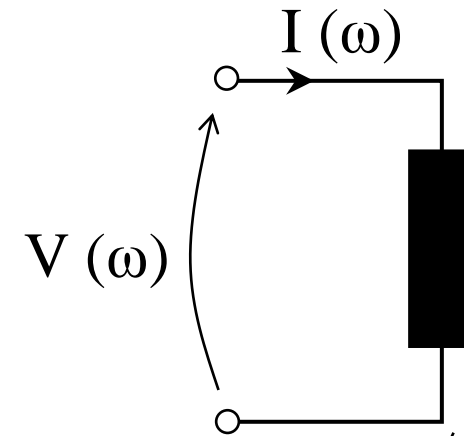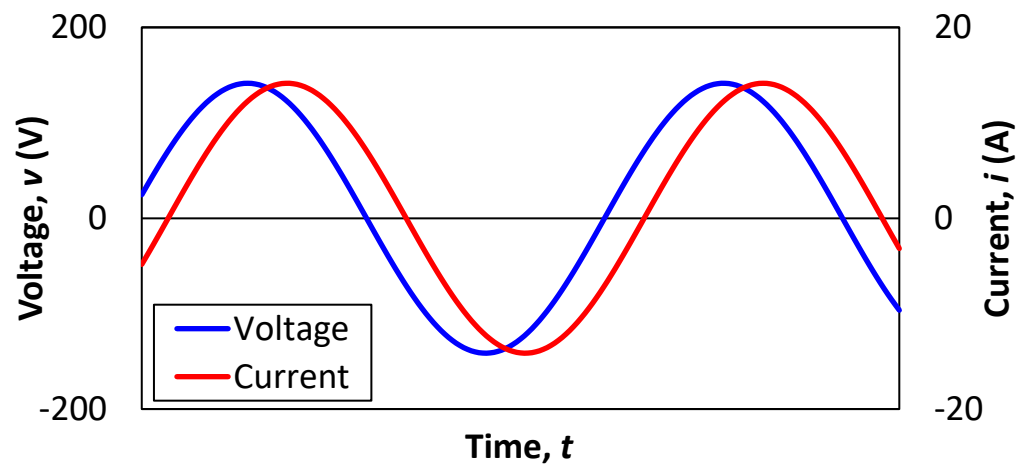
$$i(t) = 10 \times \sqrt{2} \sin(\omega t - 20)$$





$$V(\omega) = 100 \angle +10^\circ \text{ V}$$
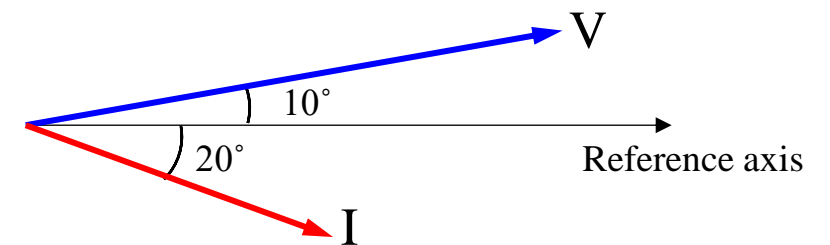
$$I(\omega) = 10 \angle -20^\circ \text{ A}$$


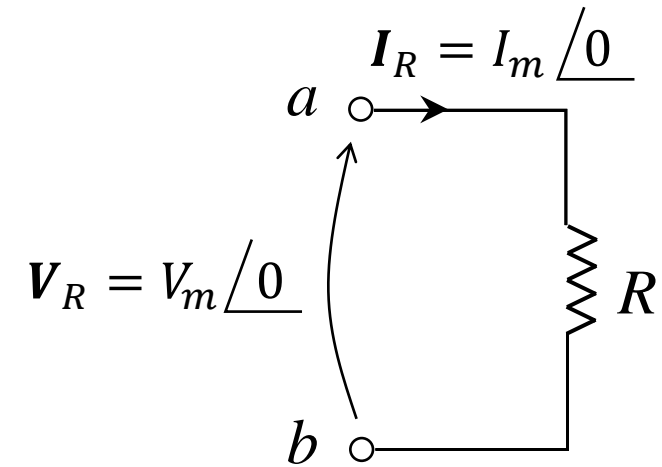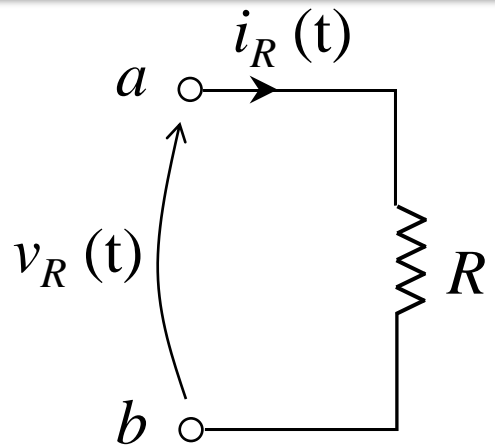
## Performance of a resistor in ac circuit:





$$i_R(t) = I_m \sin(\omega t)$$

We know from Ohm's law:

$$v_R(t) = R i_R(t)$$


$$v_R(t) = R I_m \sin(\omega t)$$

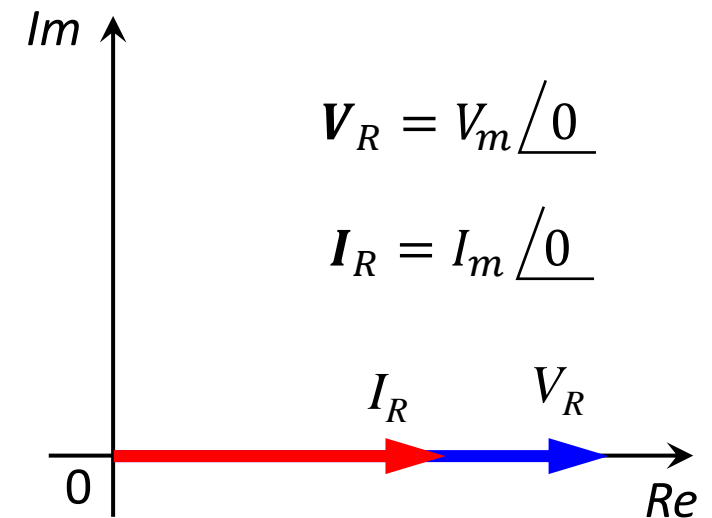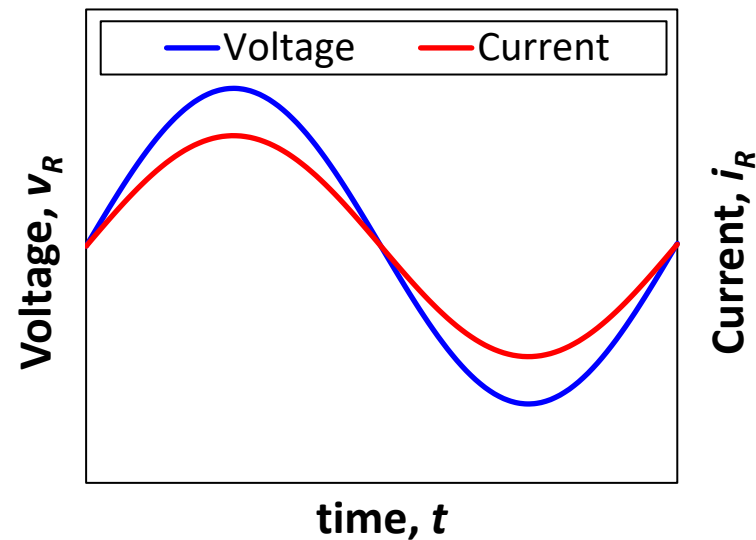

➤ In a pure resistor, the current and voltage are both “in-phase” as there is no phase difference between them.


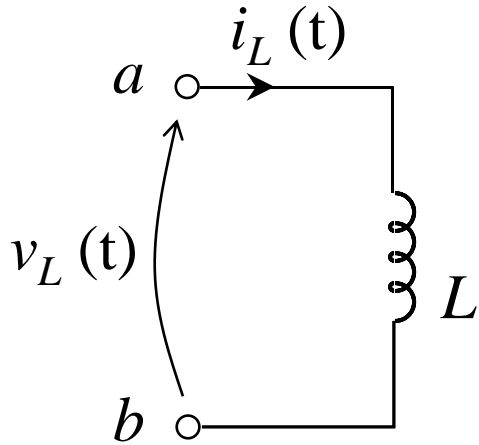
### Performance of an inductor in ac circuit:



$$i_L(t) = I_m \sin(\omega t)$$


$$v_L(t) = L \frac{di_L(t)}{dt} = L \frac{d(I_m \sin(\omega t))}{dt}$$

$$v_L(t) = L\omega I_m \cos(\omega t)$$

$$v_L(t) = L\omega I_m \sin(\omega t + 90^\circ)$$

$$i_L(t) = I_m \sin(\omega t)$$
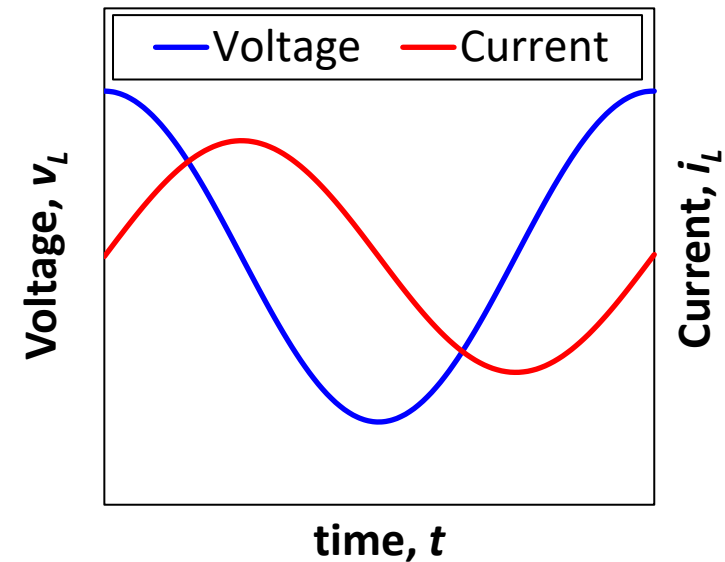
$$v_L(t) = L\omega I_m \sin(\omega t + 90^\circ)$$



### In pure inductive circuit:

Current lags the voltage by  $90^\circ$ .


Voltage leads the current by  $90^\circ$ .

## Performance of an inductor in ac circuit:

$$\begin{cases} i_L(t) = I_m \sin(\omega t) \\ v_L(t) = L\omega I_m \sin(\omega t + 90^\circ) \end{cases}$$

$$\begin{cases} \mathbf{I}_L = I_m \angle 0^\circ \quad [\text{A}] \end{cases}$$

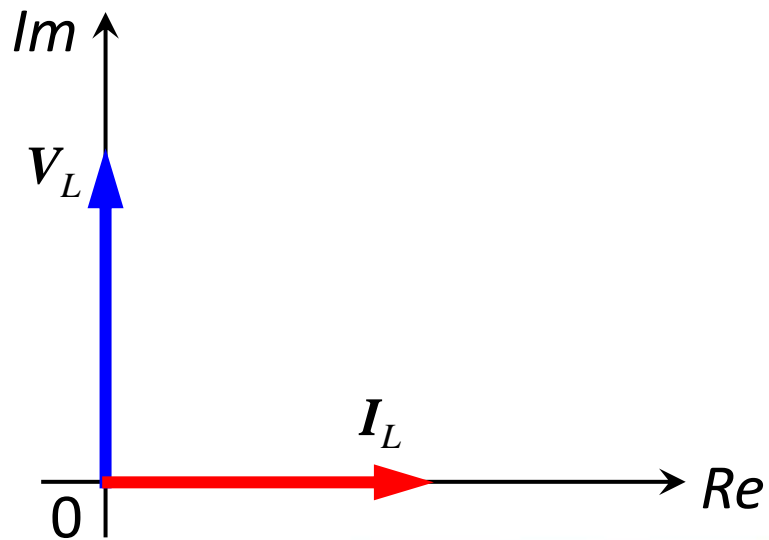
$$\begin{cases} \mathbf{V}_L = L\omega I_m \angle 90^\circ \quad [\text{V}] \end{cases}$$



From Ohm's law:


$$Z_L = \frac{\mathbf{V}_L}{\mathbf{I}_L} = \frac{L\omega I_m \angle 90^\circ}{I_m \angle 0^\circ} = L\omega \angle 90^\circ \quad [\Omega]$$
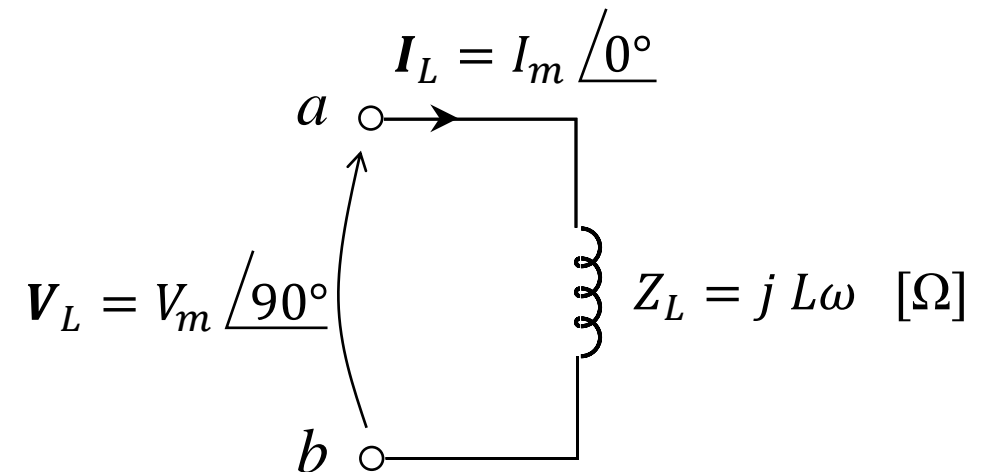
$$Z_L = j L\omega \quad [\Omega] \quad \text{Inductive impedance}$$




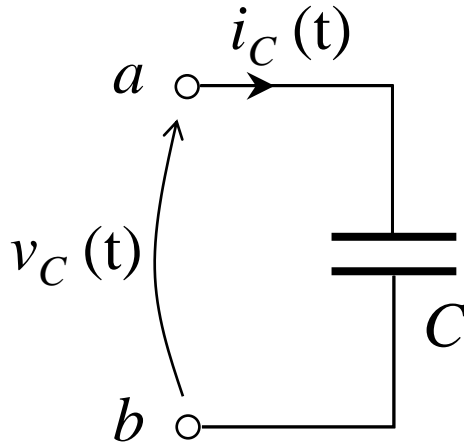
### Performance of an capacitor in ac circuit:



$$v_C(t) = V_m \sin(\omega t)$$


$$i_C(t) = C \frac{dv_C(t)}{dt} = C \frac{d(V \sin(\omega t))}{dt}$$

$$i_C(t) = C\omega V_m \cos(\omega t)$$

$$i_C(t) = C\omega V_m \sin(\omega t + 90^\circ)$$

$$v_C(t) = V_m \sin(\omega t)$$
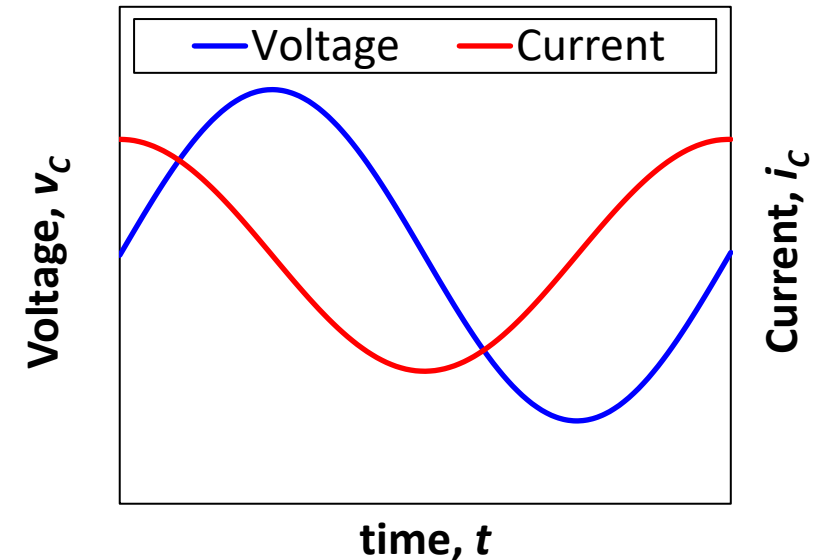
$$i_C(t) = C\omega V_m \sin(\omega t + 90^\circ)$$



### ➤➤ In a pure capacitive circuit:


Voltage lags the current by  $90^\circ$ .

Current leads the voltage by  $90^\circ$ .
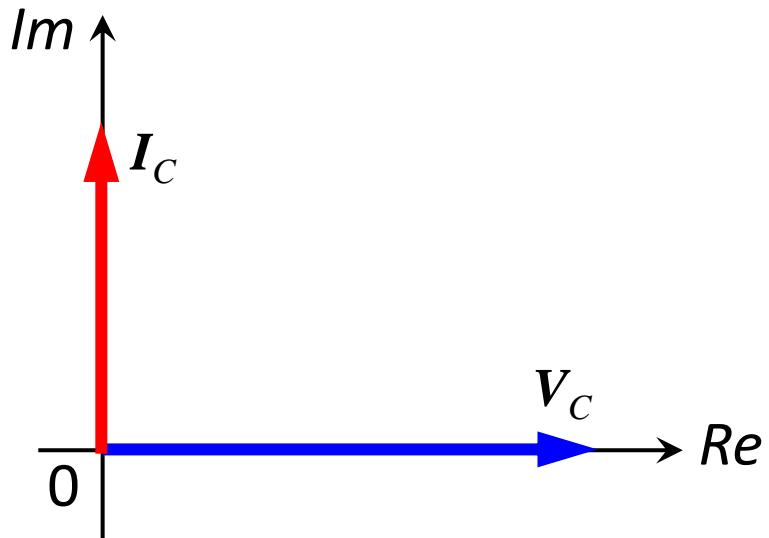
## Performance of an capacitor in ac circuit:

$$\begin{cases} v_C(t) = V_m \sin(\omega t) \\ i_C(t) = C\omega V_m \sin(\omega t + 90^\circ) \end{cases}$$


$$\begin{cases} V_C = V_m \angle 0^\circ & [\text{V}] \\ I_C = C\omega V_m \angle 90^\circ & [\text{A}] \end{cases}$$



From Ohm's law:







$$Z_C = \frac{V_C}{I_C} = \frac{V_m \angle 0^\circ}{C\omega V_m \angle 90^\circ} = \frac{1}{C\omega} \angle -90^\circ \quad [\Omega]$$
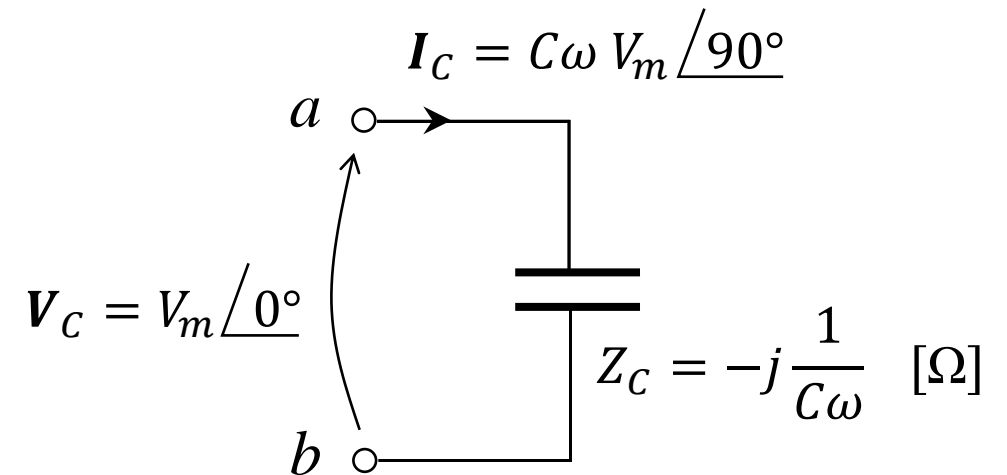
$$Z_C = -j \frac{1}{C\omega} \quad [\Omega] \quad \text{Capacitive impedance}$$










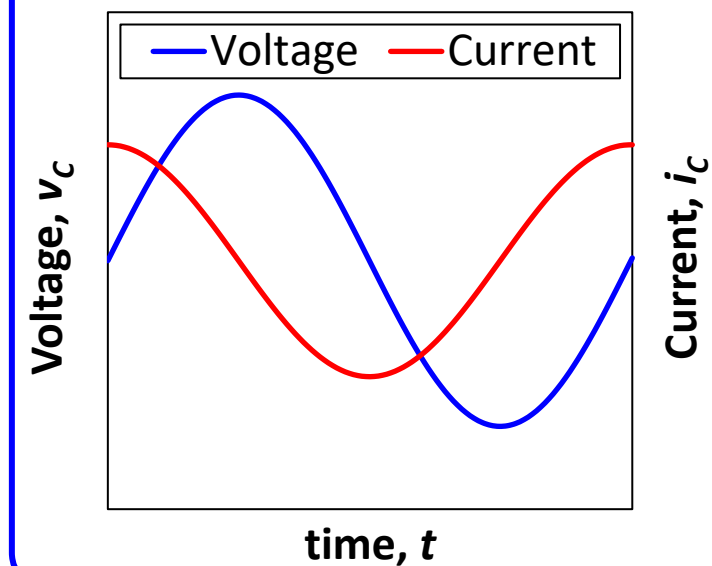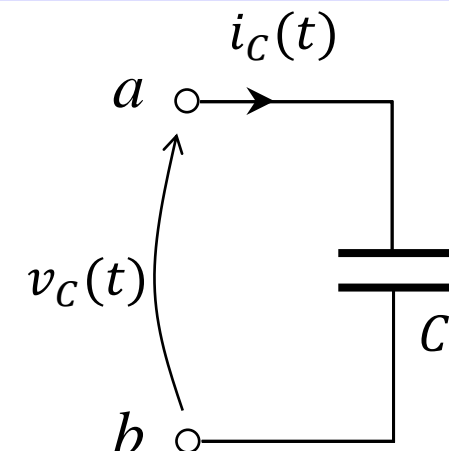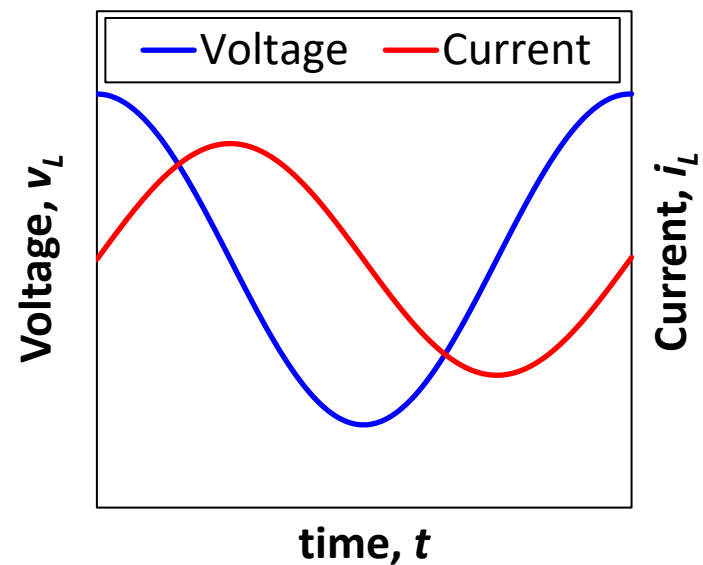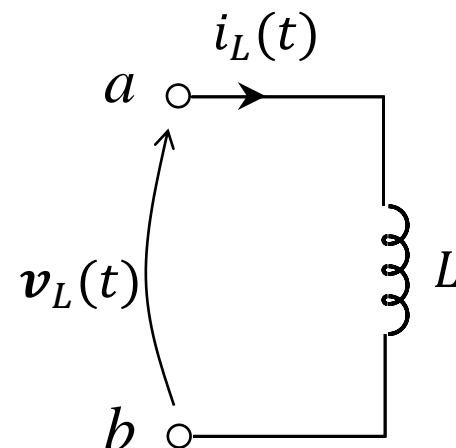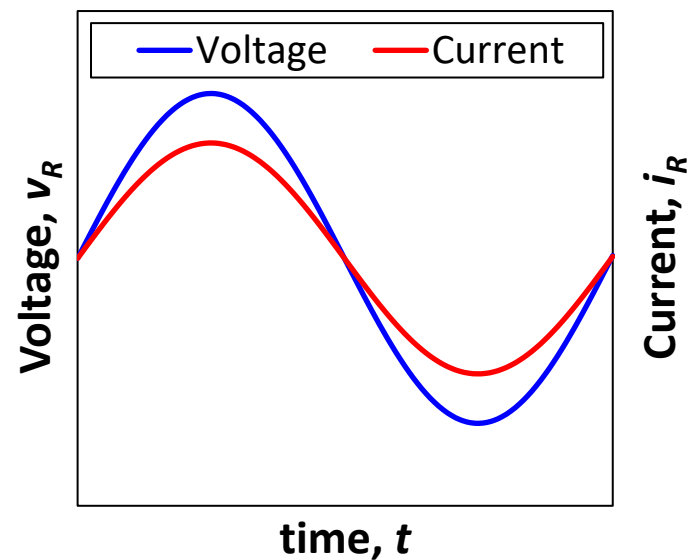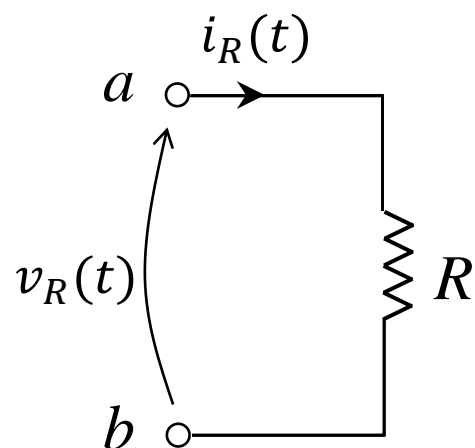
## Performance of ideal circuit elements in ac circuit:



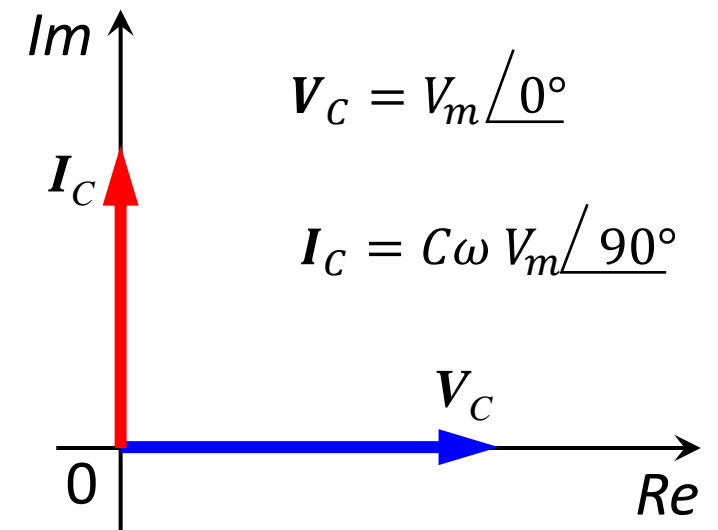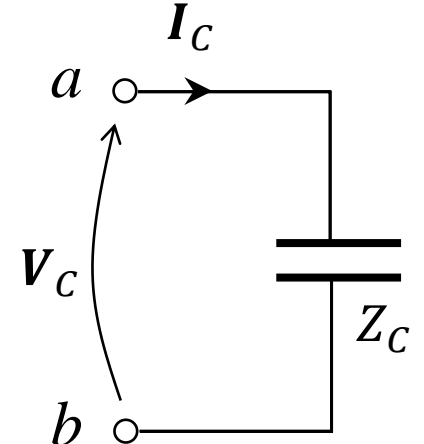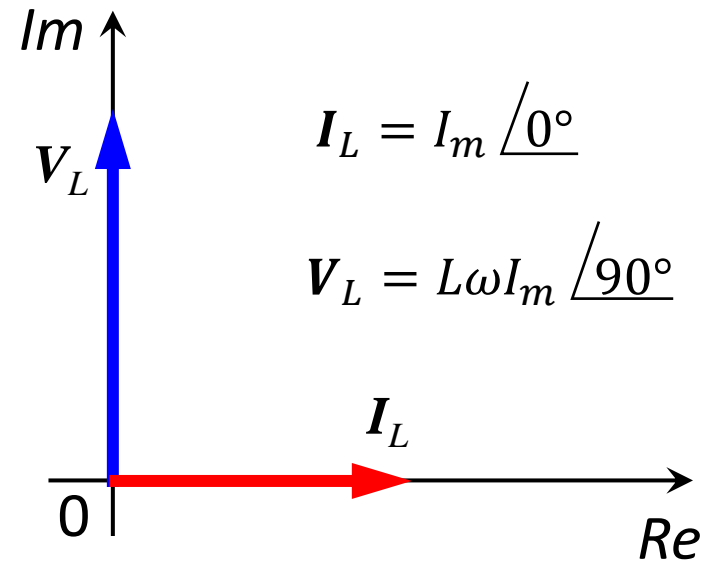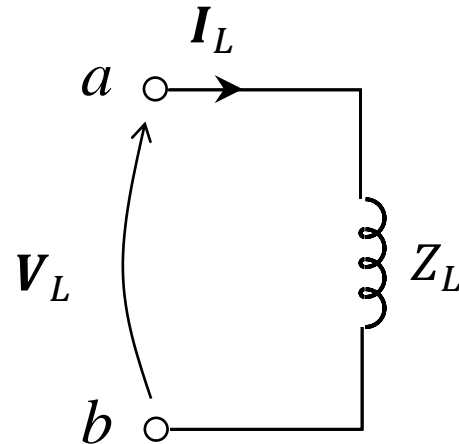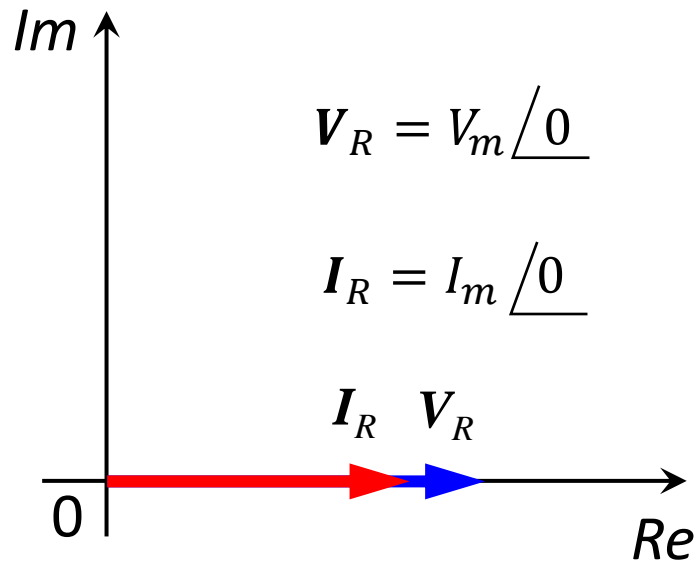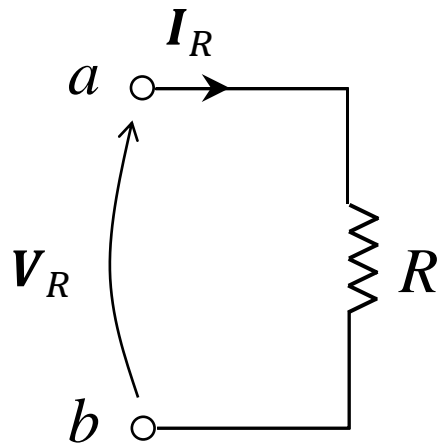
## Performance of ideal circuit elements in ac circuit:





## Performance of ideal circuit elements in ac circuit:

### Phasor impedance (Reactance):

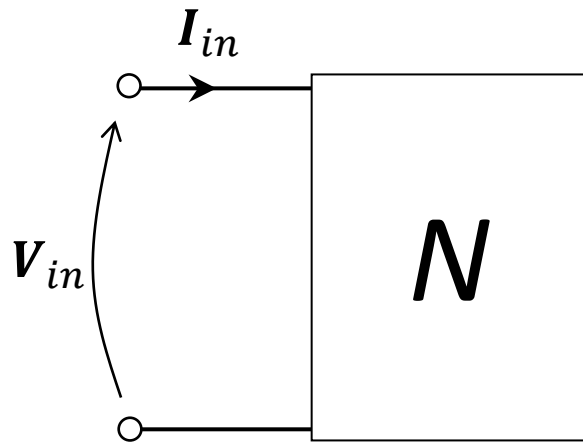

$$V_{in} = V_{rms} \angle \theta_v$$

$$I_{in} = I_{rms} \angle \theta_i$$

$$Z_{in} = \frac{V_{in}}{I_{in}} = \frac{V_{rms} \angle \theta_v}{I_{rms} \angle \theta_i}$$


$$Z_{in} = |Z| \angle \theta_v - \theta_i = |Z| \angle \varphi \quad [\Omega]$$

$$Z_{in} = \underbrace{|Z| \cos \varphi}_{\text{Resistive component}} + j \underbrace{|Z| \sin \varphi}_{\text{Reactive component (Inductive or Capacitive)}} \quad [\Omega]$$

Reactive component  
(Inductive or Capacitive)  
Resistive component

## Performance of ideal circuit elements in ac circuit:

### Example:


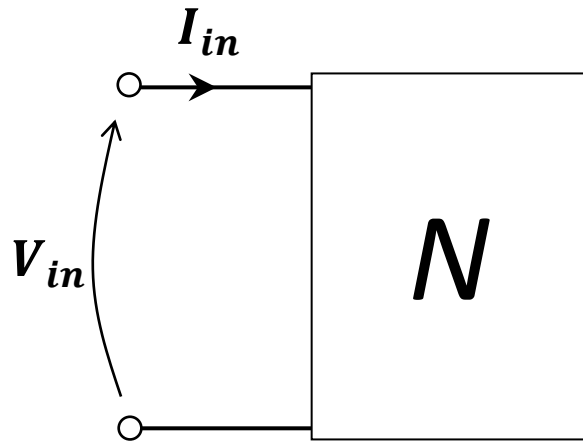


$$V_{in} = 75 \angle 60^\circ \text{ V}$$

$$I_{in} = 25 \angle 30^\circ \text{ A}$$

$$Z_{in} = \frac{V_{in}}{I_{in}} = \frac{75 \angle 60^\circ}{25 \angle 30^\circ} = 3 \angle 30^\circ \quad [\Omega]$$


$$Z_{in} = 2.6 + j1.5 \quad [\Omega]$$

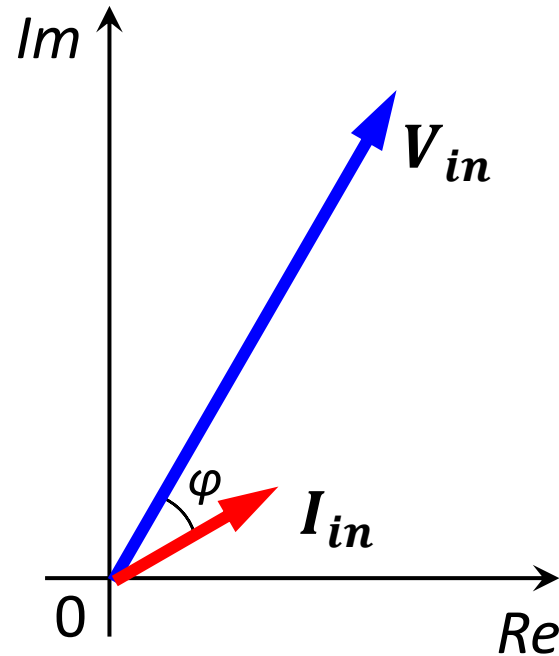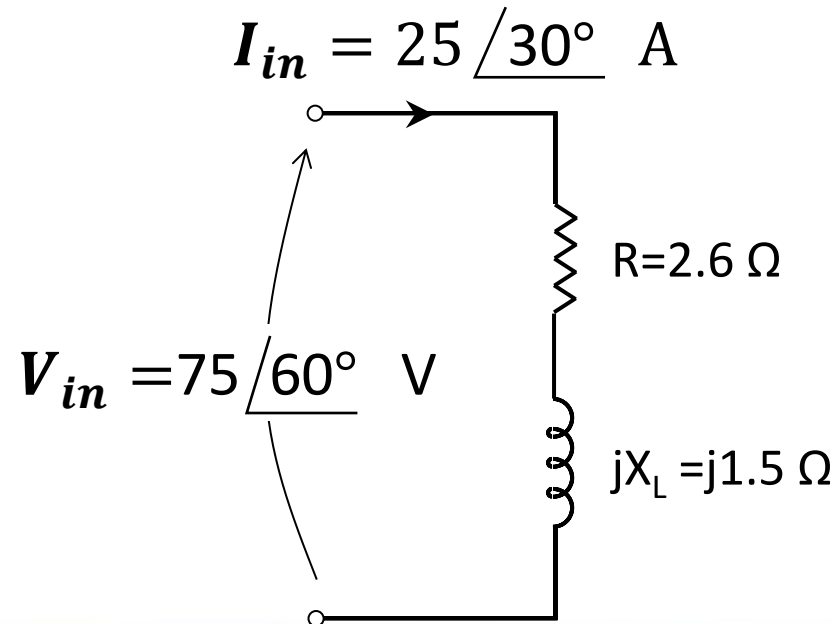



Performance of ideal circuit elements in ac circuit:

Example:


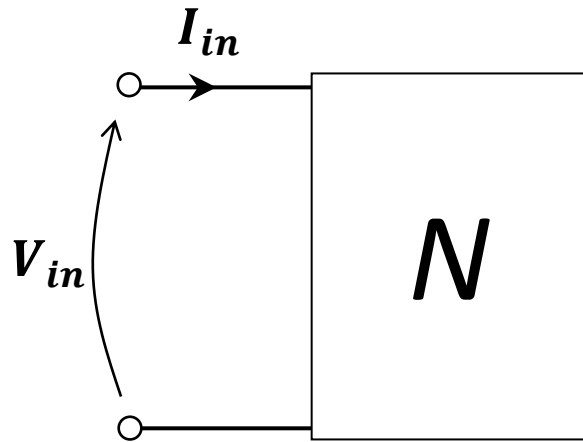


$$V_{in} = 75 \angle 30^\circ \text{ V}$$

$$I_{in} = 25 \angle 60^\circ \text{ A}$$

$$Z_{in} = \frac{V_{in}}{I_{in}} = \frac{75 \angle 30^\circ}{25 \angle 60^\circ} = 3 \angle -30 \quad [\Omega]$$

$$Z_{in} = 2.6 - j1.5 \quad [\Omega]$$

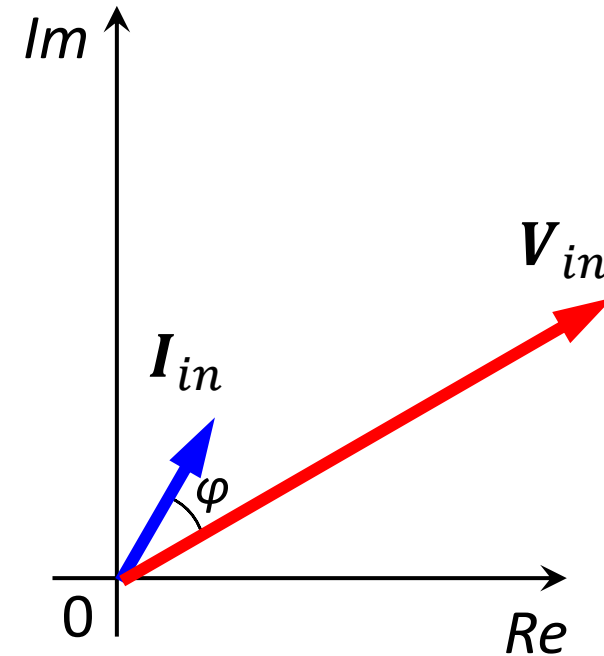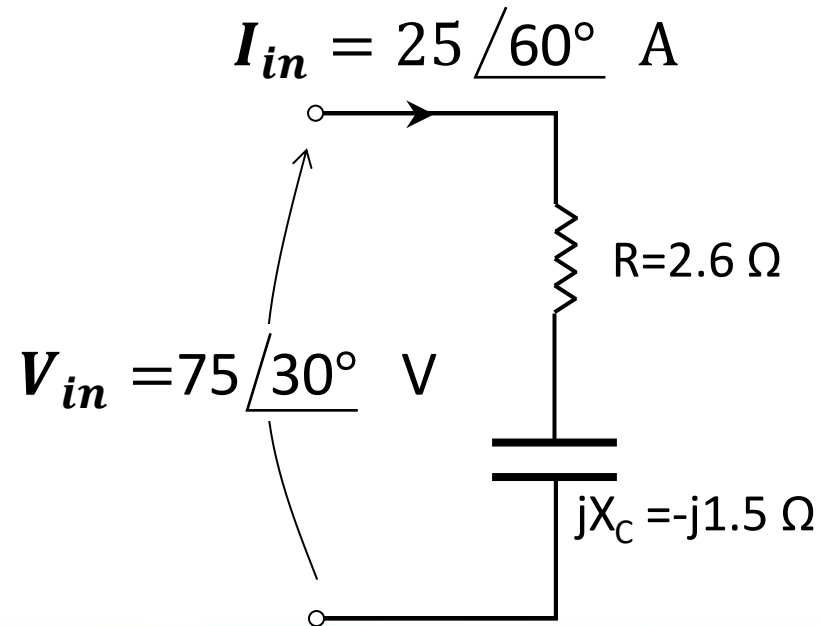


## Performance of ideal circuit elements in ac circuit:
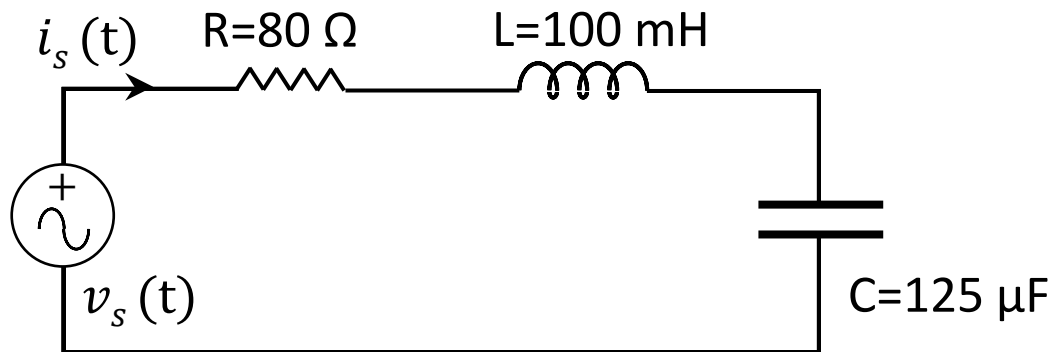
### Example:

Consider the following circuit:

- Convert the circuit to phasor
- Find the current
- Find the voltage drop on each element
- Draw the phasor diagram of the circuit




$$v_s(t) = 240\sqrt{2} \sin(200t)$$

$$X_L = j \omega L = j 200 \times 100 \times 10^{-3} = j 20\ \Omega$$

$$X_C = -j \frac{1}{\omega C} = -j \frac{1}{200 \times 125 \times 10^{-6}} = -j 40\ \Omega$$


$$V_s = 240 \angle 0^\circ\ \text{V}$$

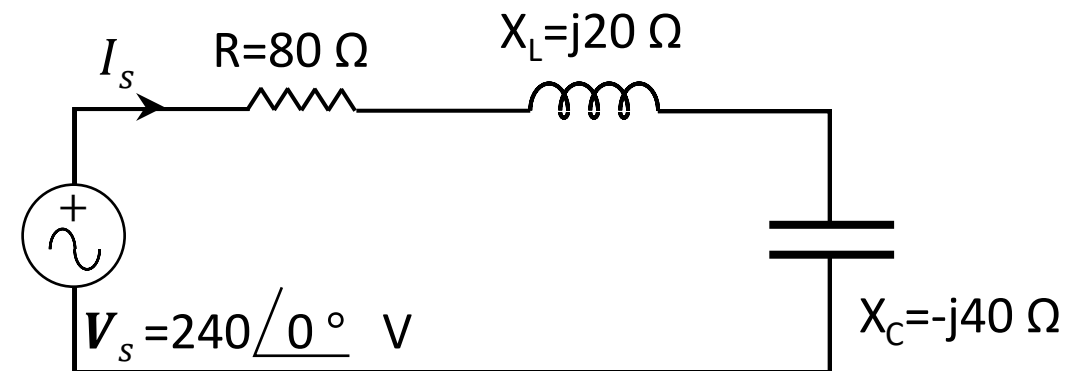



## Performance of ideal circuit elements in ac circuit:

### Example:

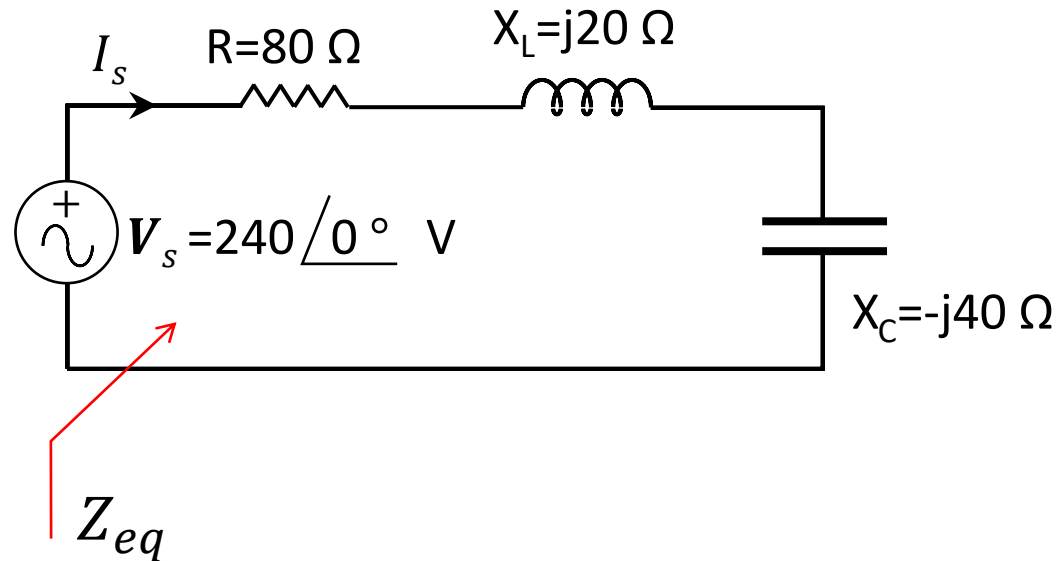

$$Z_{eq} = 80 + j20 - j40 = 80 - j20 \Omega$$

$$Z_{eq} = 82.46 \angle -14.03^\circ \Omega$$

$$I_s = \frac{240 \angle 0^\circ}{82.46 \angle -14.03^\circ} = 2.91 \angle 14.03^\circ \text{ A}$$




$$V_R = R I_s = 233.8 \angle 14.03^\circ \text{ V}$$

$$V_{X_L} = j X_L I_s = 58.2 \angle 104.03^\circ \text{ V}$$

$$V_{X_C} = -j X_C I_s = 116.4 \angle -75.97^\circ \text{ V}$$

## Performance of ideal circuit elements in ac circuit:

### Example:

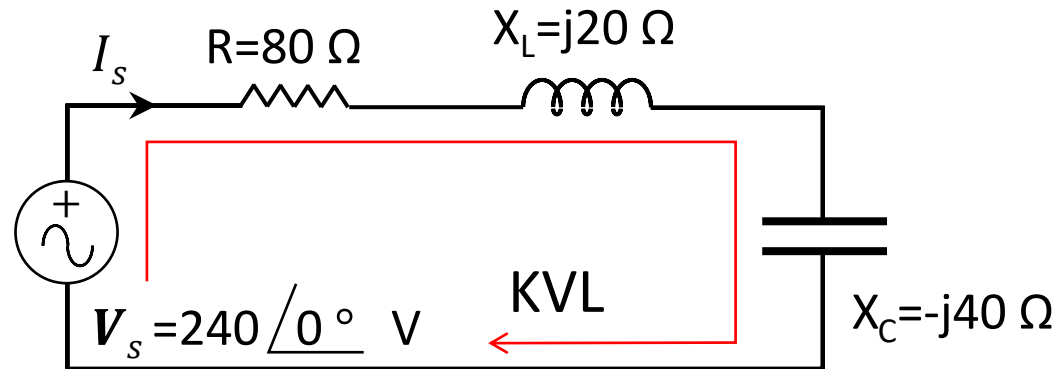

KVL:

$$-V_s + R I_s + j X_L I_s - j X_C I_s = 0$$


$$-240 \angle 0 + 80 I_s + j 20 I_s - j 40 I_s = 0$$

$$I_s = 2.91 \angle 14.03^\circ \text{ A}$$

$$V_R = R I_s = 233.8 \angle 14.03^\circ \text{ V}$$

$$V_{X_L} = j X_L I_s = 58.2 \angle 104.03^\circ \text{ V}$$
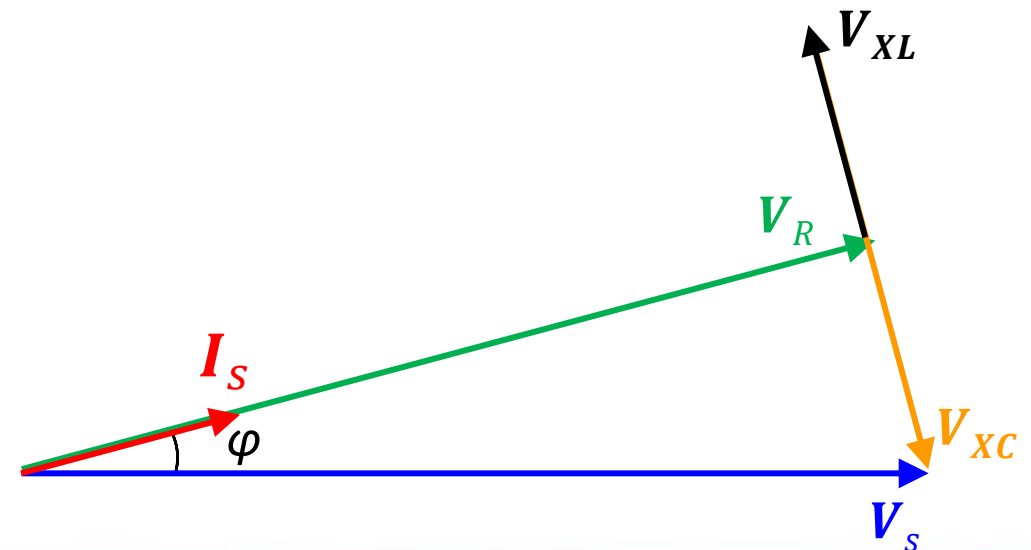
$$V_{X_C} = -j X_C I_s = 116.4 \angle -75.97^\circ \text{ V}$$






### Example:

### Drill:

In the following circuit  $I_x = 5 \angle 35^\circ \text{ A}$ ,  $V_x = 25 \angle 15^\circ \text{ V}$ , and  $I_y = 3 \angle -25^\circ \text{ A}$ .

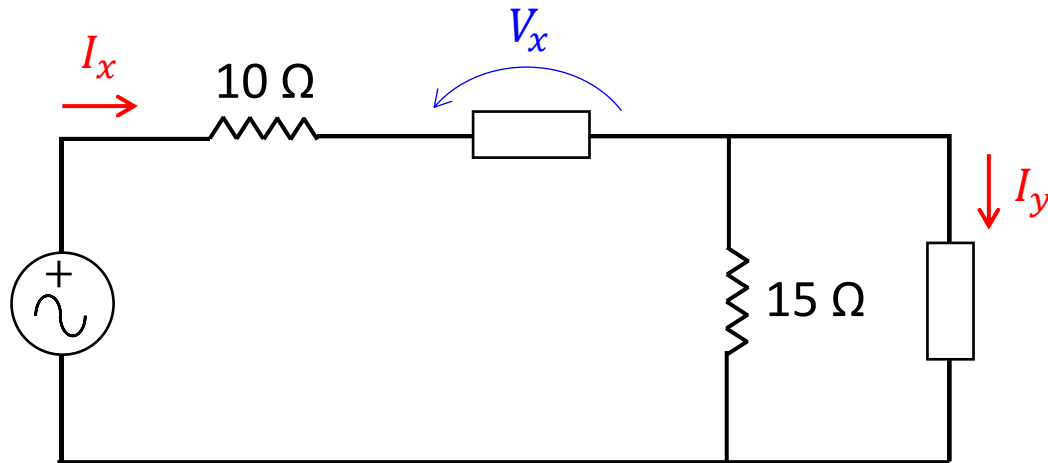- a) Find current of the  $15 \Omega$  resistor
- b) Find phasor of the voltage source  $V_s$ .



Answer:

a)  $I_{15} = 4.35 \angle 71.52^\circ \text{ A}$

b)  $V_s = 129.52 \angle 48.3^\circ \text{ V}$

## Module description:

### Recommended text books:

- DeCarlo Lin, "*Linear Circuit Analysis*", Oxford University Press, Second Edition, 2003
- W H Hayt, J E Kemmerly, S M Durbin, "*Engineering Circuit Analysis*", McGraw-Hill, 9<sup>th</sup> Edition, 2019

