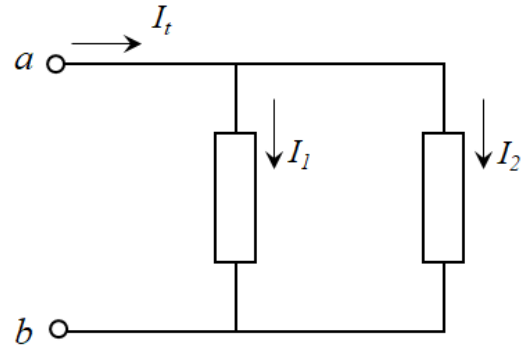


- 1 In the following circuit, currents  $i_1$  and  $i_2$  are given as:

$$i_1(t) = 2.4 \sin(\omega t + 10^\circ) \text{ A}$$

$$i_2(t) = 3.6 \sin(\omega t - 15^\circ) \text{ A}$$

Find the current at the input terminal.



**Solution:**

$$I_1 = 2.4 \angle 10^\circ \quad I_2 = 3.6 \angle -15^\circ$$

A KCL equation at the top node gives:

$$I_T = I_1 + I_2 = 2.4 \angle 10^\circ + 3.6 \angle -15^\circ$$

$$I_T = (2.36 + j0.416) + (3.48 - j0.931) = 5.84 - j0.515$$


$$I_T = 5.86 \angle -5.02^\circ$$

And finally the total current in time domain:

$$i_T(t) = 5.86 \sin(\omega t - 5.02^\circ) \text{ A}$$

- 2 The following circuit is operating at angular frequency of  $\omega=10$  rad/sec.

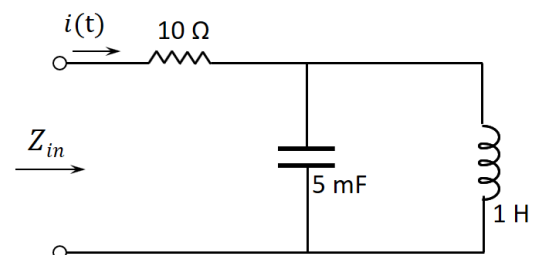Find the input impedance. If the circuit is supplied through a voltage source with *rms* value of 120 V, find phasor of the input current.




**Solution:**

First we need to convert the circuit to phasor domain with the given angular frequency:

$$X_L = j\omega L = j10 \times 1 = j10 \, \Omega$$
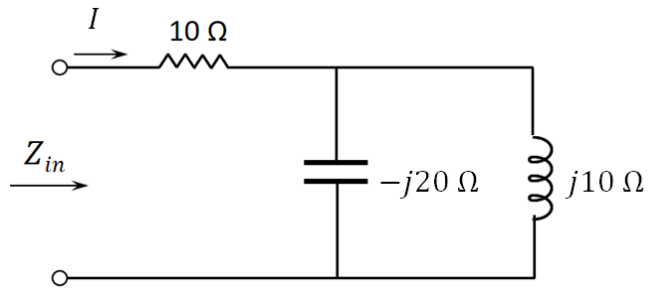
$$X_c = -j \frac{1}{\omega C} = -j \frac{1}{10 \times 5 \times 10^{-3}} = -j20 \, \Omega$$



From this circuit the total input impedance is:

$$Z_{in} = 10 + (-j20 \parallel j10) = 10 + \frac{(-j20 \times j10)}{(-j20 + j10)}$$

$$Z_{in} = 10 + j20 \, \Omega$$

And finally current can be calculated as:

$$I = \frac{120 \angle 0^\circ}{10 + j20} = 5.367 \angle -63.43^\circ \text{ A}$$