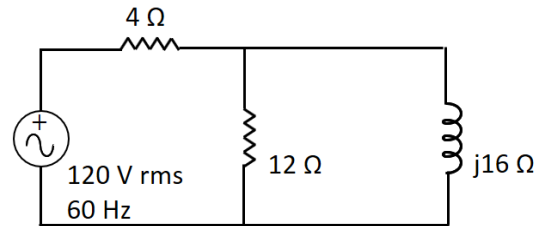


- 1 Consider the following circuit:
- Find phasor of the current of the voltage source
  - Find the complex power of the voltage source



**Solution:**

- To find the current, first we need to find the total impedance of the circuit from the terminal of the voltage source:

$$\mathbf{Z}_t = 4 + (12 \parallel j16) = 4 + \frac{12 \times j16}{12 + j16} = 11.68 + j5.76 \ \Omega$$

And hence the total current is:

$$\mathbf{I}_s = \frac{120 \angle 0^\circ}{11.68 + j5.76} = 9.21 \angle -26.25^\circ \text{ A}$$


- Complex power of the voltage source:

$$\mathbf{S} = \mathbf{V} \mathbf{I}^* = 120 \angle 0^\circ \times 9.21 \angle 26.25^\circ = 1105.2 \angle 26.25^\circ \text{ VA}$$

$$\mathbf{S} = 991.22 + j488.82 \text{ VA}$$

- 2 The following circuit operates at  $\omega=500 \text{ rad/s}$  and *rms* voltage of 100 V.

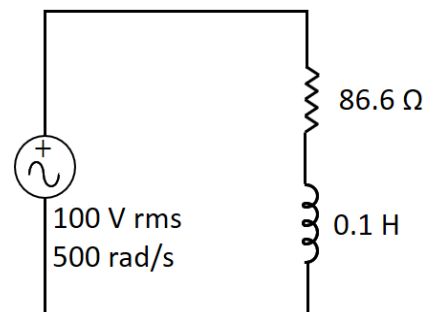
- Find the complex power delivered to this load
- Find the required capacitive reactive power to correct power factor to 0.94 lagging



**Solution:**

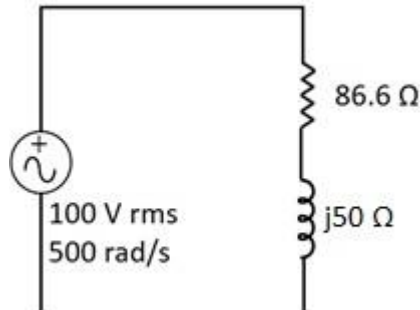a) To analyse this circuit, first we need to transfer it into phasor domain:

$$X_L = j\omega L = j500 \times 0.1 = j50 \Omega$$



And total current of the circuit is:

$$I_s = \frac{100 \angle 0^\circ}{86.6 + j50} = 1.0 \angle -30^\circ \text{ A}$$

Therefore, complex power of the source is:

$$S = V I^* = 100 \angle 0^\circ \times 1.0 \angle 30^\circ = 100 \angle 30^\circ \text{ VA}$$

$$S = 86.6 + j50 \text{ VA}$$

b) Capacitive reactive power is calculated by:

$$Q_c = P_L (\tan \varphi_1 - \tan \varphi_2)$$

The initial phase angle is  $\varphi_1 = 30^\circ$  and phase angle after compensation is  $\varphi_2 = \cos^{-1}(0.94) = 19.95^\circ$ .  
And hence:

$$Q_c = 86.6(\tan 30^\circ - \tan 19.95^\circ) = 18.53 \text{ VA}$$