

# Electrical Engineering 2

**ENGI2191**

**Three phase systems**

**Dr Hamed Bahmani**  
**Hamed.h.bahmani@Durham.ac.uk**  
**E108**



## Lecture Objectives:

### Aim of this lecture:


The aim of this lecture is to understand the basic concepts of three-phase systems in electrical networks and power systems.

### Intended Learning Outcomes:


**At the completion of the lecture and associated problems you should be able to:**

- Discuss the differences between single-phase and three-phase systems.
- Discuss the characteristics of Y and  $\Delta$  connections.
- Calculate voltage and current values for both Y and  $\Delta$  connections.
- Analyse the balanced three phase circuits.
- Calculate complex power in three phase systems.


## Single phase voltage source:

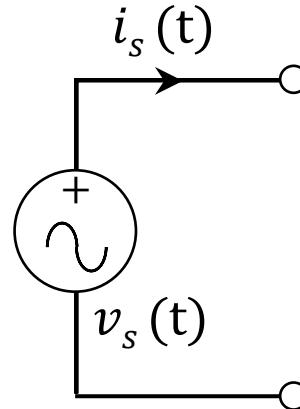

$$v(t) = V_m \sin(\omega t + \varphi)$$

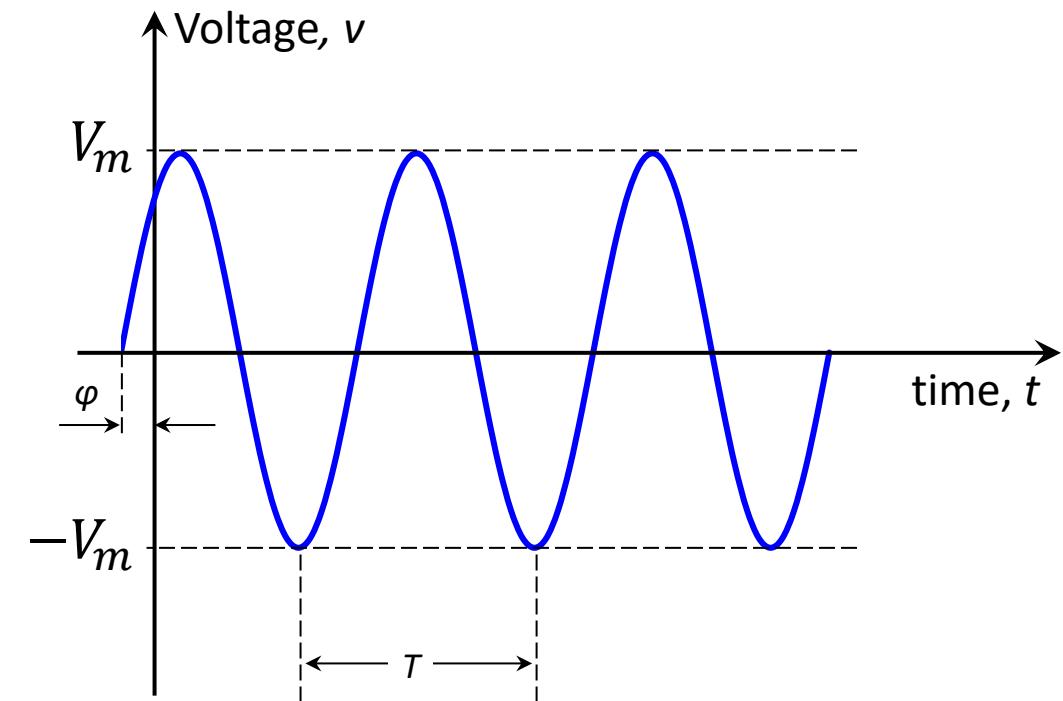


$$V = V_m < \varphi^\circ$$

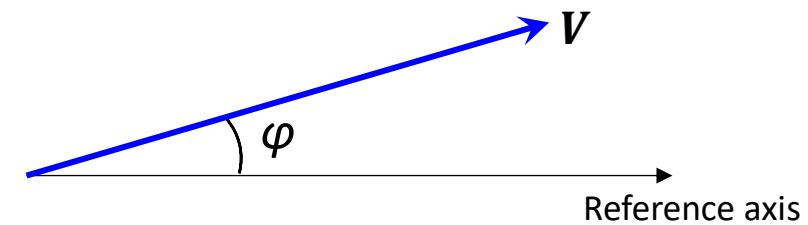



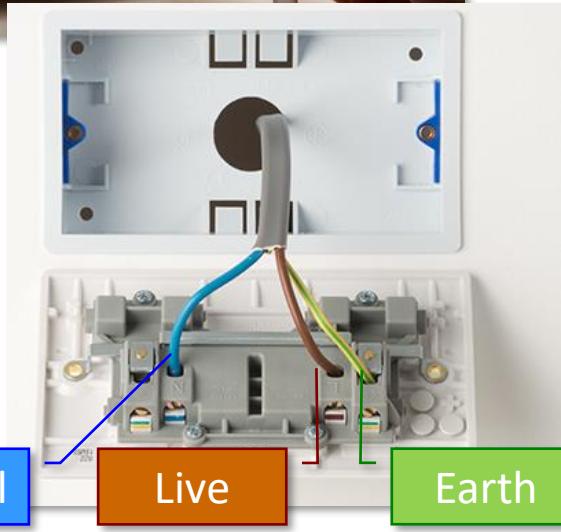
## ► Single phase voltage source:

Households and non-industrial small businesses  
use single phase power.



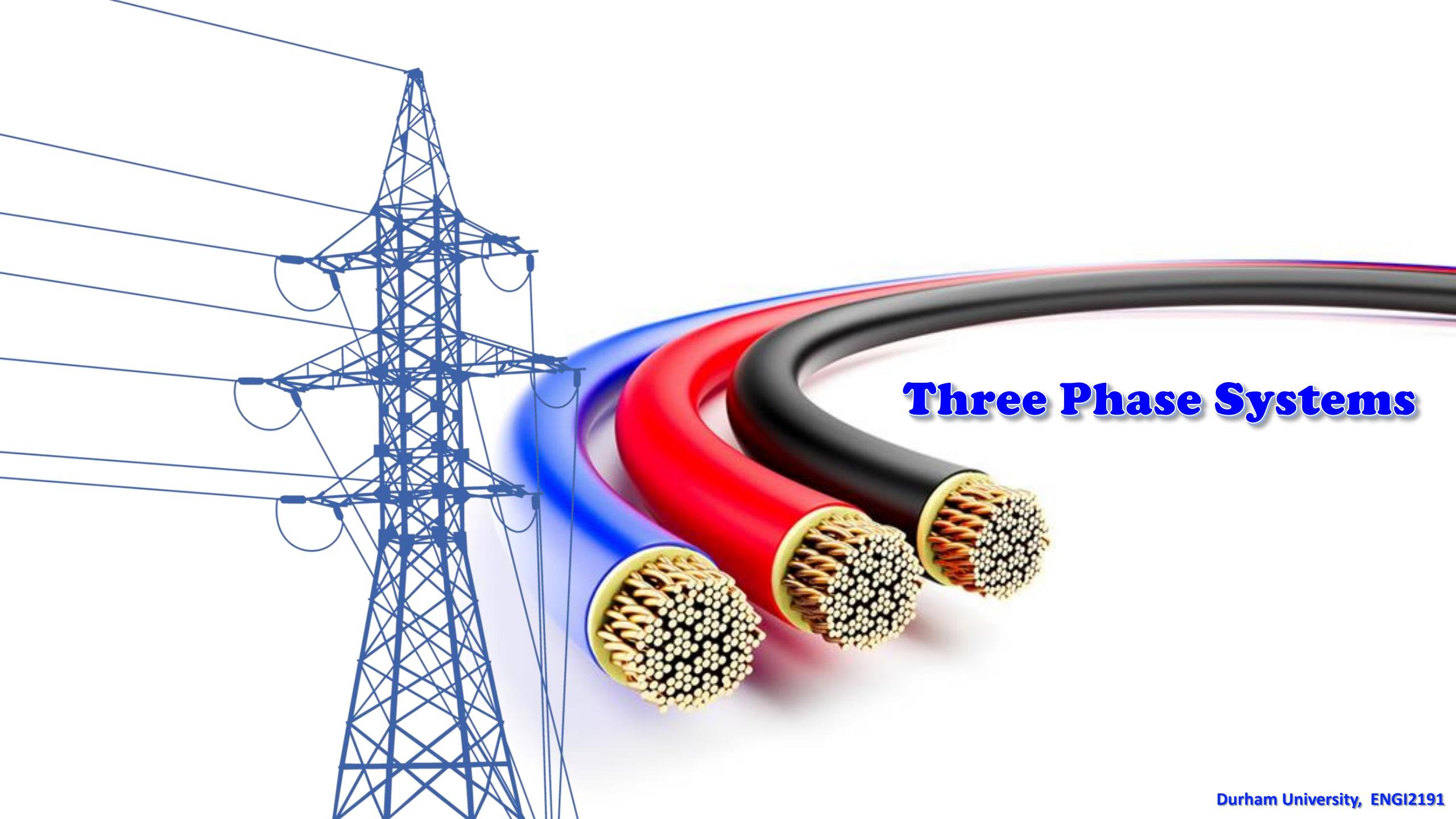


## Three Phase Systems



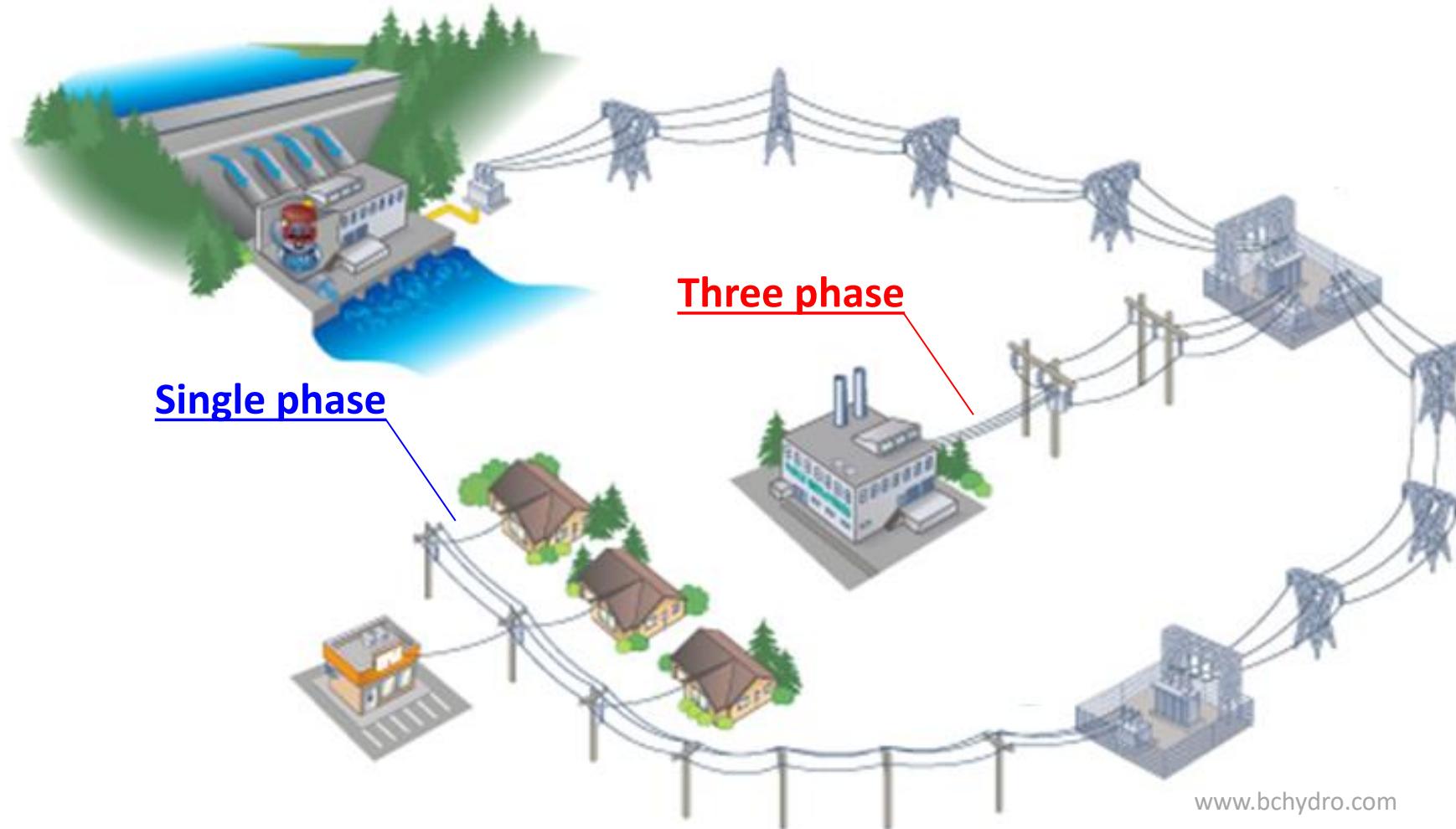
## ► Three phase voltage source:

Electrical energy is generated, transferred and distributed in three phase system.





## Three phase generators:

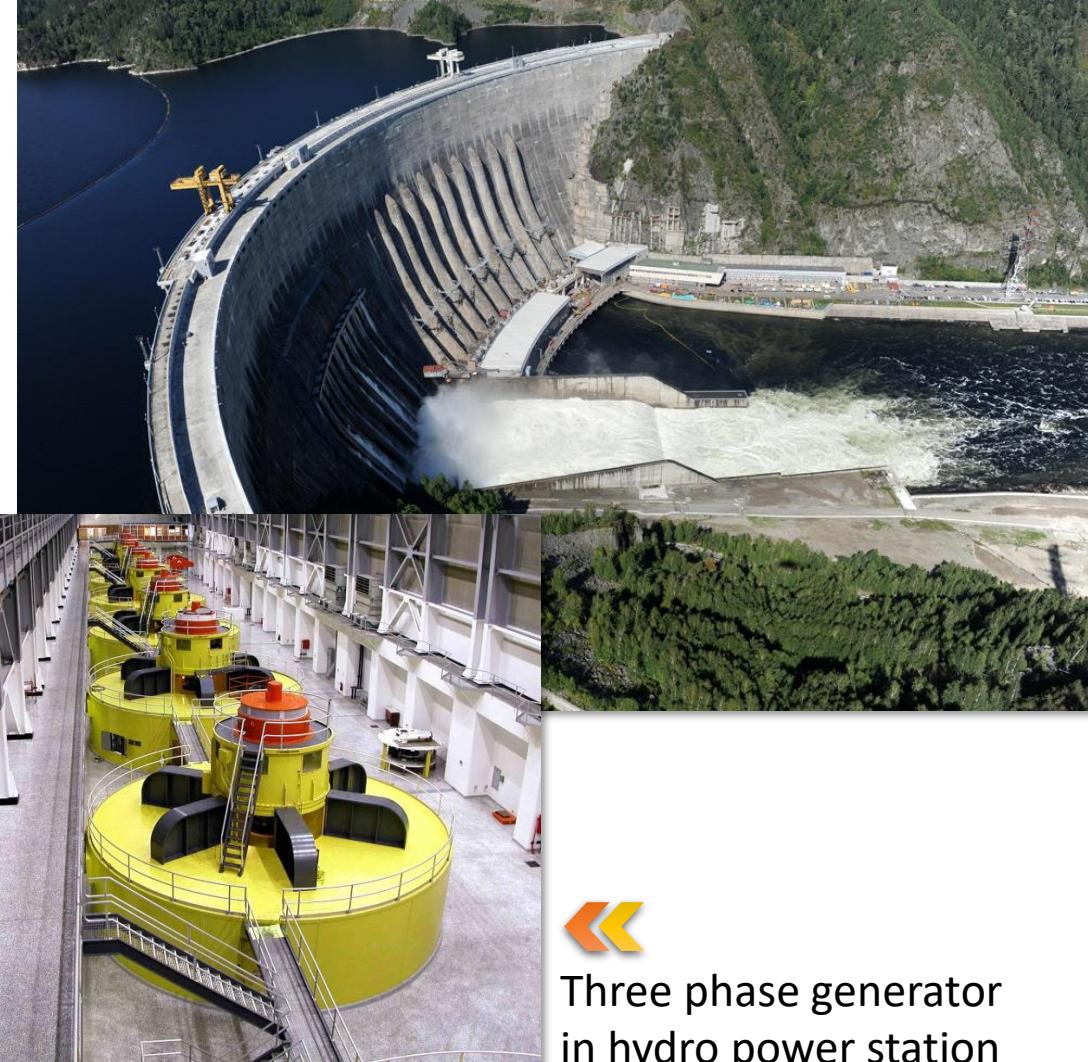

Three phase generator  
in hydro power station



Three phase generator  
in wind turbine



## ▶ Three phase transmission lines:



400 kV power line  
Cheshire



132 kV power line  
Western Power Distribution



11 kV distribution system




## ► Three phase loads:

Three phase induction motors are one of the most popular electrical machines in industrial drives.




Akronbearing.com

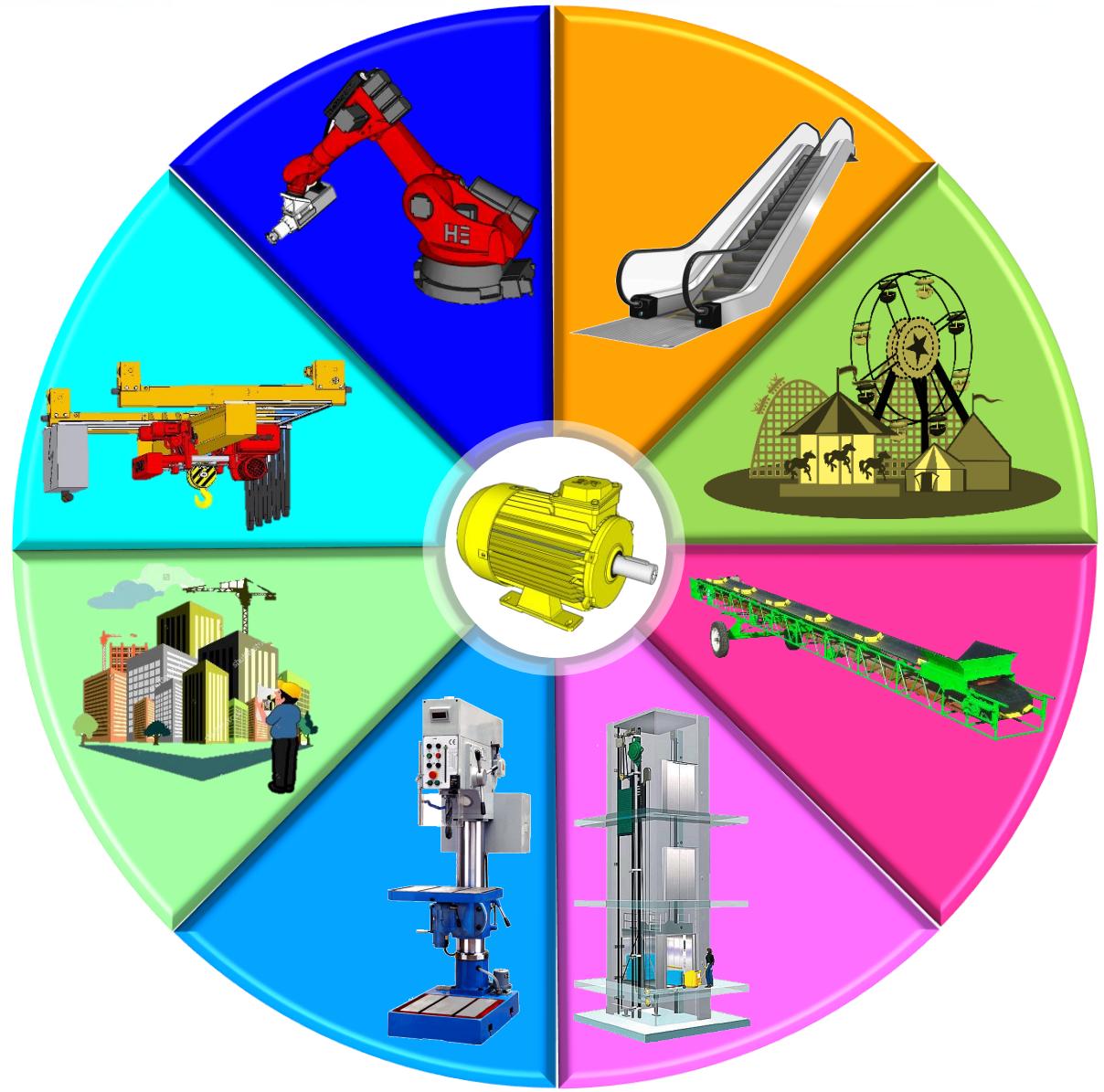




## Three phase loads:

### Single-phase plug and socket

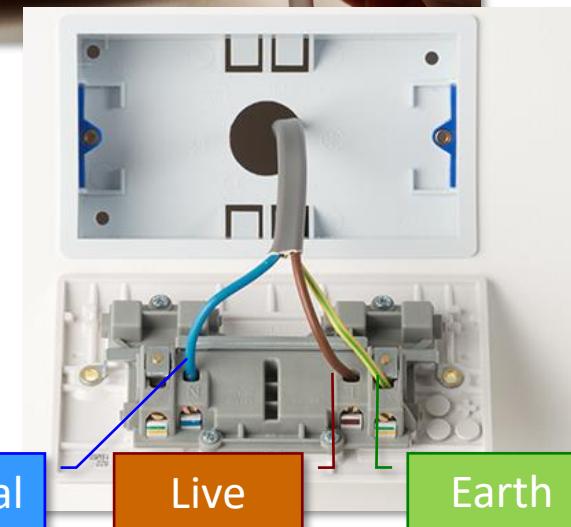




### Three-phase plug and socket

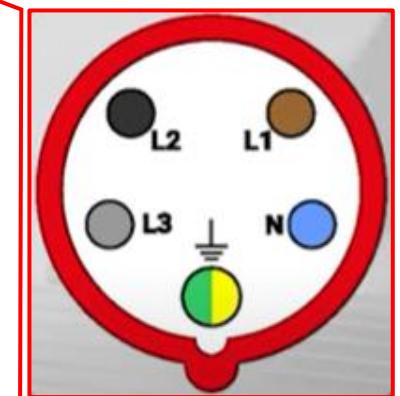


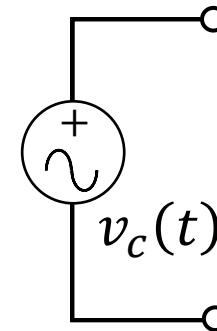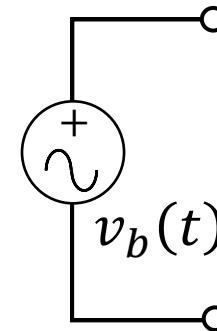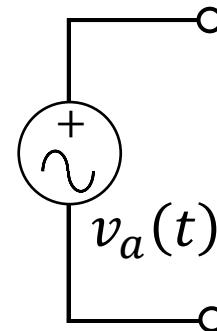
## ► Three phase voltage source:

A three-phase voltage source consists of three independent single phase sinusoidal voltage sources with the same frequency and amplitude, but with phase angles separated by  $120^\circ$ .



$$v_a(t) = V_m \sin(\omega t)$$

$$v_b(t) = V_m \sin(\omega t - 120^\circ)$$

$$v_c(t) = V_m \sin(\omega t + 120^\circ)$$


$$V_a = V_{rms} < 0^\circ$$

$$V_b = V_{rms} < -120^\circ$$

$$V_c = V_{rms} < 120^\circ$$



## Three phase systems:

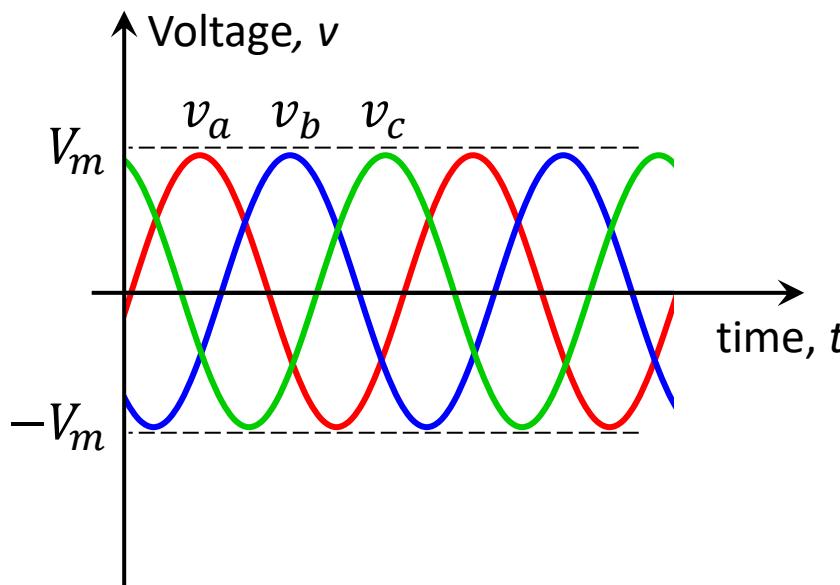

$$v_a(t) = V_m \sin(\omega t)$$


$$v_b(t) = V_m \sin(\omega t - 120^\circ)$$

$$v_c(t) = V_m \sin(\omega t + 120^\circ)$$

$$V_a = V_{rms} < 0^\circ$$

$$V_b = V_{rms} < -120^\circ$$


$$V_c = V_{rms} < 120^\circ$$

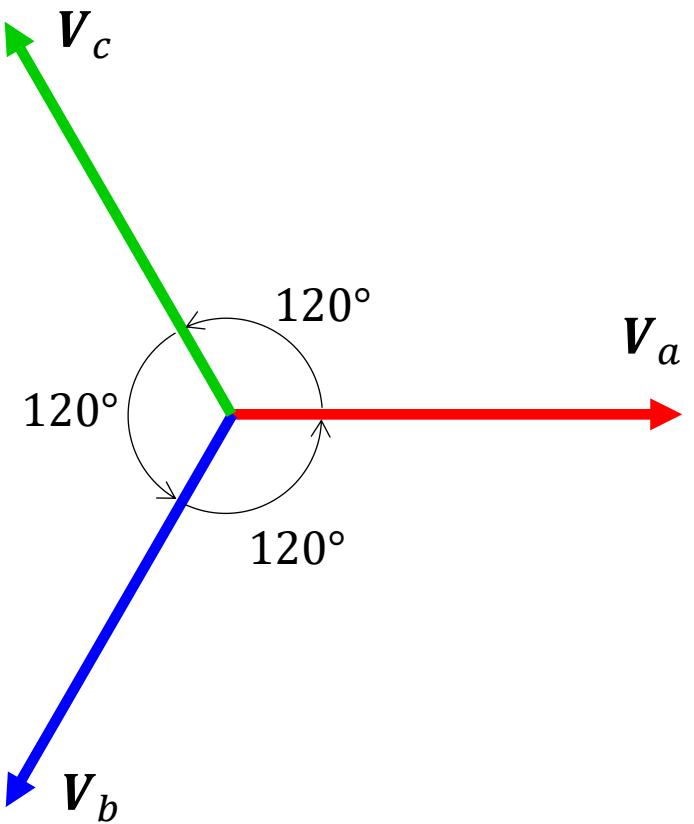


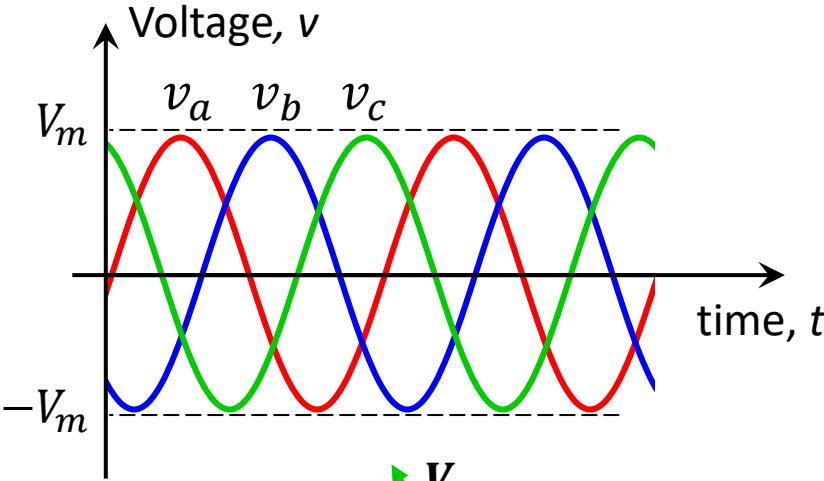
## Three phase systems:

Based on the rotating direction of the three-phase generator, two phase sequences are defined:



Positive sequence (*abc*):

$v_b(t)$  lags  $v_a(t)$  by  $120^\circ$

120°


120°

120°

$V_a$

$V_b$

$V_c$

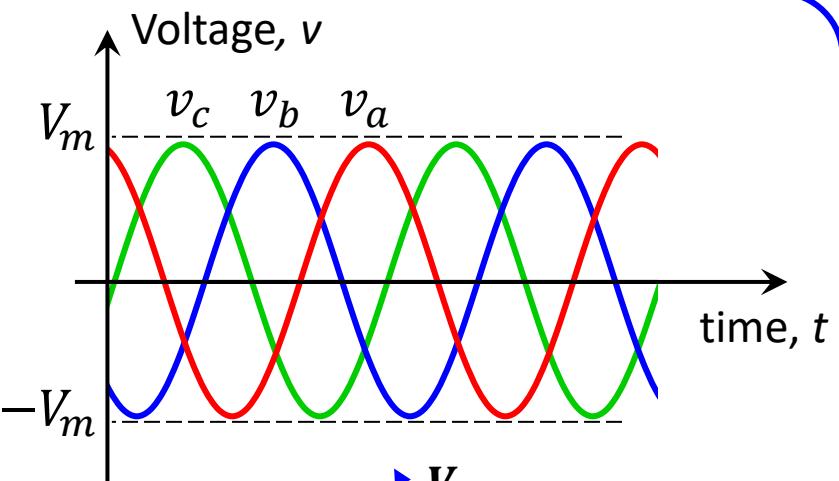

Negative sequence (*cba*):

$v_b(t)$  leads  $v_a(t)$  by  $120^\circ$

120°

120°

120°

$V_a$

$V_b$

$V_c$


➤➤➤ In both systems,  $V_a$  is considered as the reference voltage. ⇚




## Three phase systems:
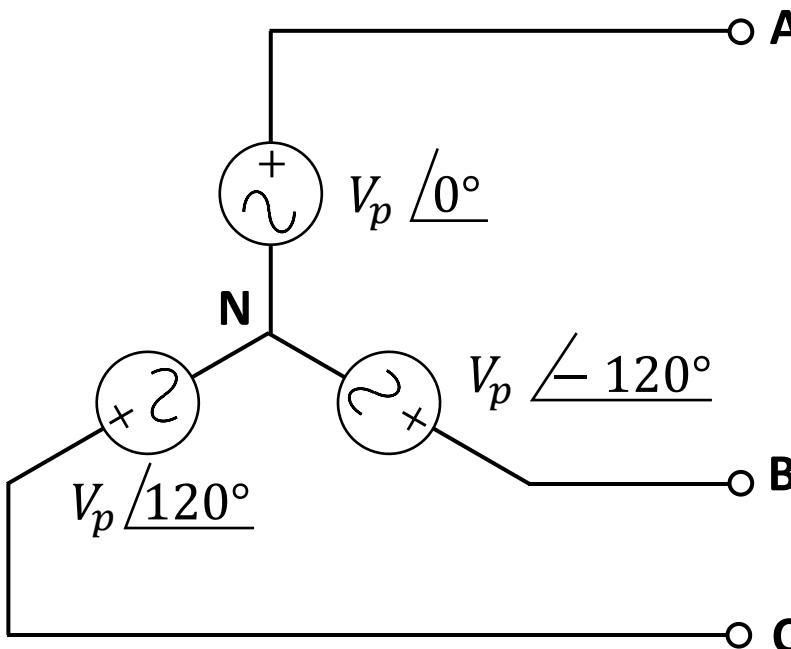
### Three phase voltage source:

There are two common connections in three phase systems



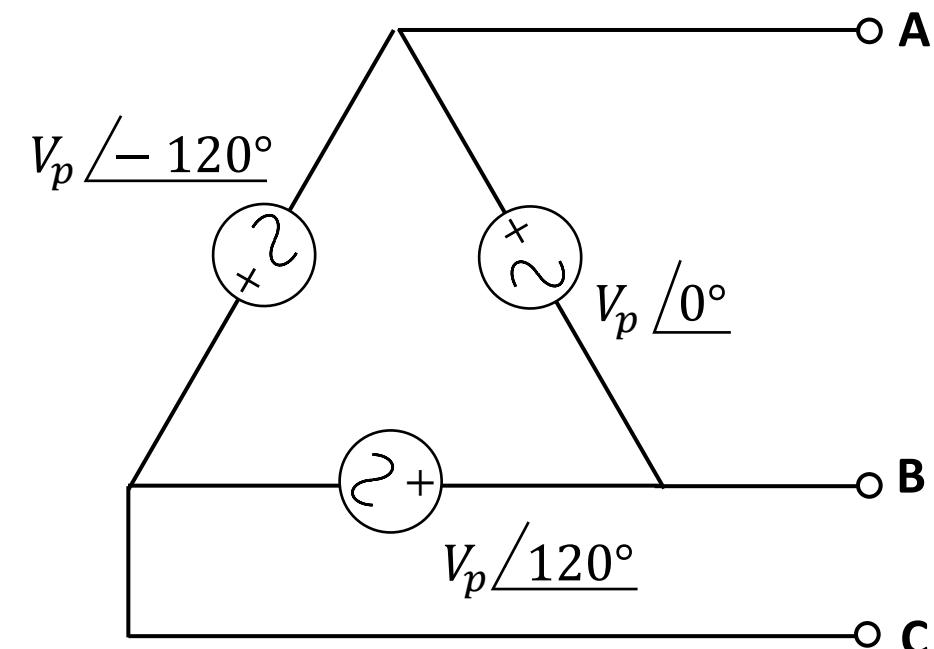Y, Wye or star connected three-phase  
voltage source



$\Delta$  connected three-phase  
voltage source



$V_p$  is called phase voltage, is voltage across each single-phase voltage source.



## Three phase systems:
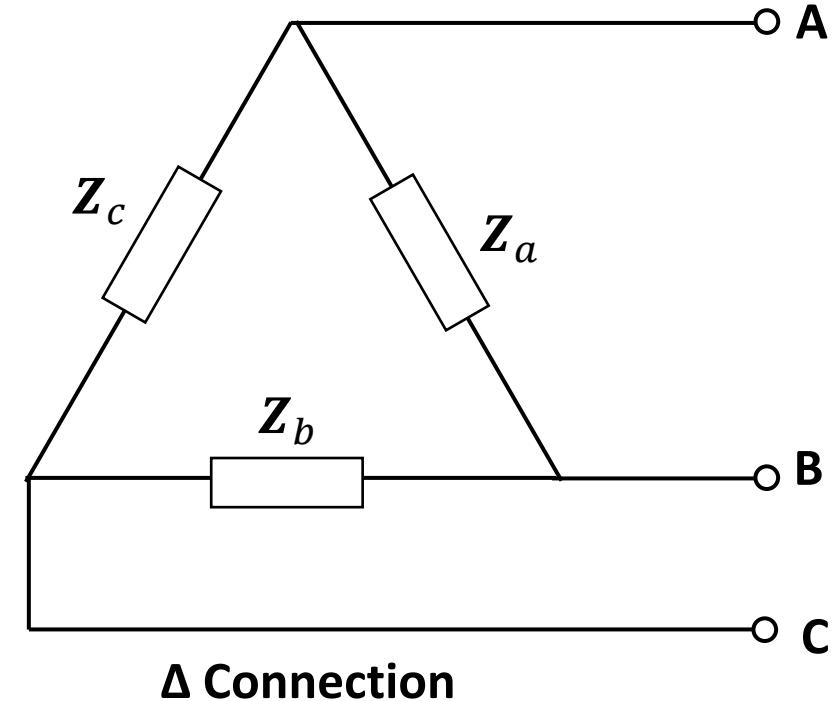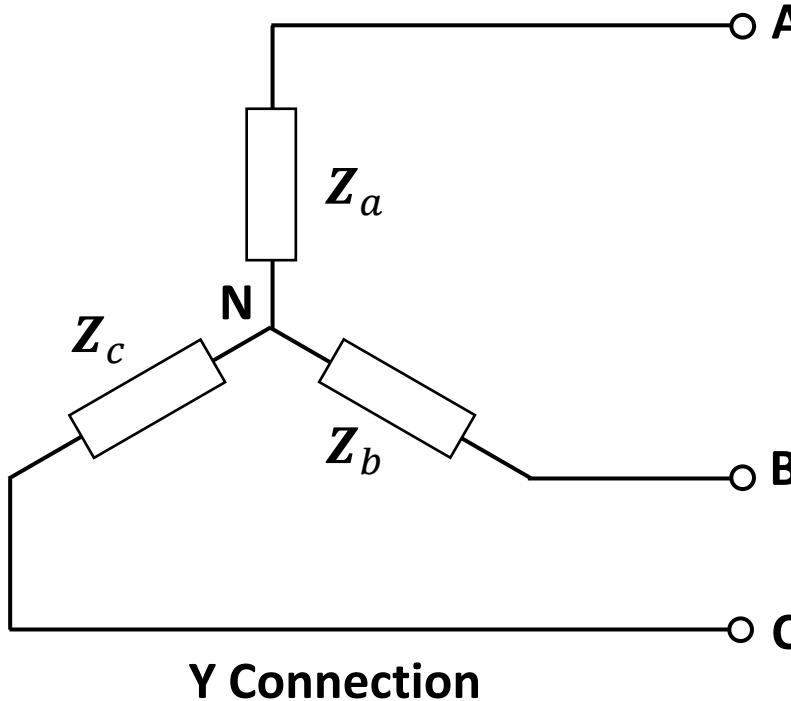
### Three phase loads:

Three phase load impedance are also connected either Y or  $\Delta$  connection.





In a balance three phase load:  $Z_a = Z_b = Z_c$

Any circuit that does not have all loads with the same impedance in all three phases, is unbalanced load.



## Three phase systems:

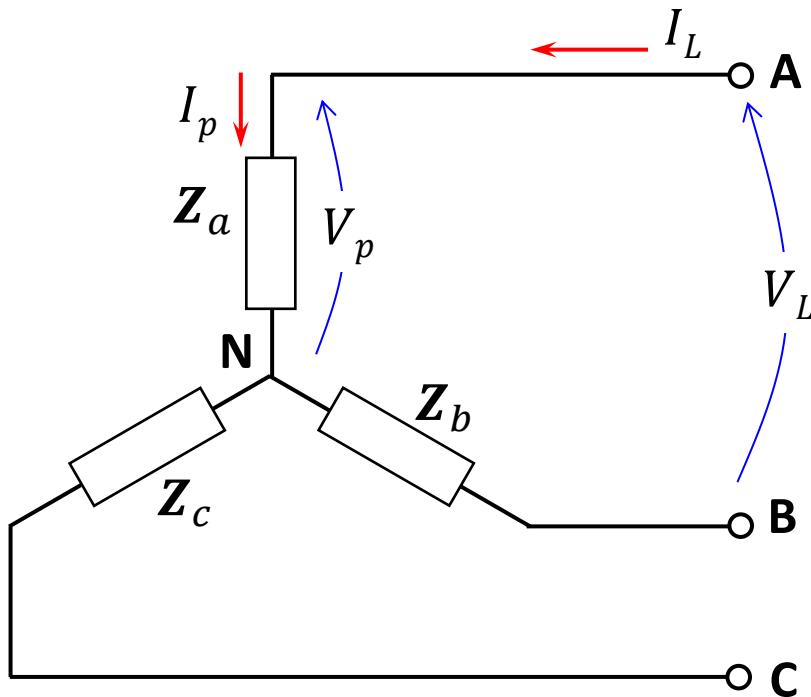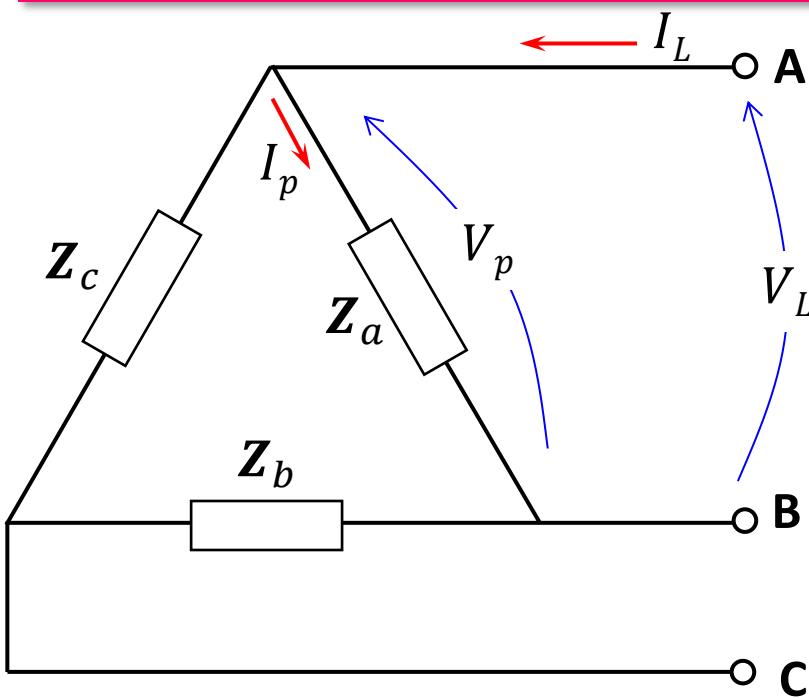

In three phase loads:

**Phase voltage,  $V_p$ :**

Voltage across each impedance.

**Phase current,  $I_p$ :**

Current flowing through each impedance.

**Line voltage,  $V_L$ :**

Voltage between any pair of lines or terminals.


**Line current,  $I_L$ :**

Current flowing through each line.





## Three phase systems:

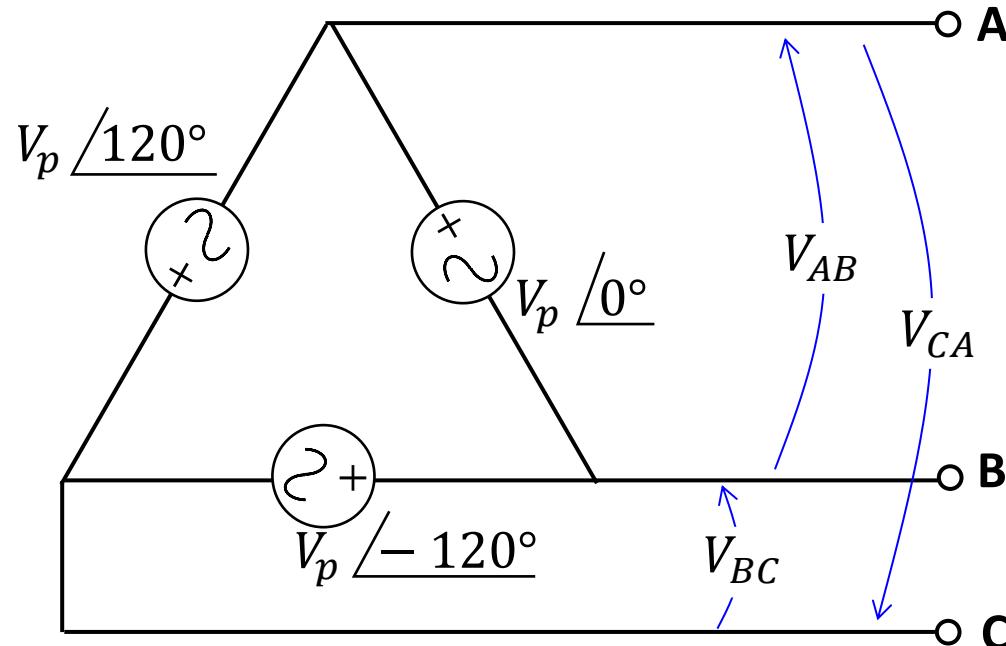

$$\left\{ \begin{array}{l} V_{AB} = V_p \angle 0^\circ \\ V_{BC} = V_p \angle -120^\circ \\ V_{CA} = V_p \angle 120^\circ \end{array} \right.$$



In three phase voltage sources:

**Phase voltage,  $V_p$ :**

Voltage across each source.

**Line voltage,  $V_L$ :**

Voltage between any pair of lines or terminals.



In three phase Δ-connected systems:

In  $\Delta$  connection:

$$V_L = V_p$$



## Three phase systems:

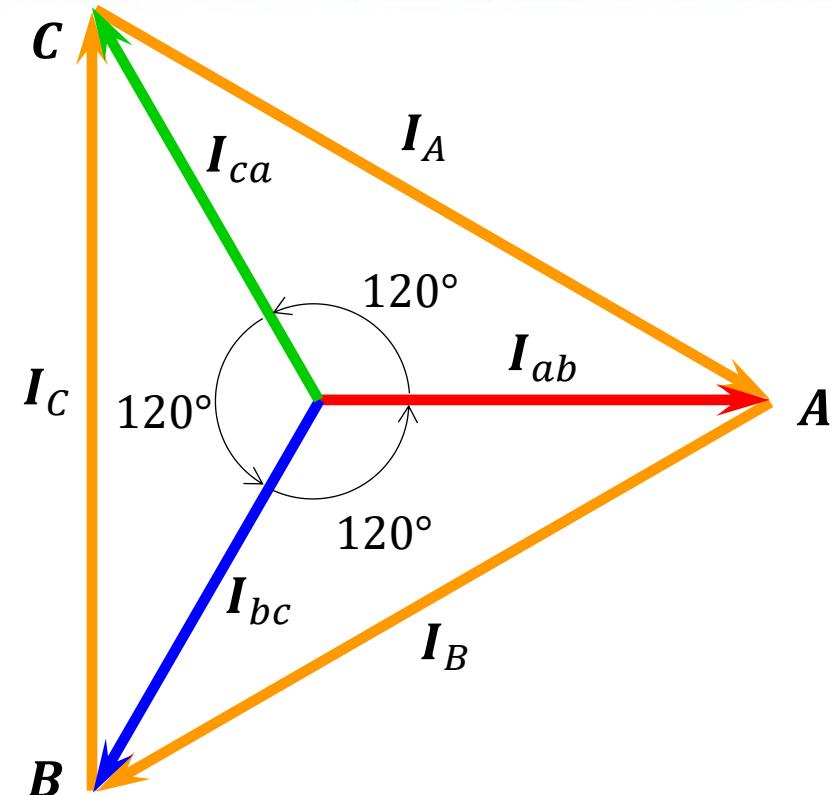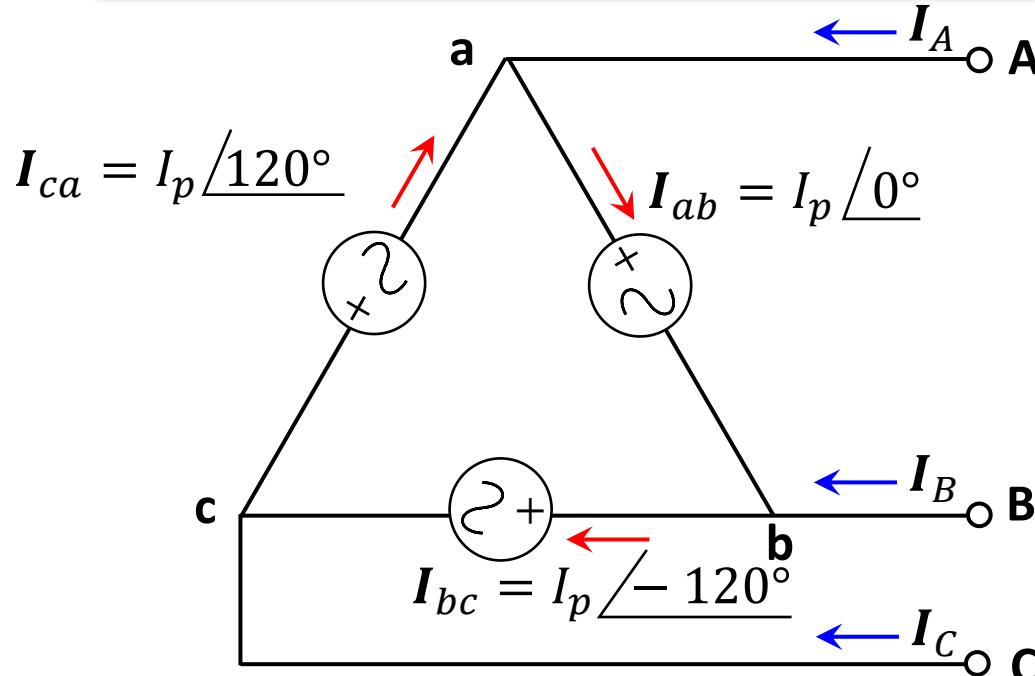

From KCL the relation between the phase and line currents can be obtained:

$$I_A = I_{ab} - I_{ca} = I_p / 0^\circ - I_p / 120^\circ = \sqrt{3} I_p / -30^\circ$$

$$I_B = I_{bc} - I_{ab} = I_p / -120^\circ - I_p / 0^\circ = \sqrt{3} I_p / 210^\circ$$

$$I_C = I_{ca} - I_{bc} = I_p / 120^\circ - I_p / -120^\circ = \sqrt{3} I_p / 90^\circ$$


In  $\Delta$  connection:

$$I_L = \sqrt{3} I_p$$





## Three phase systems:

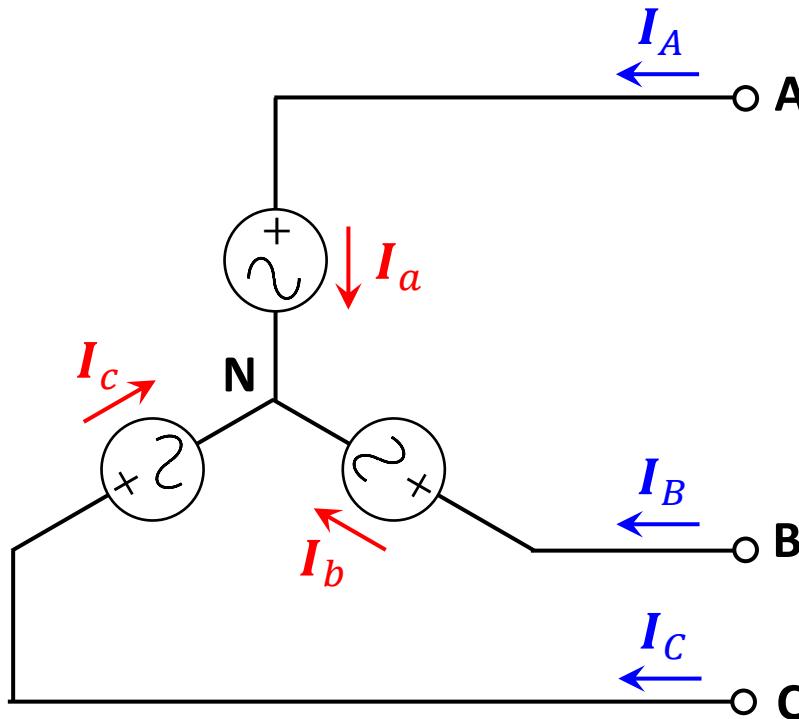

$$\left\{ \begin{array}{l} I_A = I_a \\ I_B = I_b \\ I_C = I_c \end{array} \right.$$



$I_a$ ,  $I_b$  and  $I_c$  are phase currents.



$I_A$ ,  $I_B$  and  $I_C$  are line currents.

In Y connection:

$$I_L = I_p$$



## Three phase systems:

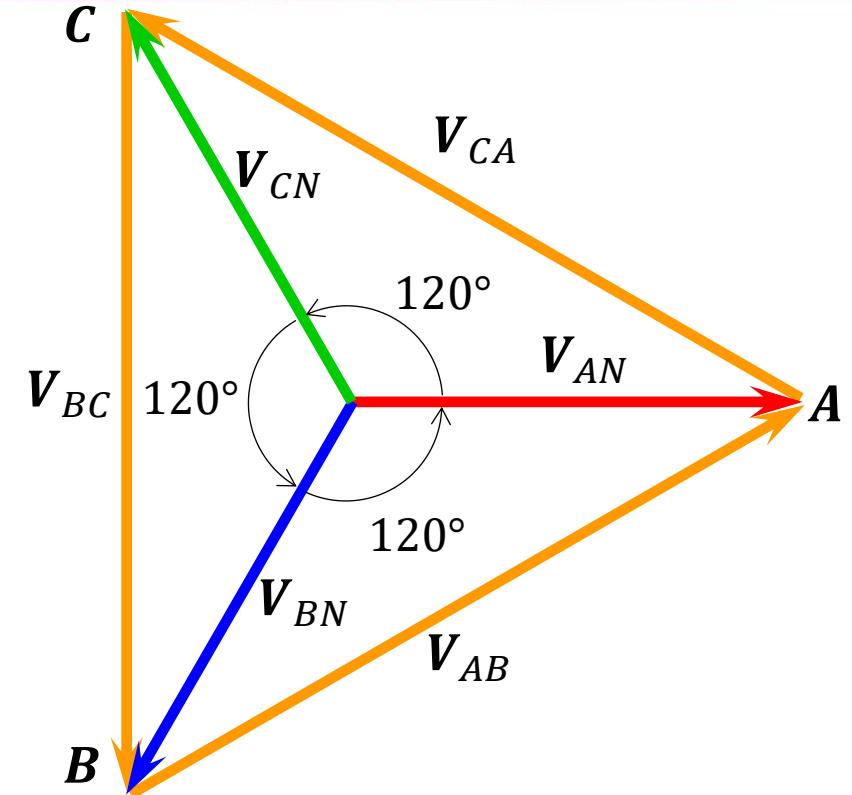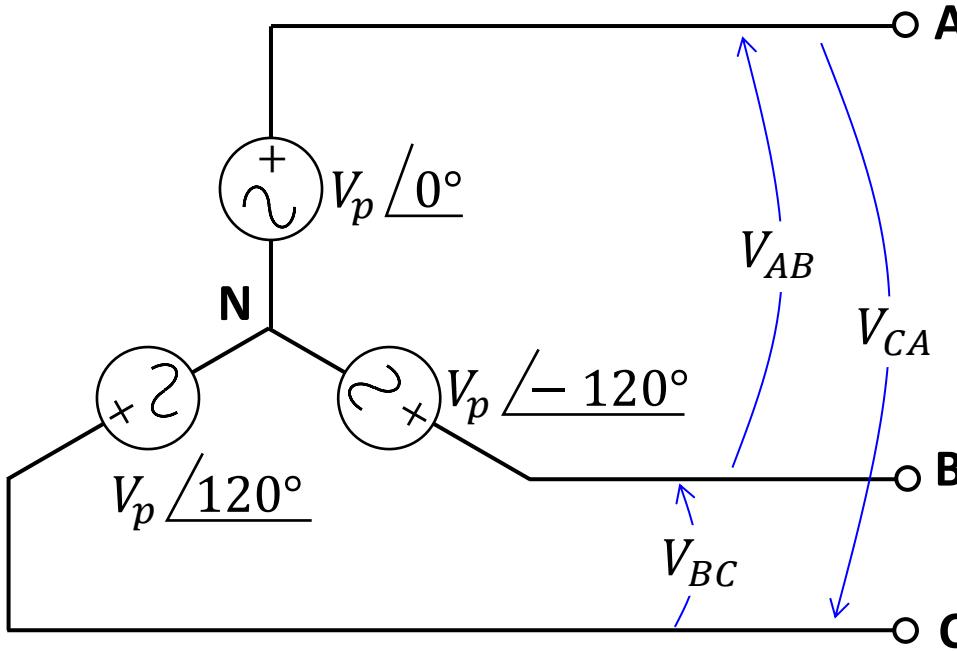

From KVL the relation between the phase and line voltages can be obtained:

$$V_{AB} = V_{AN} - V_{BN} = V_p \angle 0^\circ - V_p \angle -120^\circ = \sqrt{3} V_p \angle 30^\circ$$

$$V_{BC} = V_{BN} - V_{CN} = V_p \angle -120^\circ - V_p \angle 120^\circ = \sqrt{3} V_p \angle -90^\circ$$

$$V_{CA} = V_{CN} - V_{AN} = V_p \angle 120^\circ - V_p \angle 0^\circ = \sqrt{3} V_p \angle 150^\circ$$

In Y connection:


$$V_L = \sqrt{3} V_p$$




## ▶ Three phase systems:

Three phase Y-connected voltage sources are available in two configurations:

Three-wires circuit

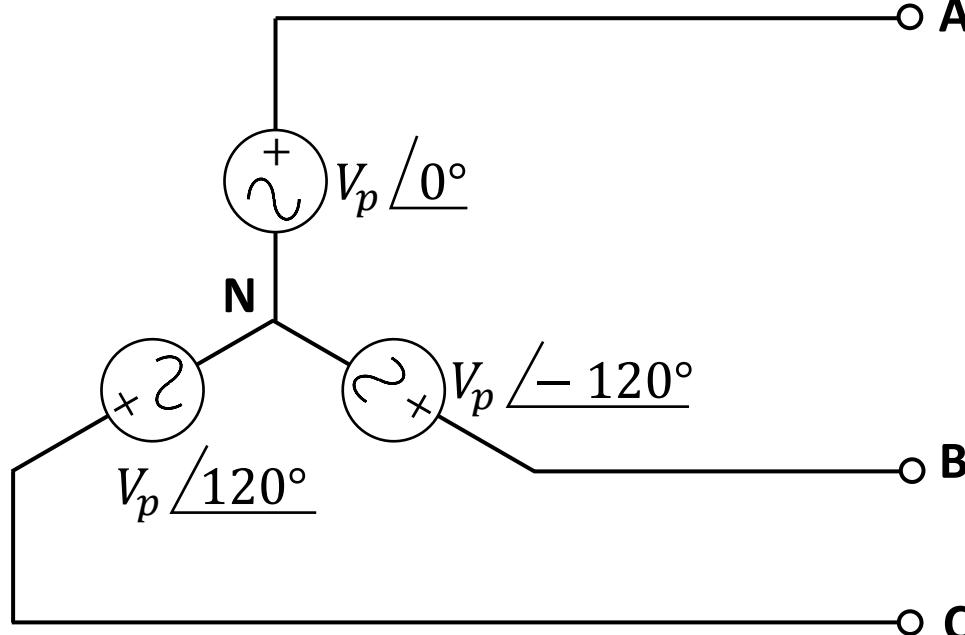

Four-wires circuit


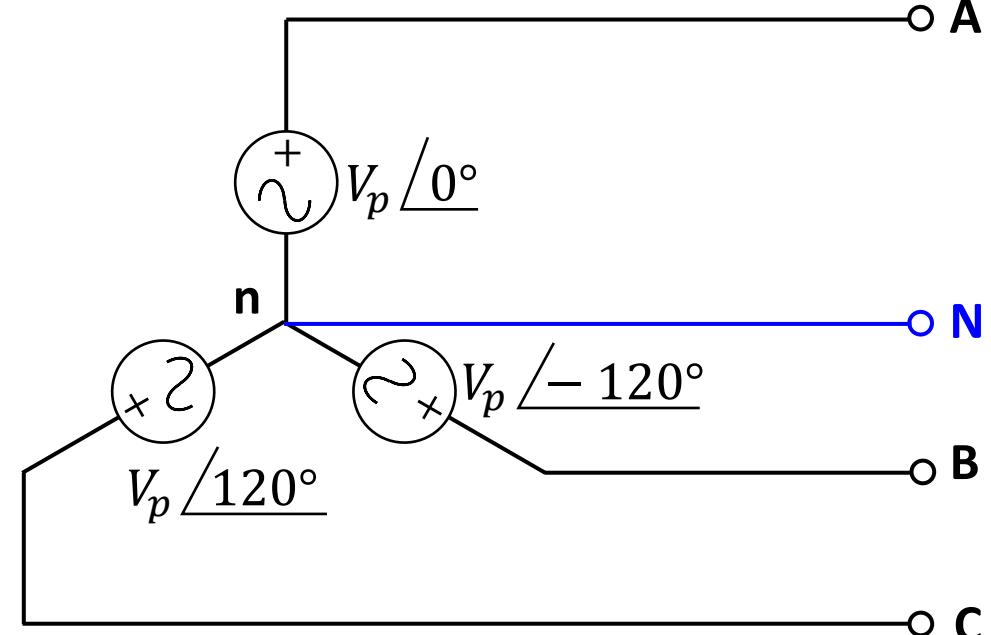


A four-wire system with symmetrical voltages between phase and neutral is obtained when the neutral is connected to the "common star point" of all supply windings. The neutral point is normally grounded for protection purposes.


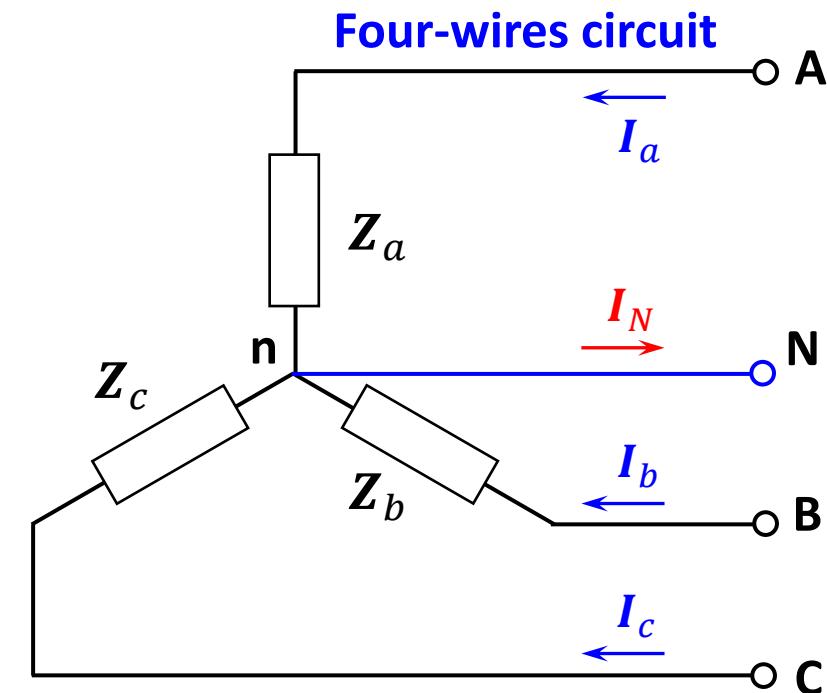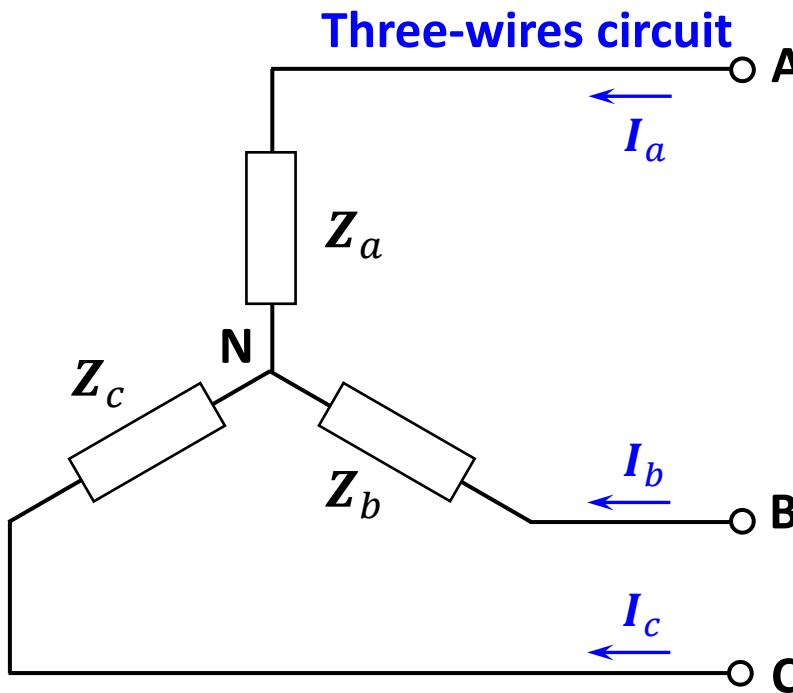
## ▶ Three phase systems:

Similarly, three phase Y-connected loads are available in two configurations:




In a balance three phase load:  $I_N = 0$

In unbalanced loads, it is necessary to use a four-wire system to maintain a balance voltage across the load impedance.



## Three phase systems:

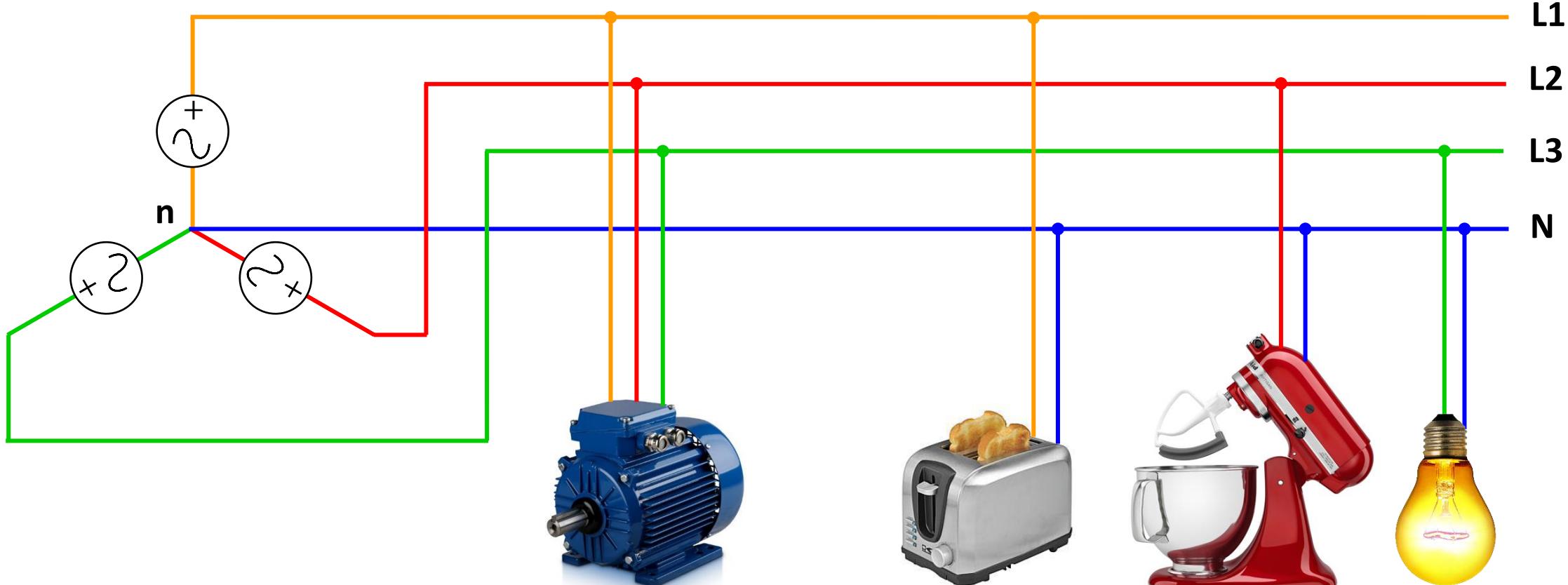

3-phase Y-connected  
4-wires power supply

Three phase motor  
Industrial load

Single phase facilities  
Household consumption



## ► Three phase systems:

Since the load distribution in the distribution networks is practically unbalanced, all of the distribution networks employ four wire system.



4 wires distribution system



5 wires distribution system

In distribution network of the UK, phase voltage is  $V_p = 230 V$ , line voltage is  $V_L = 400 V$  and  $f = 50 Hz$



# Power in Three-Phase Systems

Engineering & Technology



## Power in three phase systems:

Total power in three phase system is the sum of powers in the three phases.


$$P_t = 3 V_p I_p \cos \varphi$$

In 3-phase systems it is more convenient to use line voltage and line current. For  $\Delta$ -connection:

$$V_L = V_p \quad \& \quad I_L = \sqrt{3} I_p$$

Power in  $\Delta$  connected three-phase balance system
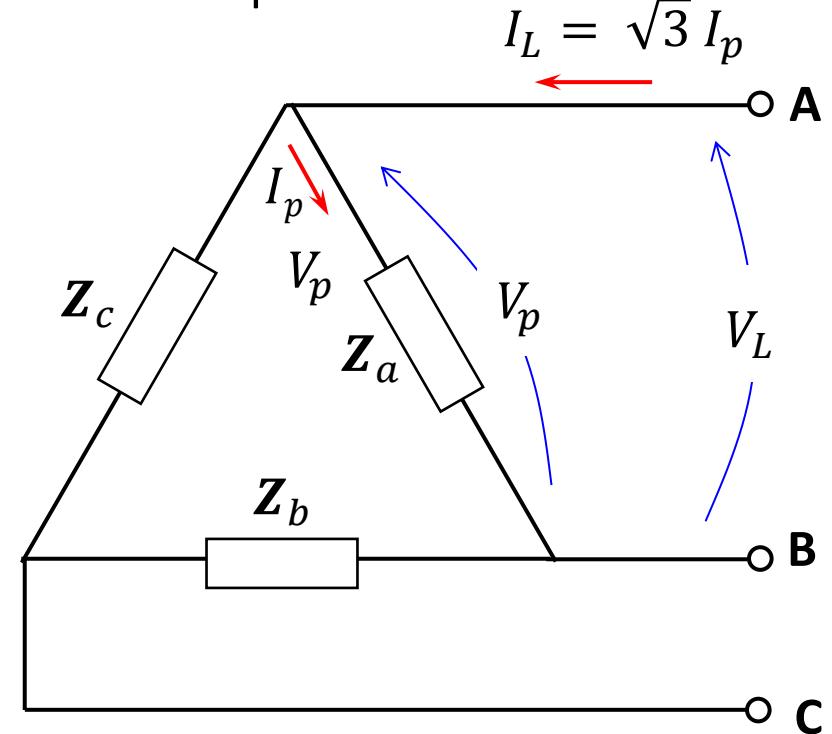
$$P_t = 3 V_L \left( \frac{I_L}{\sqrt{3}} \right) \cos \varphi \quad \Rightarrow \quad P_t = \sqrt{3} V_L I_L \cos \varphi$$





## Power in three phase systems:

Similarly, in a Y-connected three phase system total power is given as:


$$P_t = 3 V_p I_p \cos \varphi$$

In Y connection:

$$V_L = \sqrt{3} V_p \quad \& \quad I_L = I_p$$

Power in Y-connected three-phase balance system
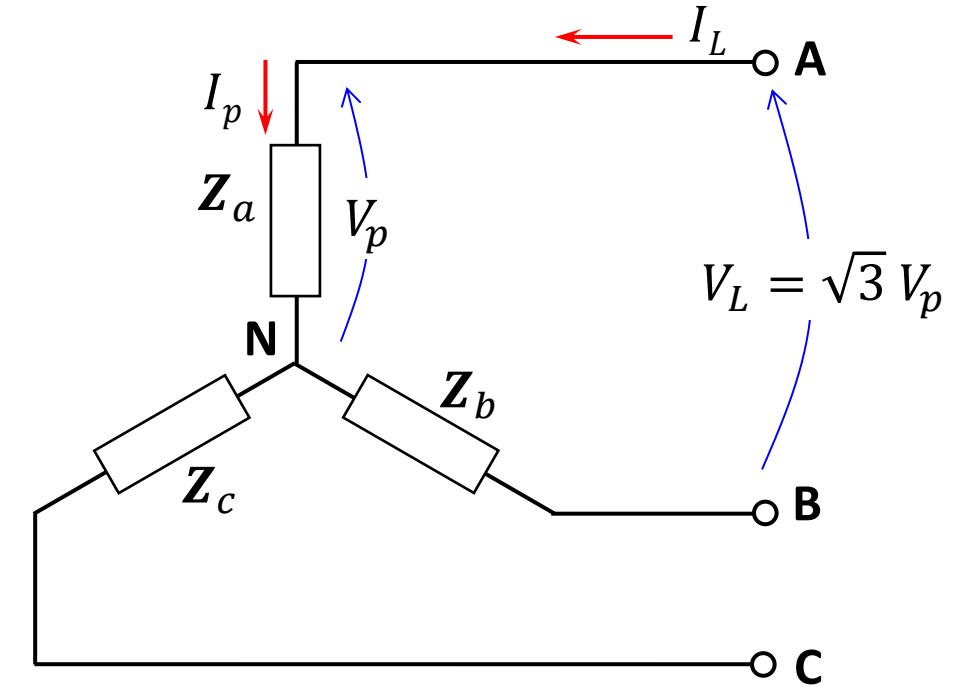
$$P_t = 3 \left( \frac{V_L}{\sqrt{3}} \right) I_L \cos \varphi$$



$$P_t = \sqrt{3} V_L I_L \cos \varphi$$



## ▶ Power in three phase systems:


Similar principle is applied to other components of power:

$$P_t = \sqrt{3} V_L I_L \cos \varphi \quad W, kW \text{ or } MW$$

$$Q_t = \sqrt{3} V_L I_L \sin \varphi \quad VAR, kVAR \text{ or } MVAR$$


$$S_t = \sqrt{3} V_L I_L \quad VA, kVA \text{ or } MVA$$
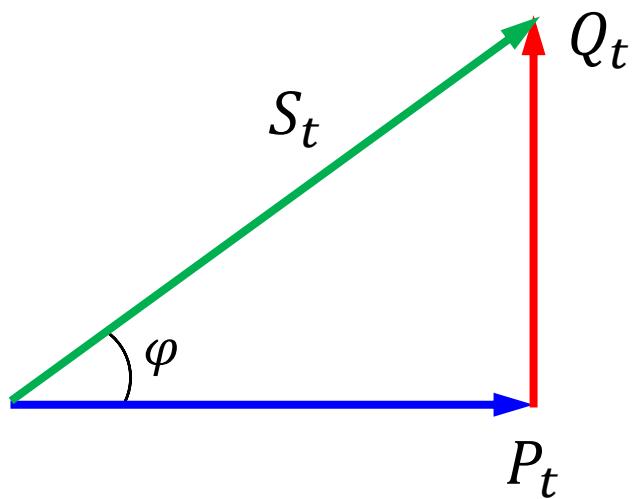
$$S_t = P_t + j Q_t \quad VA, kVA \text{ or } MVA$$





## Three phase systems:

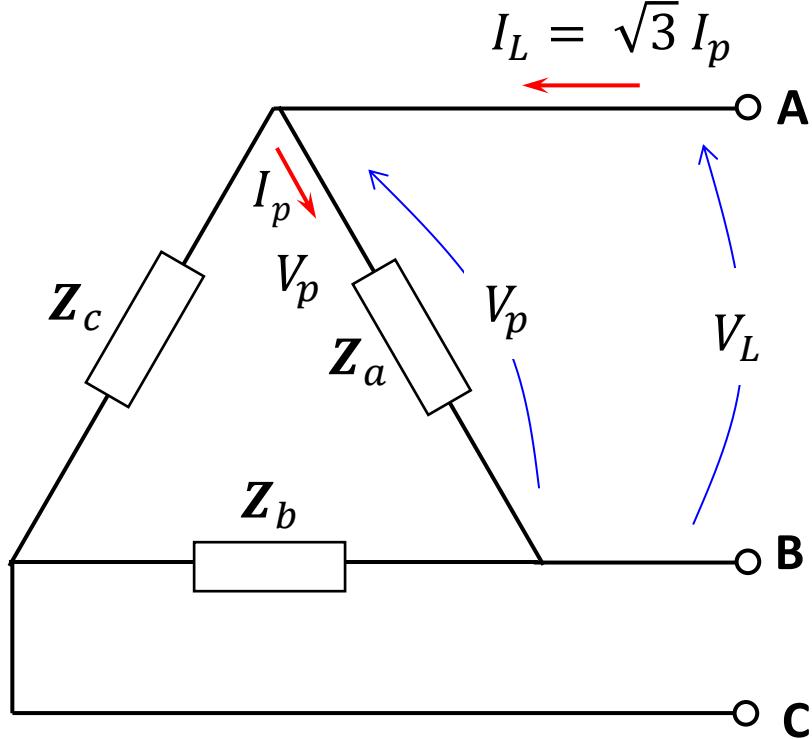


$$V_L = V_p$$

$$I_L = \sqrt{3} I_p$$

$$P_t = \sqrt{3} V_L I_L \cos \varphi$$

Only 3-wires system is possible

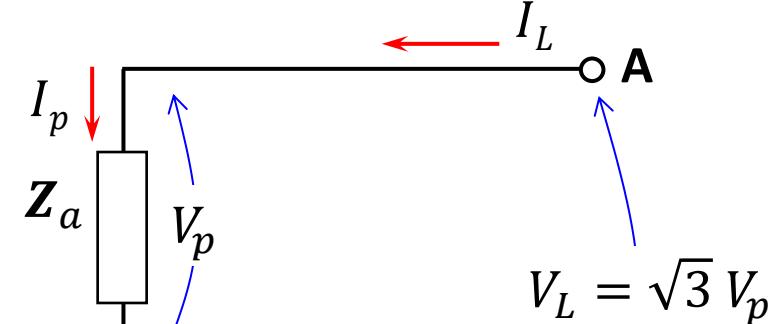

$$V_L = \sqrt{3} V_p$$

$$I_L = I_p$$

$$P_t = \sqrt{3} V_L I_L \cos \varphi$$

3-wires and 4-wires systems are possible




## ► Three phase systems:

### Example:

Consider a Y-connected three-phase balance load with phase impedance of  $Z_p = (4 + j3) \Omega$ .

This load is supplied through a 3-phase 4-wires power supply with line voltage of  $V_L = 208 V$ .

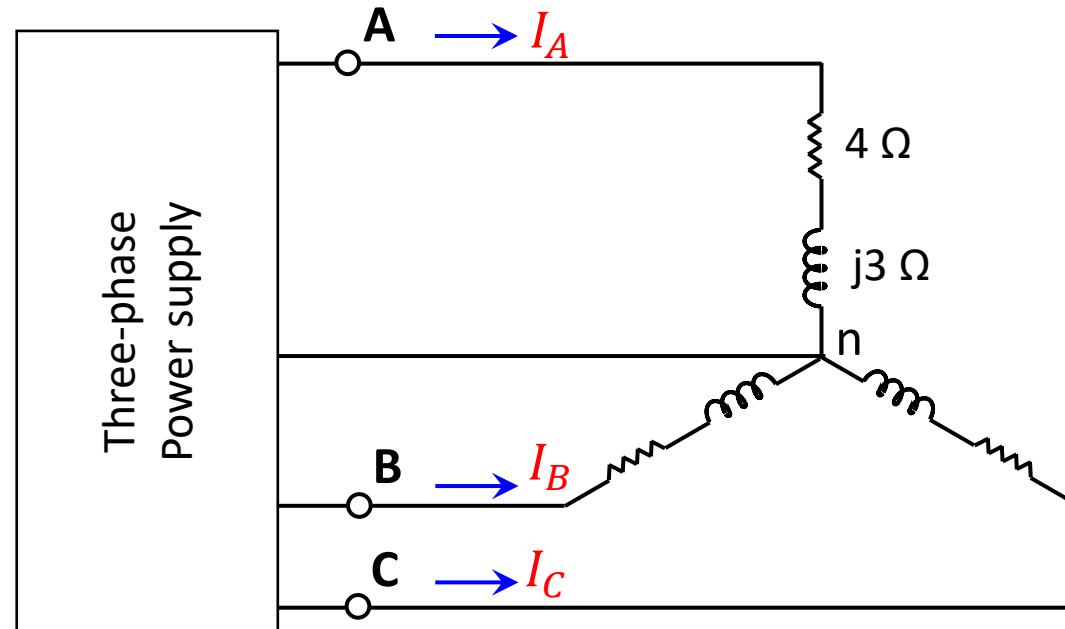a) Find the line current  $I_L$  b) Find the neutral current  $I_N$  c) Find the complex power of the load.



$$V_L = 208 \text{ V} \quad V_p = \frac{208}{\sqrt{3}} = 120 \text{ V}$$

Phase voltages across the load impedance:


$$V_{An} = 120 \angle 0^\circ \text{ V}$$

$$V_{Bn} = 120 \angle 120^\circ \text{ V}$$

$$V_{Cn} = 120 \angle -120^\circ \text{ V}$$




## Three phase systems:

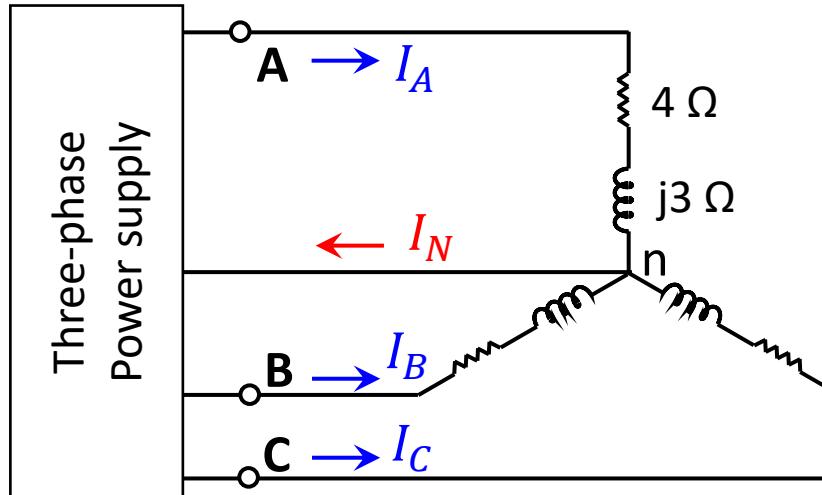

$$I_N = I_A + I_B + I_C$$

$$I_N = 24/-36.87^\circ + 24/83.13^\circ + 24/-156.87^\circ$$

$$I_N = 0$$

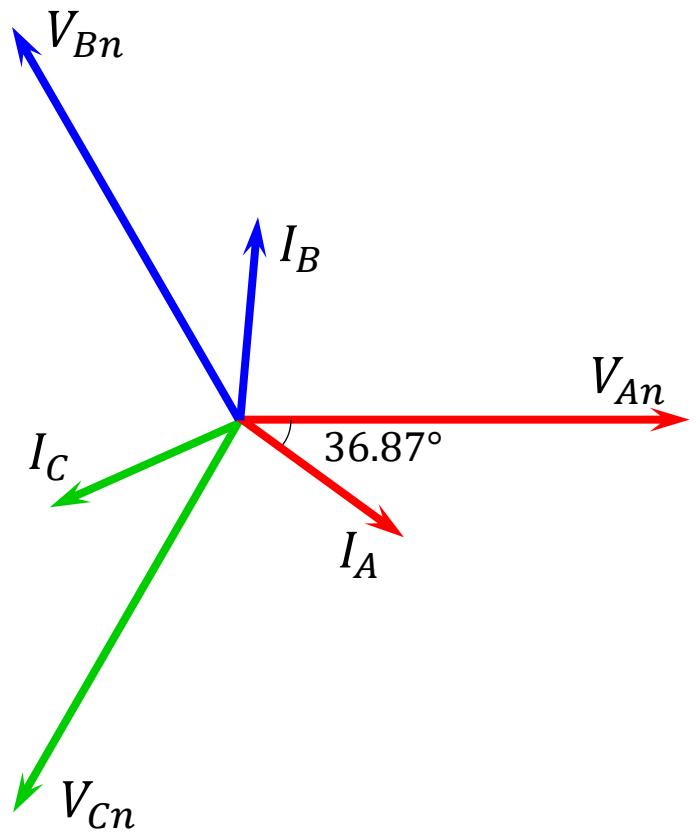



$$I_A = \frac{V_{An}}{Z_A} = \frac{120/0^\circ}{(4 + j3)} = \frac{120/0^\circ}{5/36.87^\circ} = 24/-36.87^\circ \text{ A}$$

$$I_B = \frac{V_{Bn}}{Z_B} = \frac{120/120^\circ}{(4 + j3)} = \frac{120/120^\circ}{5/36.87^\circ} = 24/83.13^\circ \text{ A}$$

$$I_C = \frac{V_{Cn}}{Z_C} = \frac{120/-120^\circ}{(4 + j3)} = \frac{120/-120^\circ}{5/36.87^\circ} = 24/-156.87^\circ \text{ A}$$



## Three phase systems:

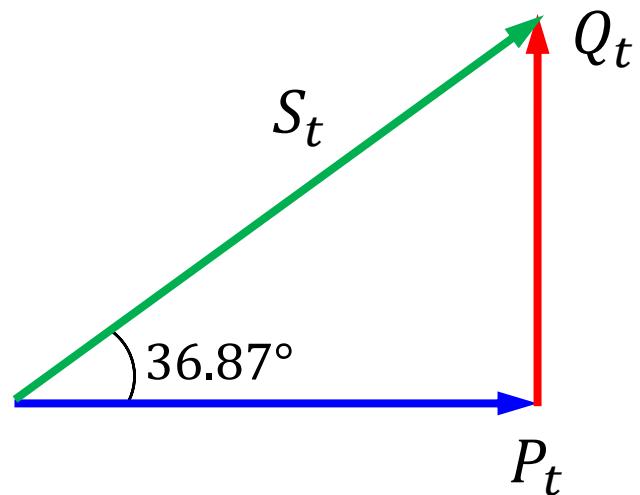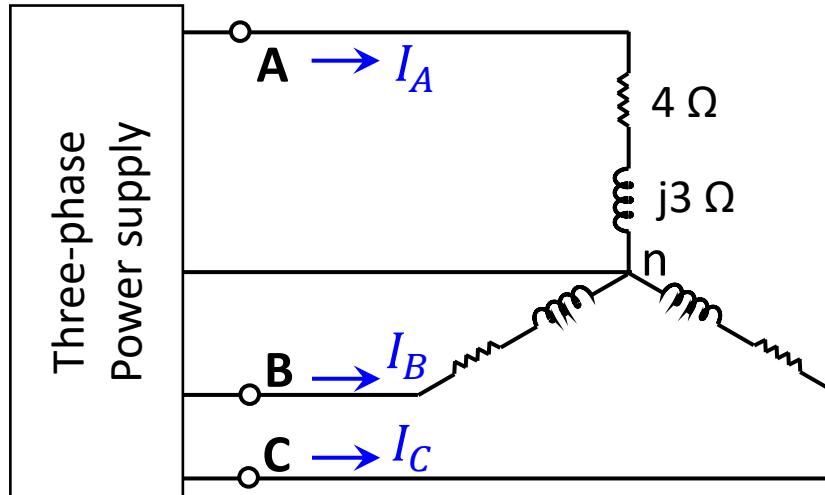

$$P_t = \sqrt{3} V_L I_L \cos \varphi = \sqrt{3} \times 208 \times 24 \times \cos(36.87^\circ) = 6.92 \text{ kW}$$

$$Q_t = \sqrt{3} V_L I_L \sin \varphi = \sqrt{3} \times 208 \times 24 \times \sin(36.87^\circ) = 5.19 \text{ kVAR}$$

$$S_t = P_t + j Q_t = 6.92 + j 5.19 \text{ kVA}$$

$$S_t = \sqrt{(P_t^2 + Q_t^2)} = \sqrt{(6.92)^2 + (5.19)^2} = 8.65 \text{ kVA}$$



## ▶ Three phase systems:

### Drill:

Repeat the last example for a  $\Delta$  connected load, with everything else unchanged.

- a) Find the line current  $I_L$
- b) Plot the phasor diagram of the voltages and currents
- c) Find the complex power of the load
- d) How do you compare the current s and voltages with the case of star connected load (results of the last example)?

Hint! In this case the load is supplied through a three phase three wires voltage source.

### Answer:

$$I_{ph} = 41.7 \text{ A}$$

$$I_L = 72.2 \text{ A}$$

$$P = 20.87 \text{ kW}$$

$$Q = 15.65 \text{ kVAR}$$



**Imagine a Blue Planet!**



**Imagine a Green Planet!**



**Together  
we can save  
our planet**

© 2010  
Dimitris Kotsopoulos  
www.diko.gr

owall.net

**Together we can fight the climate change.  
Together we can save our planet.**

A close-up photograph of bright green leaves with sunlight filtering through them. The leaves are backlit, creating a soft, glowing effect and casting long shadows. The veins on the leaves are clearly visible, and the overall color palette is dominated by various shades of green.

**Stay Green,  
Have a Green Day.**



## Reading list:

### Recommended text books:

- DeCarlo Lin, “*Linear Circuit Analysis*”, Oxford University Press, Second Edition, 2003
- W H Hayt, J E Kemmerly, S M Durbin, “*Engineering Circuit Analysis*”, McGraw-Hill, 9<sup>th</sup> Edition, 2019

