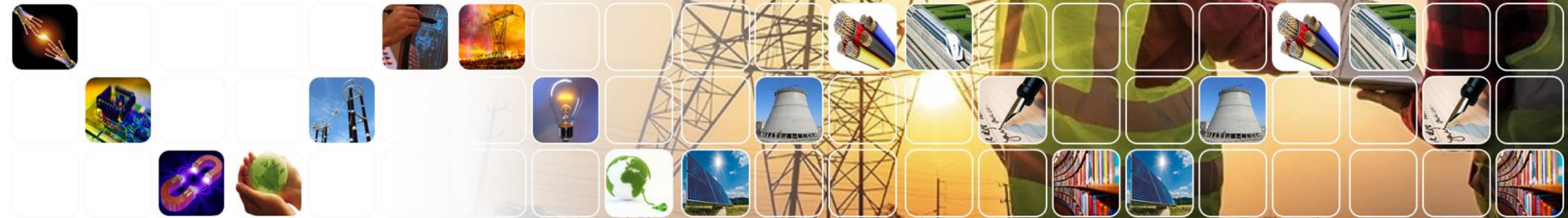


Electrical Engineering 2

ENGI2191

Power Factor Correction or Reactive Power Compensation





Lecture Objectives:

Aim of this lecture:

The aim of this lecture is to understand the concepts of power factor correction or reactive power compensation in electrical networks and power systems.

Intended Learning Outcomes:


At the completion of the lecture and associated problems you should be able to:

- Understand the concept of reactive power in electric networks.
- Identify the importance of reactive power in electric networks.
- Calculate capacitive reactive power for power factor correction.

Power Factor Correction or Reactive Power Compensation



Complex Power and Components:

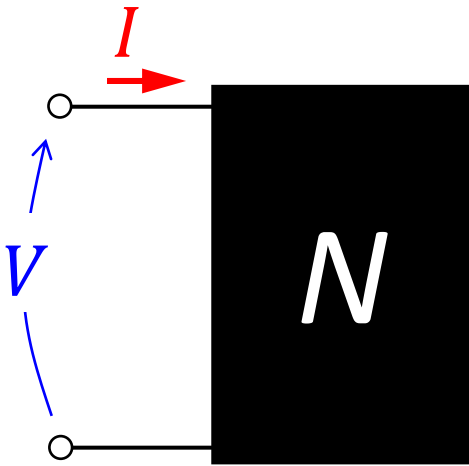

$$V = V_{rms} \angle \theta_v$$

$$I = I_{rms} \angle \theta_i$$

$$S = \underbrace{V_{rms} I_{rms} \cos(\varphi)}_{\text{Active power, } P} + j \underbrace{V_{rms} I_{rms} \sin(\varphi)}_{\text{Reactive power, } Q}$$

Active power, P

Reactive power, Q

$$P = \text{Re}[S] = V_{rms} I_{rms} \cos(\varphi) \quad \text{W, kW, MW}$$


$$Q = \text{Im}[S] = V_{rms} I_{rms} \sin(\varphi) \quad \text{VAR, kVAR, MVAR}$$

$$S = P + jQ$$

The magnitude of the complex power S is defined as apparent power:

$$S = |S| = \sqrt{P^2 + Q^2} = V_{rms} I_{rms} \quad \text{VA, kVA, MVA}$$

Complex Power and Components:

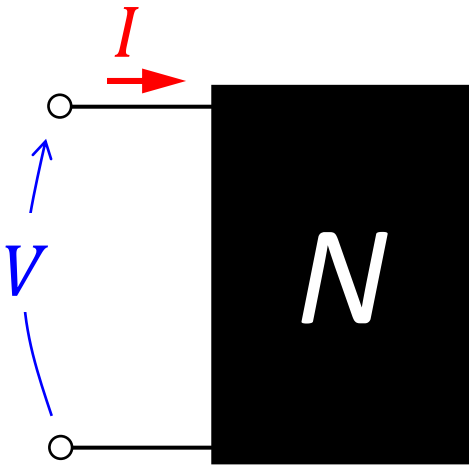


$$V = V_{rms} \angle \theta_v$$

$$I = I_{rms} \angle \theta_i$$

$$S = V_{rms} I_{rms} \cos(\varphi) + j V_{rms} I_{rms} \sin(\varphi)$$

$$S = P + jQ$$

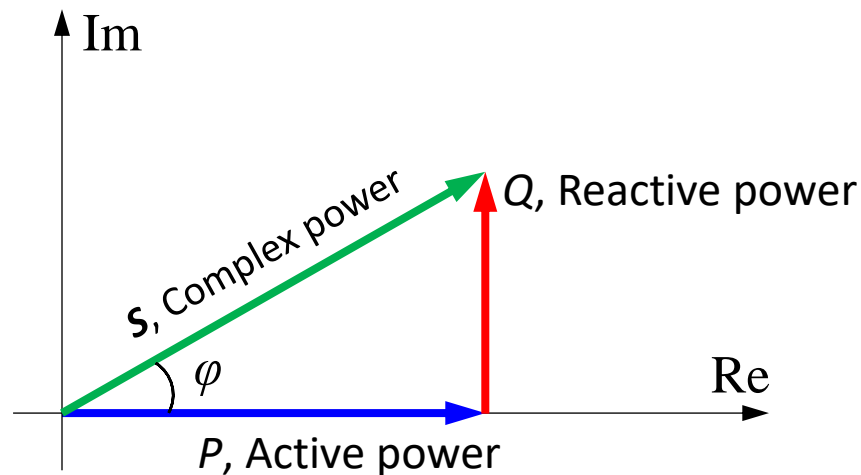The relationship between complex, active and reactive power is shown by a phasor diagram, known as “power triangle”:




$$P = S \cos(\varphi)$$


$$Q = S \sin(\varphi)$$

Power factor correction:

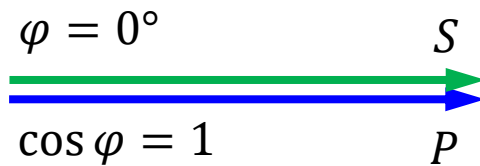
An electric generator with apparent power of $S = 100 \text{ kVA}$ is assumed. This generator supplies three different loads as follow:


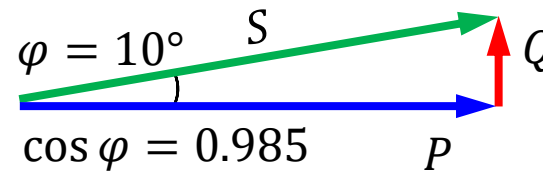
$$\begin{cases} P = 100 \text{ kW} \\ Q = 0 \end{cases}$$


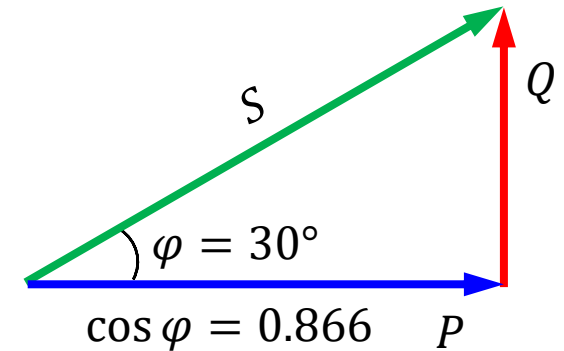
$$\begin{cases} P = 98.5 \text{ kW} \\ Q = 17.4 \text{ kVAR} \end{cases}$$




$$\begin{cases} P = 86.6 \text{ kW} \\ Q = 50 \text{ kVAR} \end{cases}$$



➡➡➡ The generator can generate 100 kW active power under unity power factor (resistive load). However, with inductive loads the effective power is reduced by a factor of $\cos \varphi$.

➡➡➡ **This results in lower operational efficiency.**


Power factor correction:

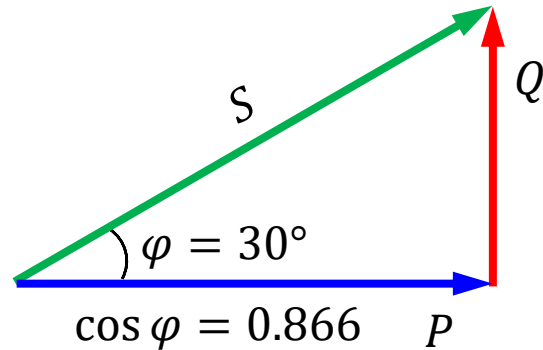

✗ Poor Power Factor

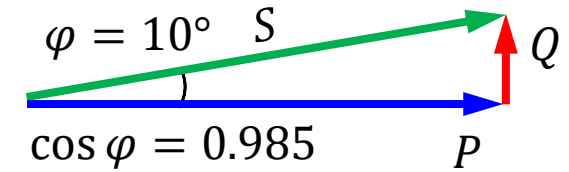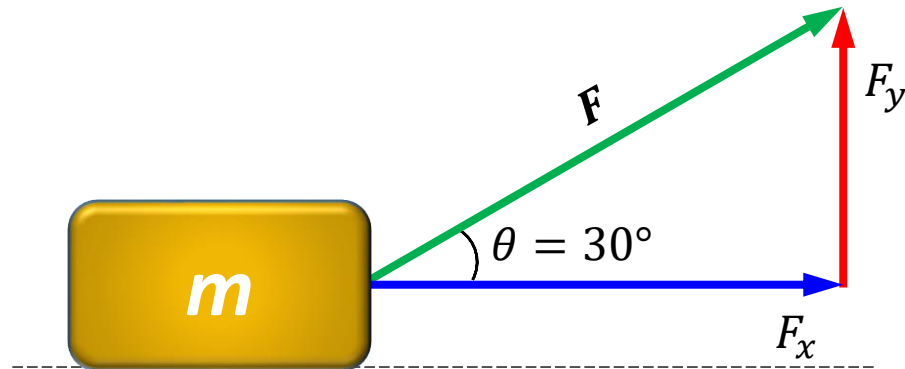


✓ Good Power Factor


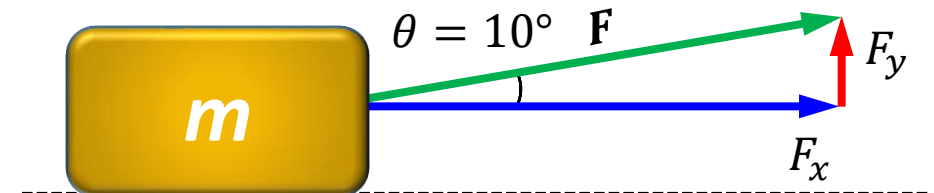


➡➡➡ In the design and operation of electric networks and power systems, high power factor (low reactive power) is always a key objective.


Power factor correction:

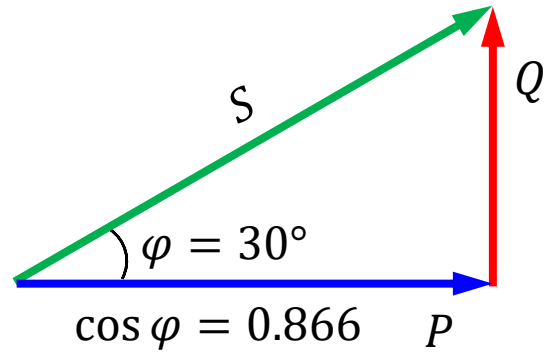

X Poor Power Factor

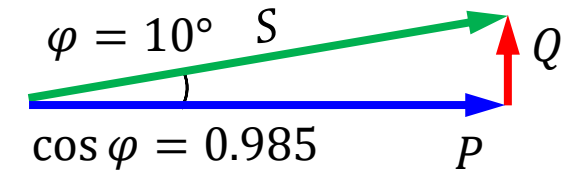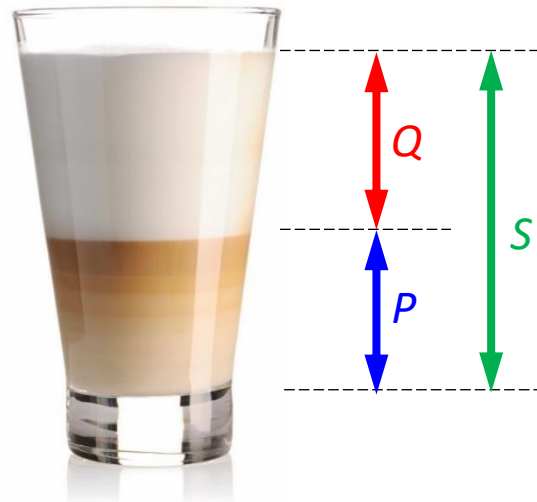

✓ Good Power Factor


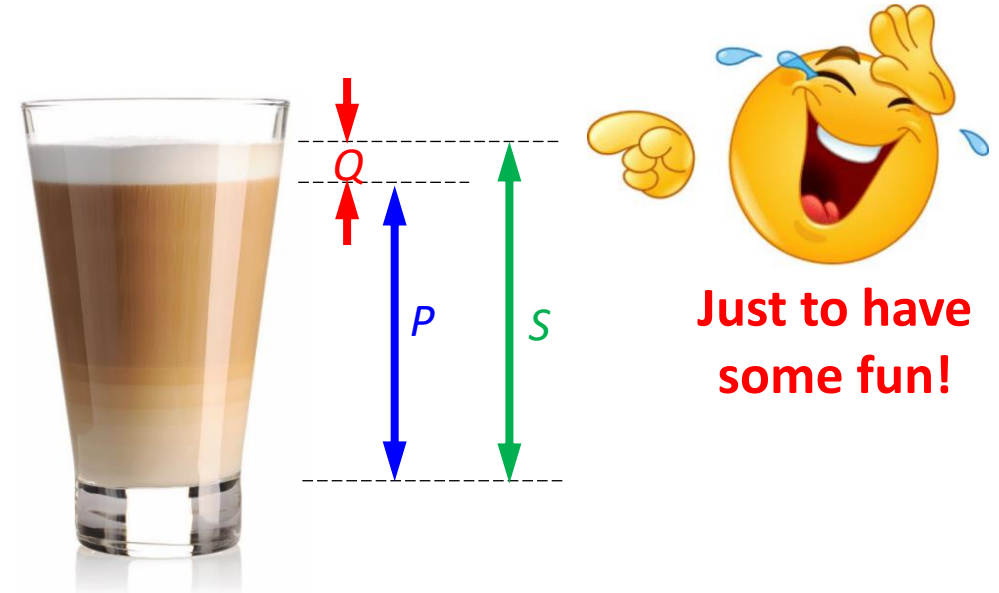


Power factor correction:

What is reactive power?

Majority of the industrial loads have inductive behaviour, it means they demand for reactive power.

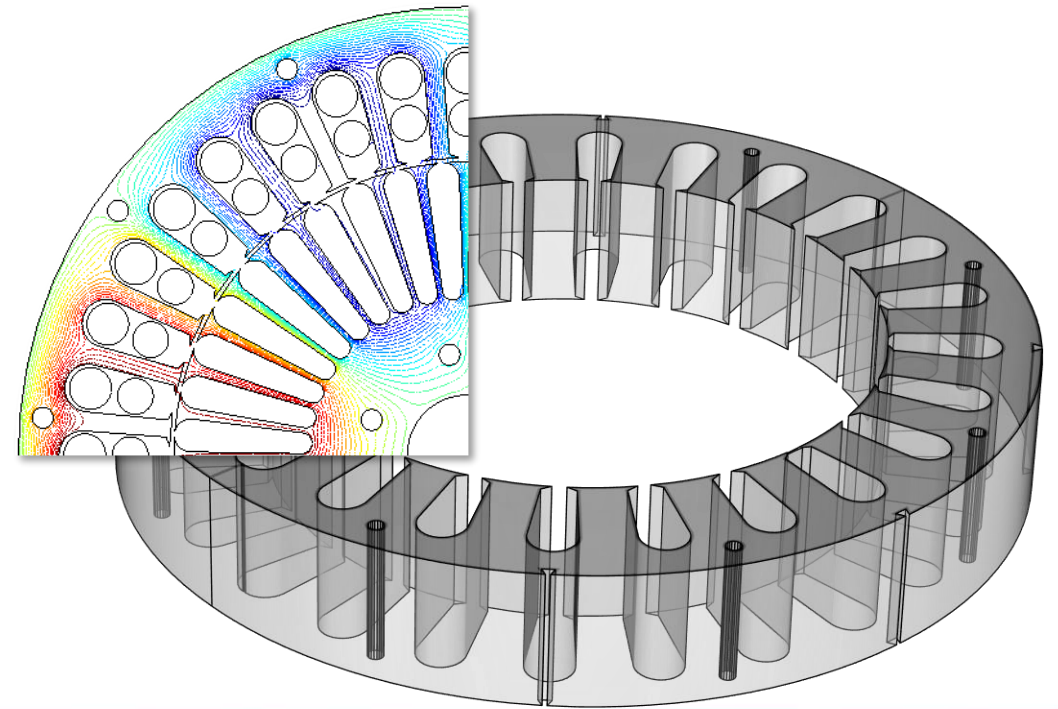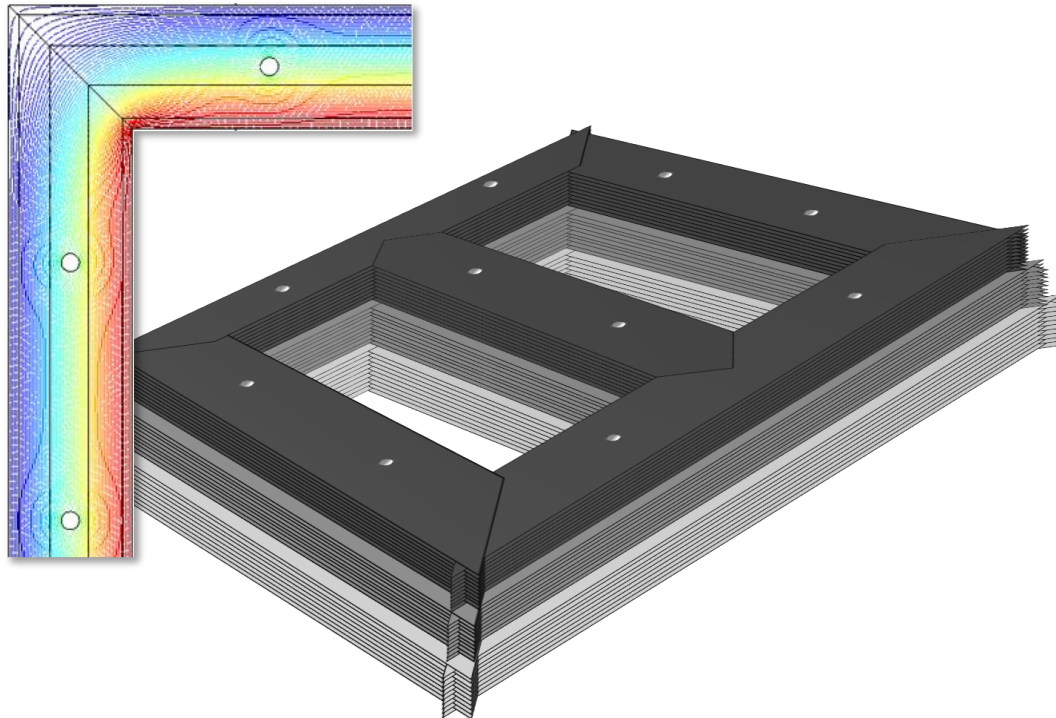For example, we need reactive power to magnetise magnetic cores of power transformers and electrical machines.



Power factor correction:

What is reactive power?

So, reactive power is demanded by industrial loads (inductive loads), however it reduces operational efficiency of the grid !!!




Power factor correction:

What is reactive power?


Reactive power has its origin in phase shift between current and voltage.

$$Q = V_{rms} I_{rms} \sin \varphi \quad [VAR]$$


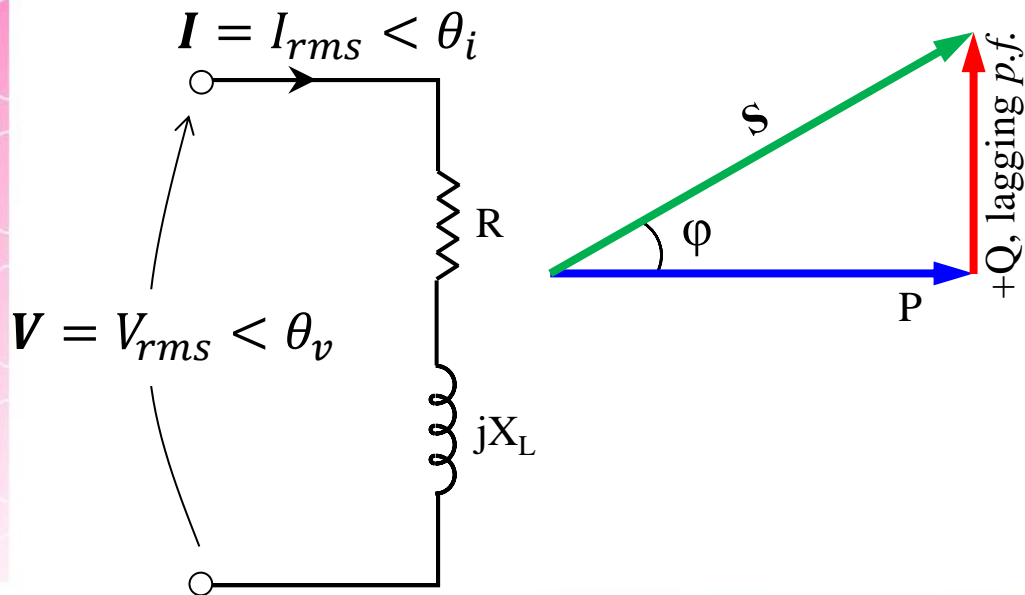
If current lags the voltage, then the device demands reactive power.



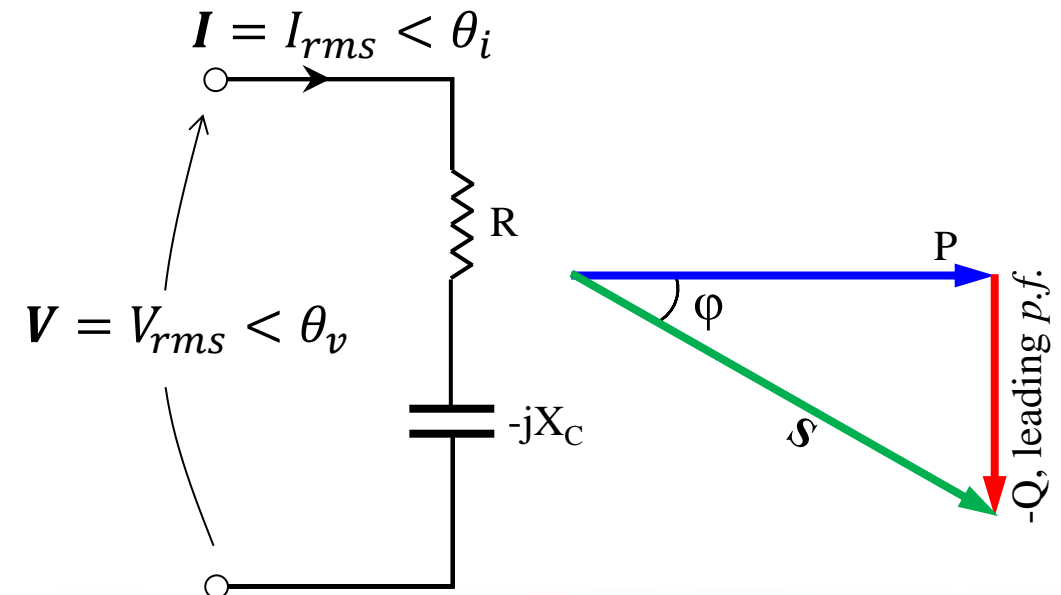
In contrast, if the voltage lags the current, then the device generates reactive power.





Power factor correction:

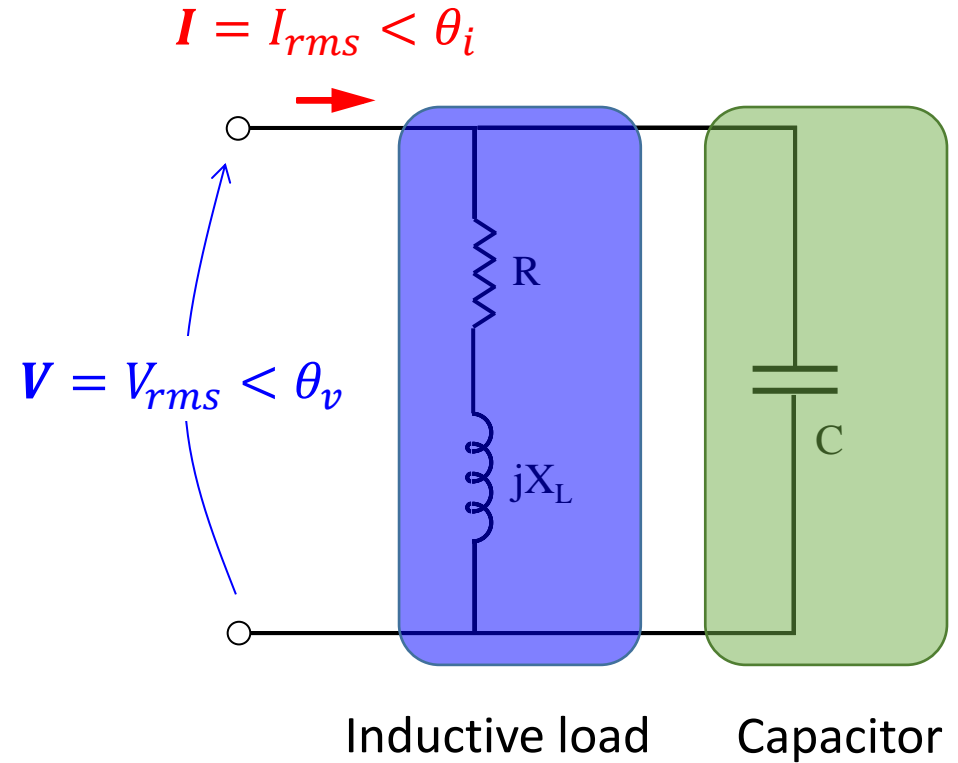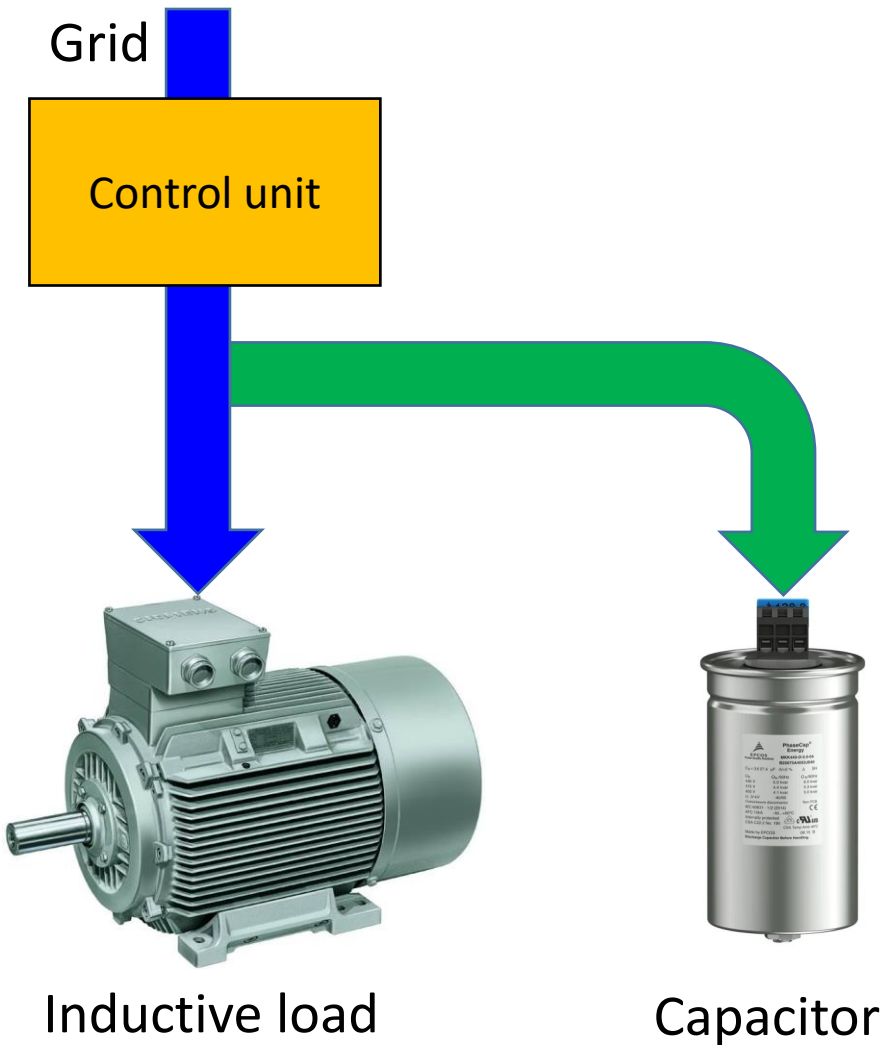

Power factor correction:

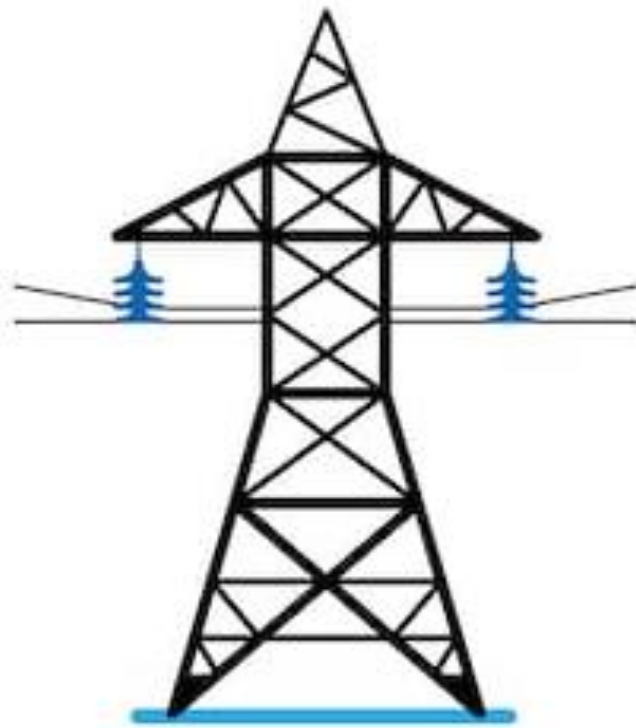


Grid

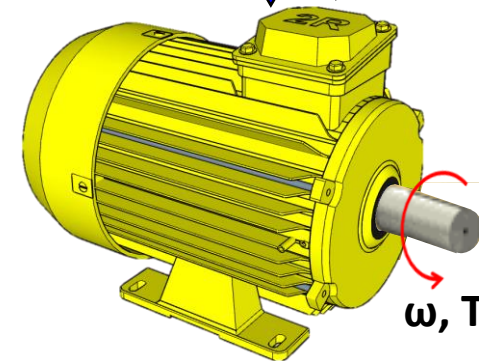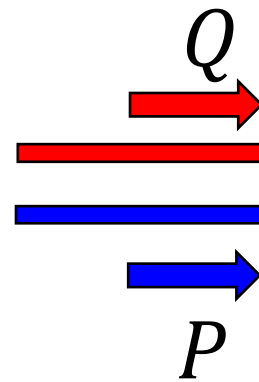


AC motor
(Inductive load)

Power factor correction:

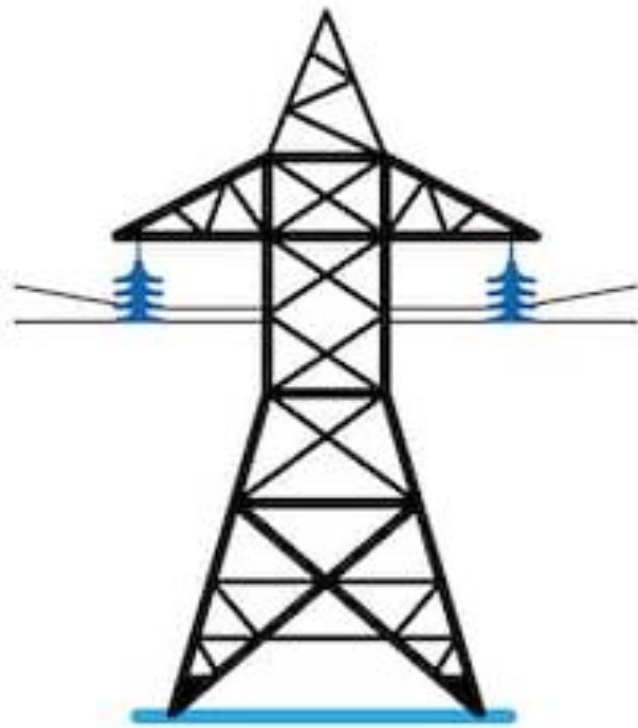

Grid

P

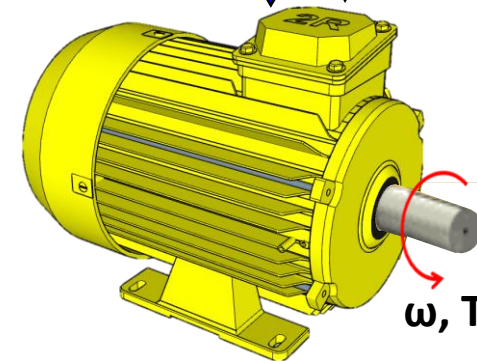

AC motor
(Inductive load)



Q



Capacitor

Power factor correction:

How much reactive power do we need?

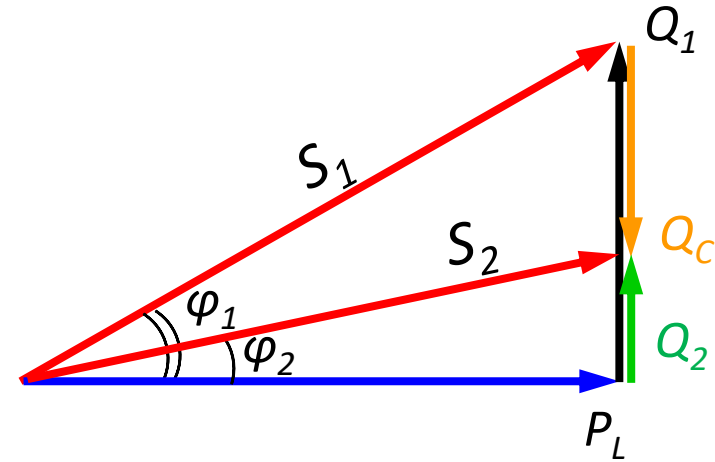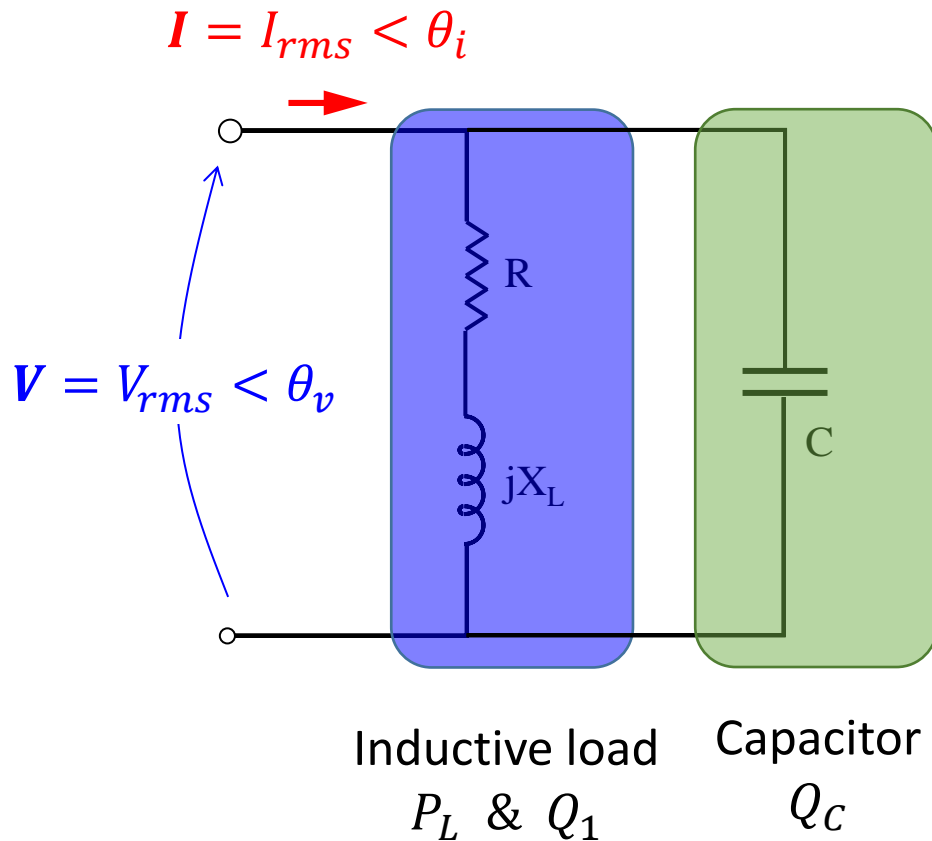

Apparent power before compensation


$$S_1 = \sqrt{P_L^2 + Q_1^2}$$

Apparent power after compensation

$$S_2 = \sqrt{P_L^2 + (Q_1 - Q_C)^2}$$

Power factor correction:

How much reactive power do we need?

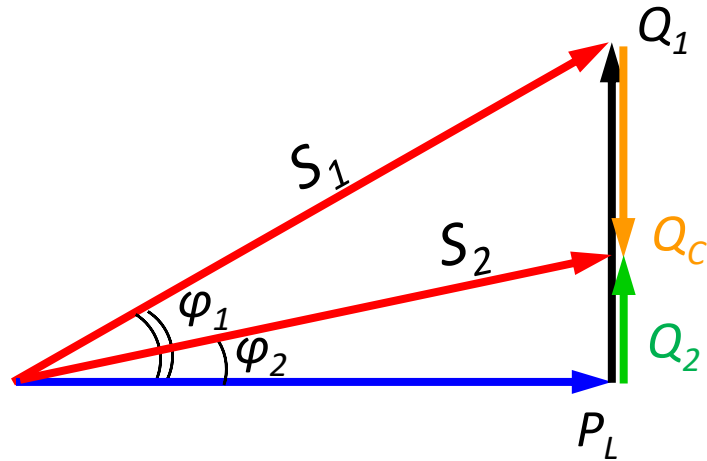

$$\begin{cases} Q_1 = P_L \tan \varphi_1 \\ Q_2 = P_L \tan \varphi_2 \end{cases}$$

$$Q_C = Q_1 - Q_2$$



$$Q_C = P_L \tan \varphi_1 - P_L \tan \varphi_2$$

$$Q_C = P_L (\tan \varphi_1 - \tan \varphi_2)$$

➡➡➡ In industrial loads, typically the corrected power factor will be 0.92 to 0.95.

Power factor correction:

Capacitive banks:



 HV substation (115 kV)



 Distribution network (11 kV)

 Low voltage network (400 V)



Power factor correction:

Capacitive banks:



 High Voltage Capacitor Bank

 Low Voltage Capacitor Bank



Power factor correction:

Different types of capacitors:



1 μ F, 100 V



2200 μ F, 50 V

Electronic Capacitor



**PhaseCap®
Energy Plus**
MKK415-D-15.0-04
B25675C4152J015

$C_N = 3 \times 92.4 \mu\text{F} -5/+5\%$ Δ SH

U_N	$Q_N / 50\text{Hz}$	$Q_N / 60\text{Hz}$
415 V	15.0 kvar	18.0 kvar
400 V	13.9 kvar	16.7 kvar
380 V	12.6 kvar	15.1 kvar

$U_i = 3/8\text{kV} -40/60$

Overpressure disconnecter Non PCB

IEC 60831 - 1/2 (2014)

AFC 10kA -40...+60°C

Internally protected

CSA C22.2 No. 190

Made by EPCOS 10 22N

Discharge Capacitor Before Handling.

**PhaseCap®
Energy Plus**
MKK415-D-15.0-04
B25675C4152J015

$C_N = 3 \times 92.4 \mu\text{F} -5/+5\%$ Δ SH

U_N	$Q_N / 50\text{Hz}$	$Q_N / 60\text{Hz}$
415 V	15.0 kvar	18.0 kvar
400 V	13.9 kvar	16.7 kvar
380 V	12.6 kvar	15.1 kvar

$U_i = 3/8\text{kV} -40/60$

Overpressure disconnecter Non PCB

IEC 60831 - 1/2 (2014)

AFC 10kA -40...+60°C

Internally protected

CSA C22.2 No. 190

Made by EPCOS 10 22N


Discharge Capacitor Before Handling.

Power Factor Correction Capacitor (PFC)

Power factor correction:

Different types of capacitors:

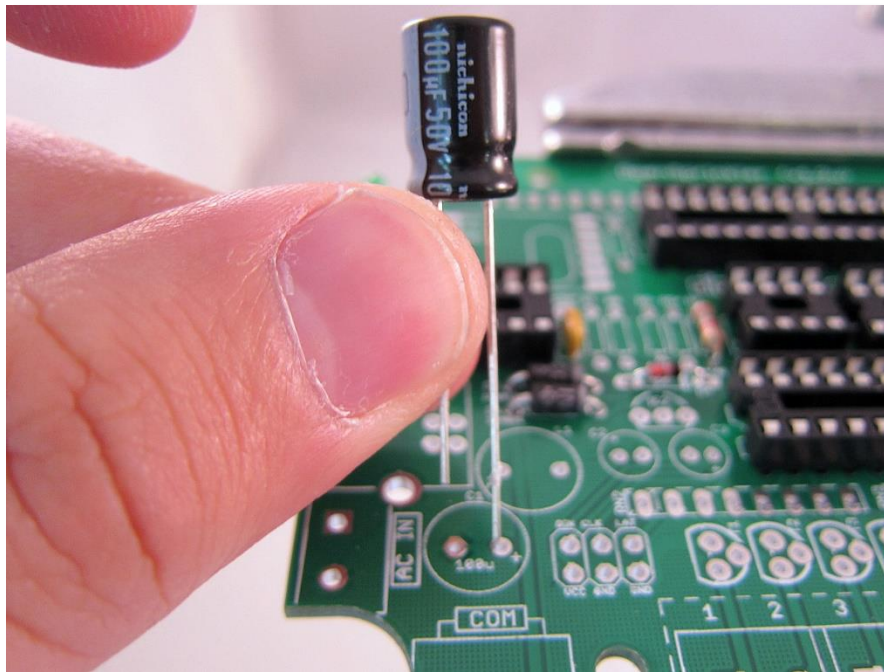In electronic circuits, capacitors are categorised by their capacitance in F . In electrical networks and power systems, capacitors are categorised by their reactive power in $kVAR$.



100 μF , 50 V capacitor in electronic circuit




75 MVAR capacitor bank at 150 kV;
Zandvliet, Belgium

Power factor correction:

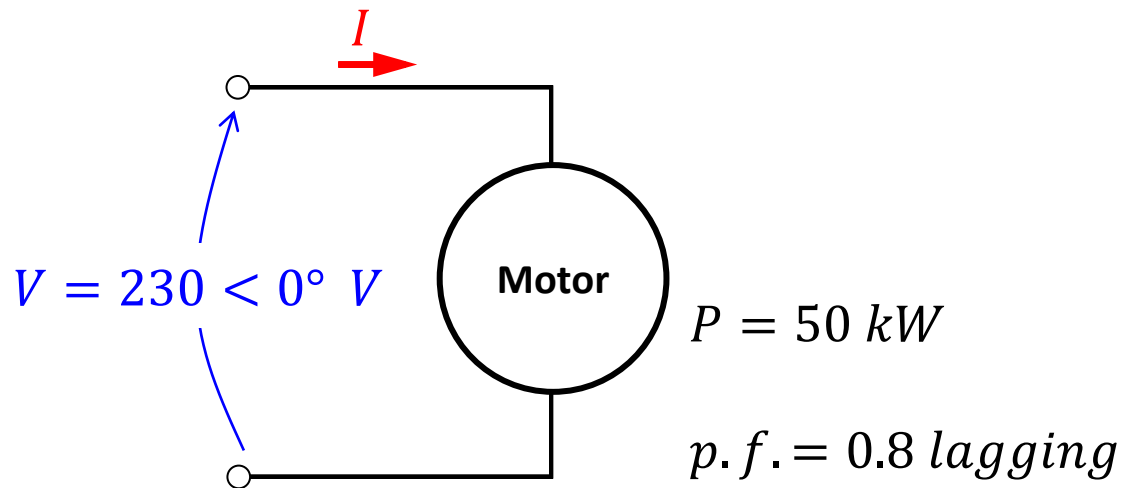Example:

An electric motor absorbs 50 kW active power at a power factor of 0.8 lagging. The motor is supplied through a voltage source with 230 V rms and frequency of 50 Hz.

- Find the complex power delivered to this motor.
- Find current of the motor i_L .
- Find the required capacitive reactive power to increase power factor to 0.95 lagging.
- Calculate the current of the source after compensation.



Power factor correction:

$$a) \quad P = V_{rms} I_{rms} \cos(\varphi) = S \cos(\varphi)$$

$$S = \frac{P}{\cos(\varphi)} = \frac{50}{0.8} = 62.5 \text{ kVA}$$

$$Q = V_{rms} I_{rms} \sin(\varphi) = S \sin(\varphi)$$

$$\cos(\varphi) = 0.8 \quad \Rightarrow \quad \varphi = 36.87^\circ$$

$$Q = S \sin(\varphi) = 62.5 \sin(36.87)$$


$$Q = 37.5 \text{ kVAR}$$

$$S = P + jQ = 50 + j37.5 \text{ kVA}$$

$$b) \quad P = V_{rms} I_{rms} \cos(\varphi)$$


$$I_{rms} = \frac{P_L}{V_{rms} \cos \varphi} = \frac{50 \times 10^3}{230 \times 0.8} = 271.74 \text{ A}$$
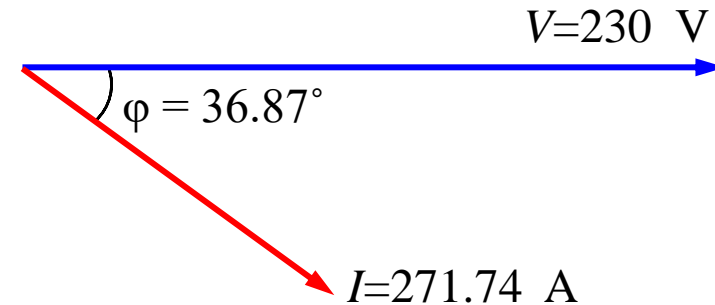
$$I = I_{rms} \angle \theta_i = 271.74 \angle -36.87^\circ$$



Power factor correction:

c)

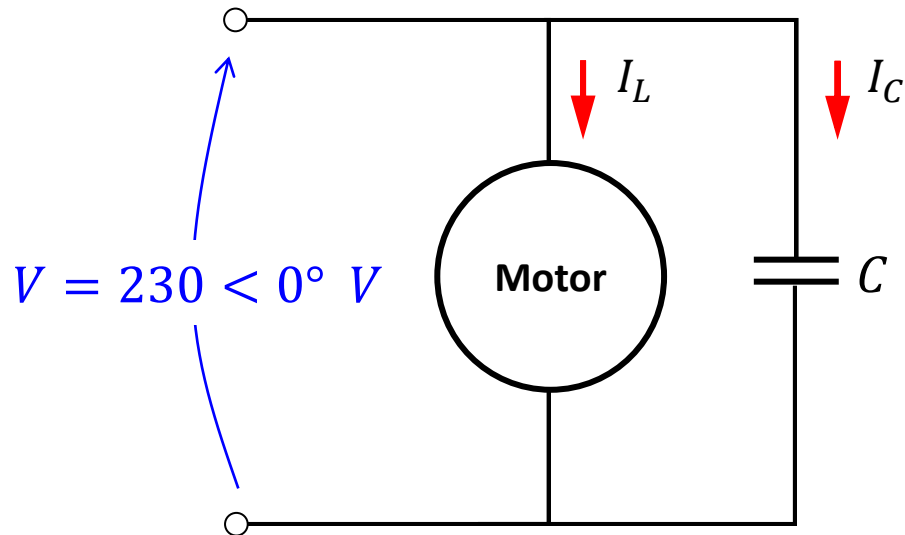

$$P = 50 \text{ kW}$$

$$pf_1 = 0.8 \quad \gggg \quad \varphi_1 = 36.87^\circ$$

$$pf_2 = 0.95 \quad \gggg \quad \varphi_2 = 18.19^\circ$$

$$Q_C = P_L (\tan \varphi_1 - \tan \varphi_2)$$

$$Q_C = 50 (\tan(36.87^\circ) - \tan(18.19^\circ))$$

$$Q_C = 21.07 \text{ kVAR}$$


$$Q_2 = Q_1 - Q_C = 37.5 - 21.07 = 16.43 \text{ kVAR}$$

$$S_2 = \sqrt{P_L^2 + Q_2^2} = \sqrt{(50^2 + 16.43^2)}$$

$$S_2 = 52.63 \text{ kVA}$$


Power factor correction:
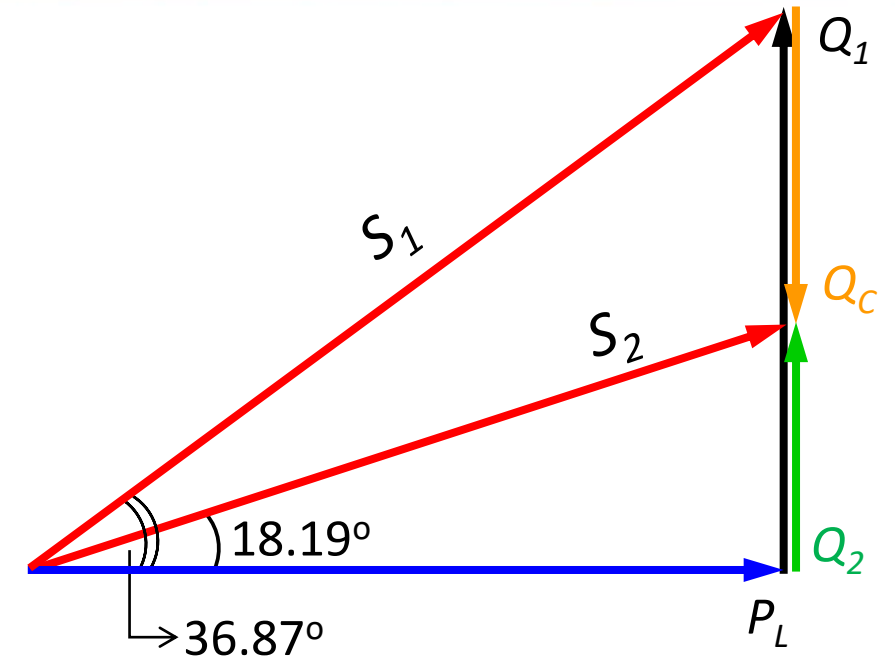
$$\begin{cases} P_L = 50 \text{ kW} \\ S_1 = 62.5 \text{ kVA} \\ Q_1 = 37.5 \text{ kVAR} \end{cases} \quad \begin{cases} S_2 = 52.63 \text{ kVA} \\ Q_2 = 16.43 \text{ kVAR} \end{cases}$$



$$d) I_{rms2} = \frac{P_L}{V_{rms} \cos \varphi_2} = \frac{50 \times 10^3}{230 \times \cos(18.19)} = 228.82 \text{ A}$$
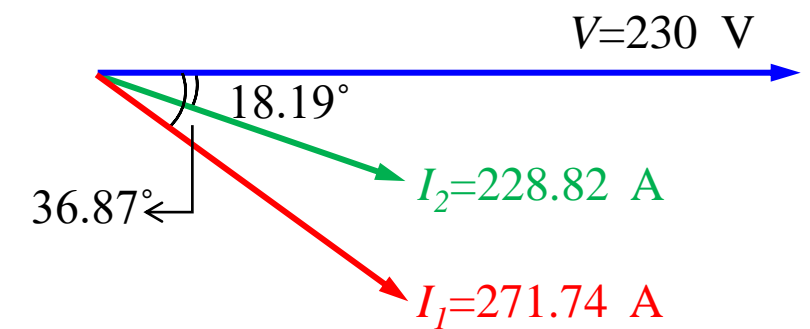
$$I_2 = I_{rms2} \angle \theta_i = 228.82 \angle -18.19^\circ \text{ A}$$




Practice: Why $I_1 \cos \varphi_1 = I_2 \cos \varphi_2$?

Power factor correction:

Drill:

The following circuit operates at $\omega=500$ rad/s and rms voltage of 100 V.

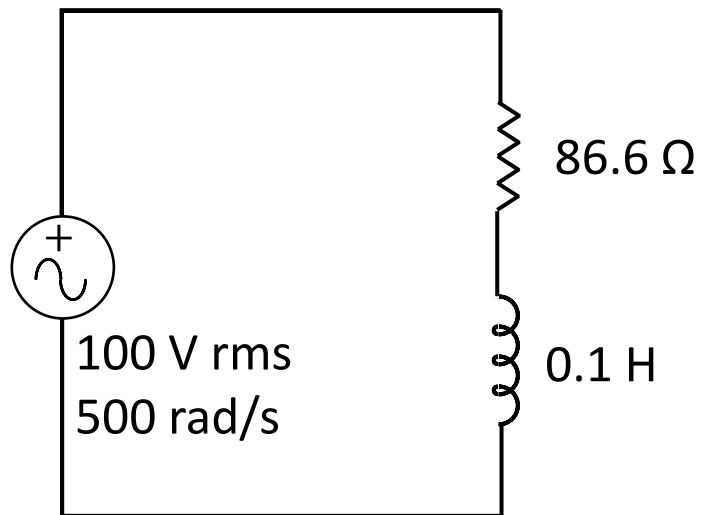- Find current of the load.
- Find the complex power delivered to this load.
- Find the required capacitive reactive power to correct power factor to 0.94 lagging
- Draw the power triangle.
- Calculate the power delivered by the source after compensation.



Answer:

a) $I = 1 \angle -30^\circ \text{ A}$

b) $S = 86.6 + j50 \text{ VA}$

c) $Q_c = 18.53 \text{ VAR}$

Happy Halloween



Module description:

Recommended text books:

- DeCarlo Lin, "*Linear Circuit Analysis*", Oxford University Press, Second Edition, 2003
- W H Hayt, J E Kemmerly, S M Durbin, "*Engineering Circuit Analysis*", McGraw-Hill, 9th Edition, 2019

